



## Editorial

ON the 12th and 13th of August, Australia's amateur transmitters held their annual Remembrance Day Contest under the auspices of their national society, the Wireless Institute of Australia—the oldest radio society in Australia, and one of the oldest in the world.

In this contest, the amateurs resident in one state attempt to contact as many amateurs as possible in other states, within the space of 24 hours. The state which wins the contest relies not only on the scores of its best six competitors, but on the proportion of its amateurs who took part.

Thus there is no individual winner of the contest, only a special cup held for one year by the state which amasses the highest score.

The contest was inaugurated after the last war as the amateurs' way of paying tribute to many companions and friends who lost their lives in it. It provides special opportunity of saying "we remember" with every contact made throughout the length and breadth of the land. Many old comrades-in-arms exchange brief greetings during the contest, each, no doubt, with a thought for a mutual friend who to this dear land of ours came back no more.

I think it was a stroke of genius which inspired those concerned to make this a contest without an individual winner. For it is just as much a celebration as a contest, and in such things individual performances don't much matter. In making their appearance on the air, even for a short time, each amateur pays his own tribute.

This contest, I think, will become the most important of all those in which we take part, and certainly it should be. There is a difference about it, an unspoken realisation of its significance, which no other contest can have. There is a splendid atmosphere of good fellowship with it, more reminiscent of a happy reunion than of a grim battle for points.

Those amateurs in whose honor the contest is held would, I am sure, be happy to know their names were linked with an event which can do so much to bring Australian amateurs together. Unfortunately, the great size of our country separates us by hundreds of miles. But we are never really separated as long as we are on the air, and we never needed the sense of our unity more than we do at the present time.

Don't let us forget this contest. This year there was a fine roll-up. See that next year and the year after we make it the highlight of our national life on the air.

*John Moyle*

## INDEX

	Page
Radio Telephone For Sydney	3
Will A Saucer Really Fly?	9
Britain's Helicopter Air Buses	11
20 Years From Now	13
Your Finger Prints Are Permanent	14
Technical Review	19
How It Works—Making Plastics	23
News And Views	25
Let's Buy An Argument	28
The Serviceman Who Tells	33
Putting Your CRO To Work	37
New Radio Lamps For Old	40
A Course In Television	45

	Page
Here's Your Answer Tom	50
The 1950 Pentagrid-Four	52
Fitting An Extension Speaker	61
A Standard Multimeter	64
Trade Reviews and Releases	71
A Reader Built It	74
Super-Fast Versatile Bomber	77
Radio Control of Modern Aircraft	79
Shortwave Notes	90
Ham Notes by Bill Moore	93
Off The Record	96
Answer To Correspondents	100

# RADIO

AND HOBBIES IN AUSTRALIA

A NATIONAL MAGAZINE  
OF RADIO, HOBBIES AND  
POPULAR SCIENCE

### EDITOR

JOHN MOYLE  
S.M.I.R.E. (AUST.)

### TECHNICAL EDITOR

NEVILLE WILLIAMS  
A.M.I.R.E. (AUST.)

### TECHNICAL STAFF

RAYMOND HOWE  
MAURICE FINDLAY  
PHILIP WATSON

VOL. 12 No. 6

### SUBSCRIPTION RATES

C'wealth & New Guinea	N.Z.	Overseas British	Foreign
1 year 12/-	13/-	15/-	18/8
6 mths. 6/-	6/6	7/3	7/9

Published on the first Friday of each month by Associated Newspapers Ltd., 60-70 Elizabeth St., Sydney.

Phone .. .. . BO333

### OUR COVER PICTURE

At the famous Greenwich Royal Observatory, founded by Charles II in 1675, an assistant turns the handle to open the roof of the solar building before photographing the sun. The Royal Observatory has now moved to Herstmonceux Castle, Sussex.



Model PA: Dynamometer - type Power Analyser.

Model VTM: Vacuum Tube (probe) Multimeter.

Hearing Aid.

Palec Electronic photo-flash models 60-1,000 joules.

Palec exposure meter.

Model SG1 Signal Generator.

Model M30: Multimeter.

Model VCT2: Valve and Circuit Tester.

# Make No Mistake!

Errors cost you time, money, reputation. Men of judgment make no mistake. They use 'Palec' instruments—the best guarantee of accuracy and quality.



Palec oven temperature gauge.



Moving coil panel instruments.



Moving iron panel instruments.



Sector-type Pyrometers.

## REMEMBER

Palec products are AUSTRALIAN made, and backed by AUSTRALIAN factory service.



# Paton Electrical

PTY. LTD.

Manufacturers of all Types of Radio & Electrical Test Equipment & Meters.


90 VICTORIA STREET, ASHFIELD, SYDNEY.

Tels.: UA 1923-1960-1982. Telegrams: "Palec."

★ PALEC ARE THE SOLE AUSTRALASIAN AGENTS FOR THE WORLD-FAMOUS "MEGATRON" BARRIER-LAYER PHOTOCELLS—STOCKS ON HAND—ENQUIRY INVITED



# RADIOPHONE COVERS METROPOLIS

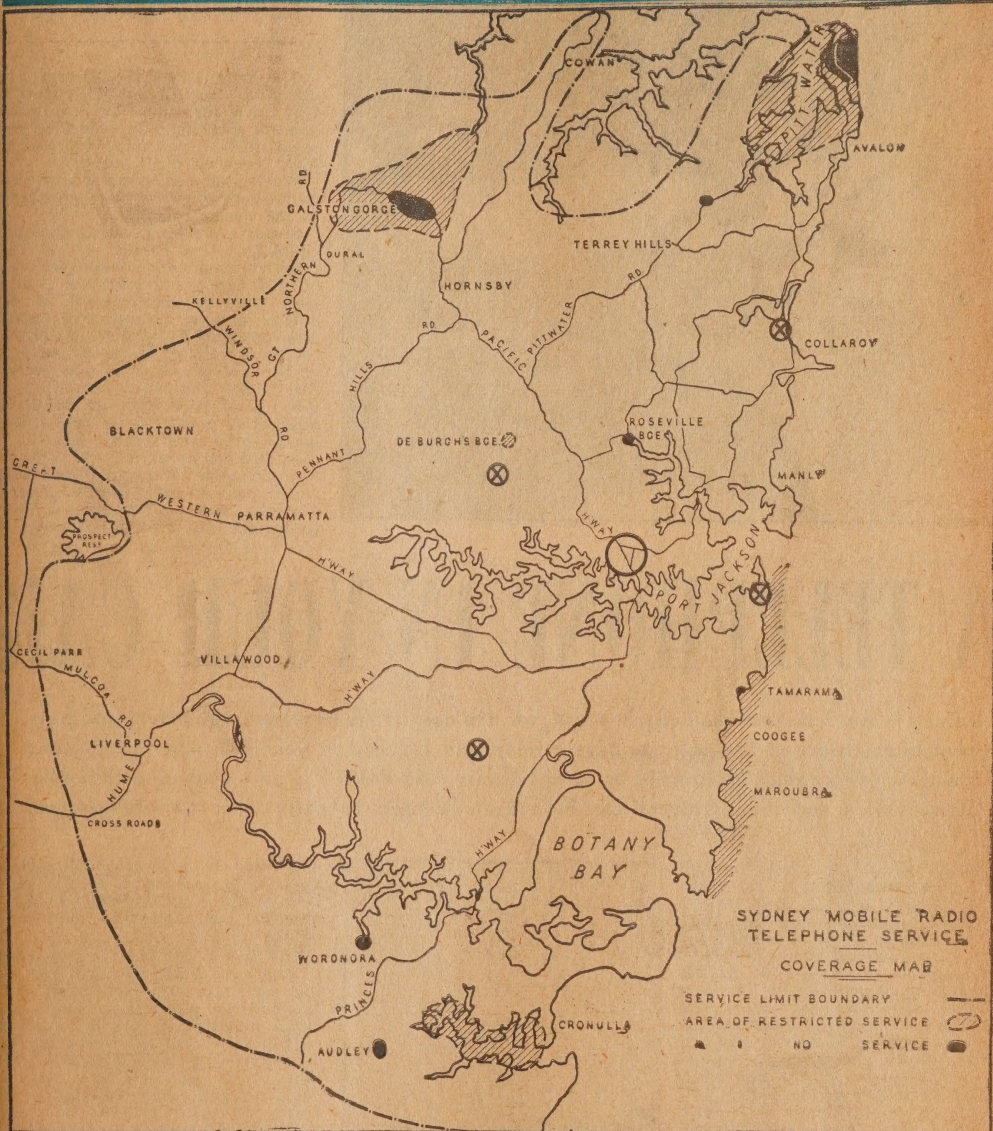

**T**HIS map is supplied to all users of the new radio-phone service so that they will know when they are within range of the main transmitter. On it we have marked the position of the transmitter at North Sydney, and also of the remote receiving positions at Collaroy, South Head, Bexley and Ryde. The "dash-dot" line shows the approximate limits within which you should be able to place and receive calls with about the same clarity as through the normal telephone. The shaded area indicates that there may be low-lying spots from which contact might be difficult or impossible. The black areas correspond with very badly shielded

places from which the radio waves from the car will almost certainly not be heard by any of the receivers.

Experience has shown that, provided your car is on a high spot within virtual visual range of North Sydney, calls may be placed well beyond the service area. For instance there will be many places along the Blue Mountains Road, even as far as Mount Victoria, from which good results will be obtained, but it would be unwise to include them within a specified coverage limit. Some technical knowledge would be necessary to "pick your spot" under these conditions, and for that reason, the average user should not expect more than the PMG engineers have indicated on the above map.





The telephone operates just like a normal handset except that a "Press to Talk" lever is squeezed by the fingers when speaking—released when listening. Handset clips into place on small control panel, when not in use.

The only essential difference in operation from a normal phone is that Uncle Joe cannot break in while you are speaking, and each time you speak to him, you must depress the little lever on the handset.

When your conversation with him is finished, you hang up your phone in the normal manner.

So far everything sounds absurdly simple, and so in fact it is. The radio communication engineers who have designed and built the system have done an excellent job of reducing a most complicated matter into ordinary telephone procedure, requiring no skill at all on the part of the operators, or of you either. But before you make your way to the nearest post office in search of application forms, there are a few points to be considered.

In the first place, one doesn't buy complete transmitter-receivers which possess such simply-operated control systems for nothing. Your equipment will have to be supplied


# A TELEPHONE IN YOUR CAR

Sydney is the first Australian city in which, for the cost of the necessary equipment and payment of the required fee, you can have a telephone installed in your car, and talk to your friends within a radius of 20 miles or so of the city. The PMG has now opened a radiotelephone service, and already several cars have been licensed to carry their own telephones.

**T**HIS apparent miracle is brought about by having installed in the car boot a small radio transmitting and receiving station which, in conjunction with a small roof aerial and a normal telephone handset, provides a radio link to the telephone exchange to take the place of the wires normally used. The telephone handset is mounted in some convenient manner (determined by the people who made the equipment you bought) on the dashboard. When Uncle Joe wishes to tell you that you have left the picnic hamper behind in your hurry to depart on a car trip, he picks up his phone at home, asks for B0707, gives your car numbers, and hangs on.

You, bowling along the highway with your radiophone switched on, suddenly hear a bell ring behind the dash. If you can drive with one hand, you pick up your handset in the car, press a "talk" lever in the handle with your finger, and answer in the normal manner.

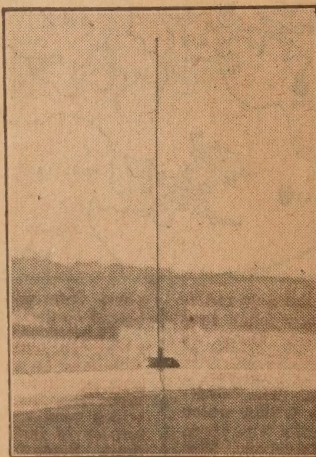A few seconds later, you are talking to Uncle Joe and, in all probability, preparing to return for the missing viands.



A small vertical aerial mounted on the car roof accommodates both sending and receiving. It is about 18 inches long and may be flexible metal rod.

and fitted by a firm which makes such things, and whose designs have been accepted by the PMG as suitable for operation with their part of the system.

The cost to you will be from £200 to £300, for which you will receive the transmitter-receiver fitted into the boot of your car, a short, rod aerial mounted on the roof, and a control panel and hand-set mounted somewhere on the dashboard. In other words, you will now carry a complete radio station adjusted to the correct frequency of about 160 megacycles, and for which a licence will be issued by the PMG.

This licence and rental will cost you £51 per year, and each call you make will cost you 6d. Your callers, too, will be charged 6d each time they ring you up.

This high charge isn't there to discourage you, or to make huge sums of money for the PMG. As we shall presently show, the cost to them of installing their part of the works is considerable, and requires highly trained technicians for its construction and maintenance.

It is possible to install a receiver



only in your car, which will allow messages to be passed to you on the road, but to which you cannot reply. This system is much cheaper for you to install and costs only about £20 per year. Its use is rather limited, however, and it is doubtful whether many will find it worthwhile.

Subscribers to the system can be pretty certain of obtaining an excellent service from their radio-phones. At the invitation of the Department, we were able to inspect the complete installation soon after it was officially opened, and to make a test run in a car fitted with a standard radiotelephone made by a Sydney manufacturer.

## TEST RUN

During the run, which embraced quite a large section of the service area, no trouble was experienced in making or receiving calls from the car. The standard of the service, and the clarity of the voices, was approximately the same as that obtained from the ordinary telephone in the home. It makes little difference whether the car is stationary or in motion, although the mechanical noises when the car is moving do make it a little harder to hear, as is only to be expected.

The apparatus is powered from the car battery, and may require up to 40 amps when transmitting—5 or 6 amps during "standby."

This is a high battery drain, and may call for extra batteries or other modification to the car's electrical system.


On page three appears a map showing the service area of the telephone, and the location of the transmitting and receiving aerials operated by the PMG. From our experience with mobile radio, we would say that this map presents the service area quite accurately, with the strong probability that in many cases it will substantially be exceeded when the car itself is on high ground.

## MAIN AERIAL

The first technical problem faced by the PMG engineers was how to get a strong signal into your car anywhere in the service area, bearing in mind that radio waves at such high frequencies travel much like light waves, and are not good at diving down deep cuttings or behind steep hills. The problem was solved by first of all using a fairly high-powered transmitter which radiates 250 watts of power, and feeding it to a very high aerial.

The aerial is, in fact, mounted on top of the FM aerial tower which most people have seen at North Sydney, and from which visual range or near it can be had to almost any spot within the city and suburbs.

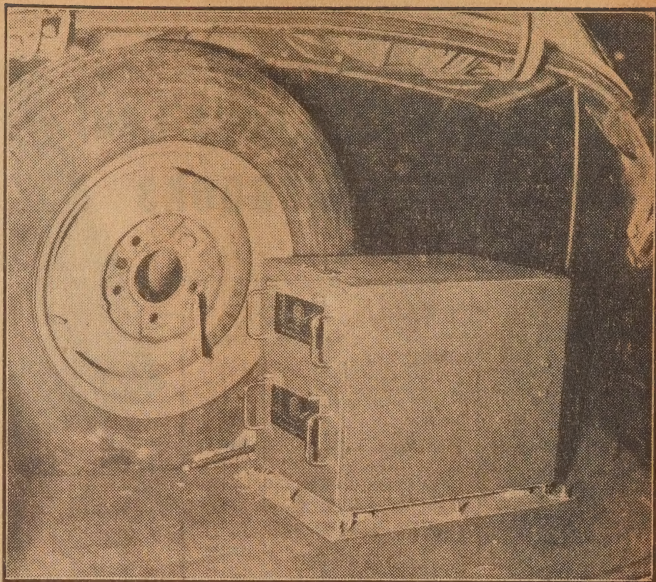This aerial is so made that it shoots the signals close to the ground in all directions, and very little up in the air. Actually the aerial is known as a "double disc" and the flattening out of its radiation pumps up the available power by 4 decibels, quite a useful increase over a plain aerial. As this gain just about balances out the loss in the cable which runs down to the trans-



Several commercially made transmitter-receivers are available approved by the PMG. This one is quite small but complete.


mitter, the full capability of the transmitter is made use of.

The control circuits to the transmitter run through wires to a telephone switch-board so that it can be remotely operated by the switch-board operator. She, of course, need know nothing of radio, because the whole intricate mass of wires and relays are quite automatic, just as


they are in normal telephone technique.

It is more difficult to provide clear, strong signals back from the cars, because their transmitters are powered with only about 25 watts, and their aerials are close to the ground, often in low-lying spots some distance from the transmitter.

The receivers which send signals

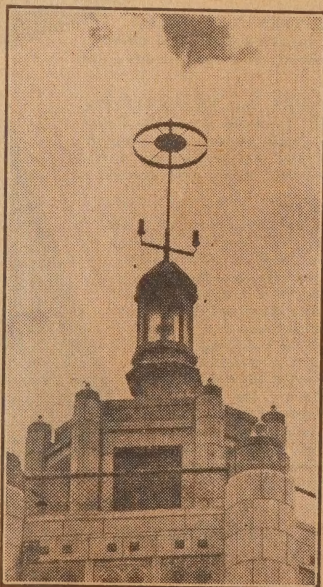

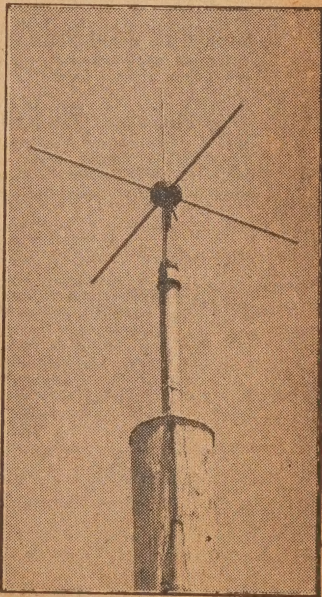
Many have already noted the receiving aerial on the Grace Building tower, Sydney, one of the city's highest points.



A standard "ground plane" aerial is mounted on a tall pole or high structure at remote receiving points.


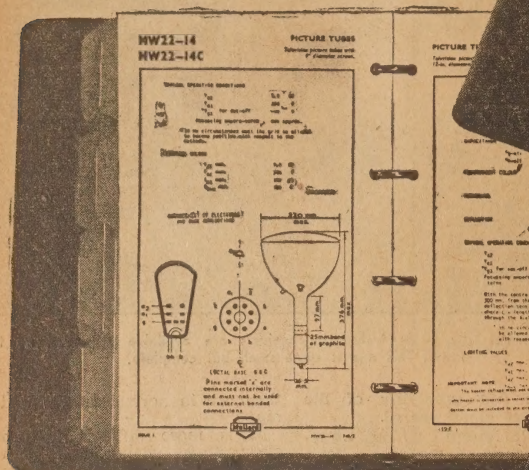
# Mullard Loose Leaf VALVE DATA HANDBOOKS



- Vol. 1: RECEIVING VALVES — EQUIPMENT TYPES, CATHODE RAY TUBES, MISCELLANEOUS TUBES.** Includes television picture tubes, photographic flash tubes, voltage stabilising tubes, accelerometer tubes and general valve data.
- Vol. 2: RECEIVING VALVES FOR MAINTENANCE ONLY.** This volume contains full data on superseded Mullard valve types as supplied for replacement and maintenance of equipment already in the field.
- Vol. 3: POWER VALVES and RECTIFIERS for TRANSMITTING AND INDUSTRIAL EQUIPMENT.** Contains data sheets and useful information relating to high power water-cooled transmitting valves, silica envelope valves, heavy duty rectifiers, VHF valves, etc., operating notes and general nomenclature relating thereto.

The three 9" by 7" volumes are leatherette covered with gold lettering and have snap rings and contain full technical data on the comprehensive range of Mullard valves. Each valve group is provided with an indexing sheet. Compiled and produced by Mullard Electronic Products Ltd., London, the data completes the gap in your valve information and comes at a most opportune time—with the expanding field of television and industrial electronics. A practical and essential addition to your reference library. The cost is £6/6/-, inclusive of the first two years' subscription for amendments and additions, subscription 15/- per year thereafter.

**Mullard** THE MASTER VALVE

Mullard Australia Pty. Ltd.  
35-43 Clarence St., Sydney  
Representatives in Australia  
Products Ltd., London, Australia  
Secure your set now by writing or cutting out this coupon and enclosing a cheque or money order for £6/6/- to Mullard Australia Pty. Ltd., Box 100, G.P.O., Sydney.

Name: \_\_\_\_\_  
Street: \_\_\_\_\_  
Town: \_\_\_\_\_  
State: \_\_\_\_\_

M5-49



back to the exchange, therefore, are placed round the various suburbs in the highest possible places, each with its own aerial on top of a pole, or a high and convenient structure, such as a water tower. Careful placement of these means that no matter where your car may be at the time, it is always within good operating distance of one or other of these aeri-als.

Wires connect each remote receiver with the exchange, and these not only send signals back to the operator, but allow the receivers to be turned on and off. They are locked up in weatherproof cases, and are unattended except for regular maintenance.

An automatic muting or "squelch" circuit keeps the receivers quiet until someone in a car makes a call. Then all the receivers capable of hearing the car feed its signal back to the switch-board.

## RECEIVING

When this happens, signals from more than one receiver may be fed back to the exchange, but, normally, only the receiver which comes into operation first is connected to the line. Receivers which can pick up only a weak signal from the car do not come into operation at all. In other words, either a strong, useful signal is heard, or none at all. There is no point in charging people for a call when the car concerned is too far away to be properly heard. That is why the PMG issue each car with a copy of our page 3 map, so they may know the limits beyond which they may not be able to place a call.

The method by which only the wanted car is called by the exchange may take one of two forms, according to the type of equipment you have bought. The exchange is

The main transmitter at North Sydney with the exciter unit partly removed. Final power stage is immediately above with an output power rating of 250 watts.

so arranged that it will work either system.


One of these, which is almost universal in America, is operated by vibrating metal reeds in the receiver, which respond only to sounds of a certain pitch. When the car is to be called, these sounds are first of all sent out over the big transmitter. As only one car answers to any one combination of sounds, its bell is the only one which rings when that call is made. The telephone operator does all this automatically when she dials the car number at the exchange. The rest is up to the equipment itself, and the ingenuity of the men who designed it.

Because only one frequency or wavelength is at present available for all this, there is a limit to the number of cars which can be connected, for you cannot make your call while others are talking. The number of cars which can be accommodated will depend on how much they use their phones. When "engaged" periods become too frequent, the only remedy is to install a new "base" transmitter on a second frequency, which is the equivalent of laying extra wires to an overloaded phone system.

The PMG expects to have radiophones installed in the capital cities and Canberra, and some of these are already partly fitted. At the moment there are no plans for extending the service elsewhere, and because of the cost and emergency value of the idea, it is unlikely that extensions will be warranted. Those who have a use for the system, however, will undoubtedly find it an invaluable addition to the growing service provided by the department.

In passing, it is interesting to compare the charges of the Sydney

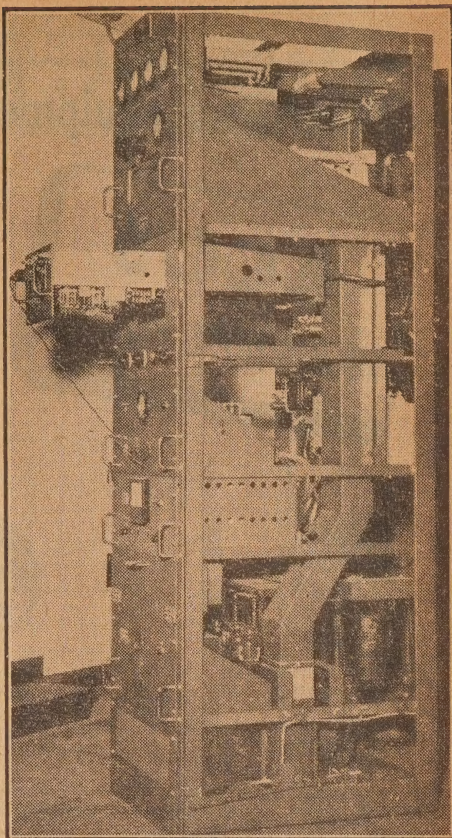
Excellent coverage of main transmitter to cars is ensured by the use of an aerial on top of the FM array at North Sydney—probably the highest point near the city.



mobile radiophone with those in America. In that country, the cost of a three-minute general service message is about three shillings, depending on the location of the land-line in the mobile service area. On long distance calls the regular person-to-person day rate applies with a minimum charge of about three and sixpence.

The equipment in the car may be supplied either by the user, or by the telephone company, remembering that in USA the telephones are operated by commercial concerns. If the company supplies the equipment, the rental is £5/10/- per month for two-way service, plus £8 installation charge—total £74 for the first year. There is also a minimum monthly message rate of 23 per month.

A point which may be stressed concerning the radiotelephone is that conversations may be picked up by anyone having a suitable receiver, and are therefore not private. Subscribers should therefore be very careful not to say anything which will not bear repeating by others, or which are of an embarrassingly private nature. It is in some comfort, however, to know that ordinary radio sets could not hear the conversations, and only confirmed stickybeaks would bother to provide themselves with special sets to listen in!

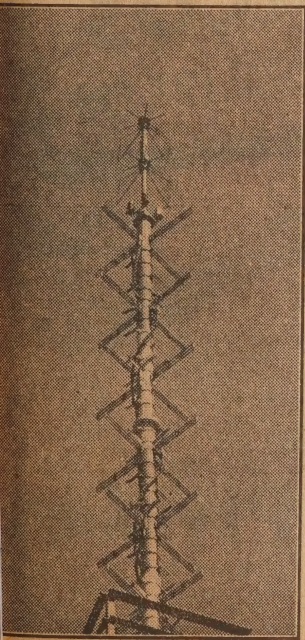



# Choose your equipment from this famous range!




**MIC. 3 DIAPHRAGM-ACTUATED** crystal microphone, specially designed for the reproduction of speech frequencies. With rising response from 1000 c/s, this microphone has exceptional sensitivity.  
Price: £1/8/2.



BACK



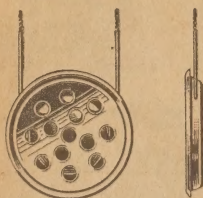**MIC. 19 SINTERCEL** fulfils the requirement for a flat insert with good sensitivity and a frequency response 40/8000 c/s. Unaffected by vibration, exceptionally robust construction.  
Price: £2/15/0.




**MIC. 18 MICROPHONE SPEECH INSERT** provides high acoustic qualities with minimum bulk. Where exceptional slimmess is required, this Insert is recommended.  
Price: £1/16/0.



**MIC. 14 STANDARD SPEECH MICROPHONE INSERT** with nickel-plate brass case which gives high corrosion resistance, mechanical strength and rigidity.  
Price: £1/8/2.



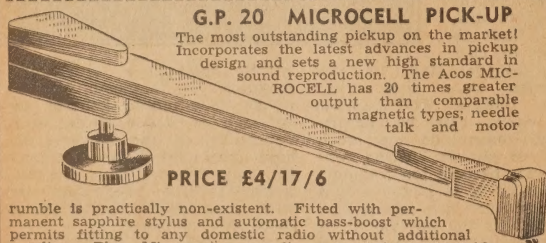**TYPE "A" MICROPHONE.** Specially designed for clear production of speech. Ideal for public address, office and factory call systems, amateur and mobile radio transmitters, etc.  
Price: £6/17/6.



## G.P. 20 MICROCELL PICK-UP

The most outstanding pickup on the market! Incorporates the latest advances in pickup design and sets a new high standard in sound reproduction. The Acos Microcell has 20 times greater output than comparable magnetic types; needle talk and motor

PRICE £4/17/6

rumble is practically non-existent. Fitted with permanent sapphire stylus and automatic bass-boost which permits fitting to any domestic radio without additional equalisers. Plays Microgroove or ordinary recordings. Available from all Radio Stores.

Price: £4/17/6


CARTRIDGE ONLY (G.P.19) .. .. . Price: £2/15/0
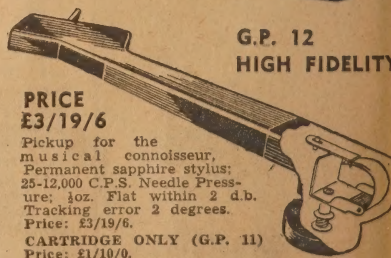
## G.P. 10 UNBREAKABLE PICK-UP



PRICE  
£2/8/6

Sturdy construction; ninety degree lift-back and exclusive needle pressure adjustment. Low Harmonic Distortion. Output 1.5 volt. Price £2/8/6.  
CARTRIDGE ONLY (G.P.9) Price, £1/2/1.



## G.P. 12 HIGH FIDELITY

PRICE  
£3/19/6

Pickup for the musical connoisseur, Permanent sapphire stylus; 25-12,000 C.P.S. Needle Pressure; 4oz. Flat within 2 d.b. Tracking error 2 degrees.  
Price: £3/19/6.  
CARTRIDGE ONLY (G.P. 11) Price: £1/10/0.

# AMPLION (A/sia) Pty. Ltd.

36-40 Parramatta Rd., Camperdown, Sydney. Phone LA2828.

SOLE AUSTRALIAN REPRESENTATIVES




# WILL A SAUCER REALLY FLY?

Flying Saucers!—we first heard of them more than a year ago speeding through Amercian skies at great speeds. Soon everyone was seeing them in all parts of the world. Some were reported as having actually crashed to the earth, complete with the remains of men from another planet! Many people now believe that there never were any saucers, Others are not so sure, and are convinced that optical illusions and auto-suggestion don't explain away the facts.

**A**LTHOUGH we have not seen evidence more concrete than some rather indistinct photographs of an alleged "saucer," there is no essential barrier to the construction of an aircraft which would look like a saucer, and fly at high speeds. It is doubtful whether saucers have actually been seen in all the places from which reports have been received, but it is perfectly possible that at least some accounts are authentic, and that the objects were in fact experimental models of a new aircraft revolutionary, by all conventional standards.

As a matter of fact, there are a number of Australian patents in existence for flying saucer aircraft, although it is not known whether any successful models have been built. How many others could be found elsewhere is not known, but there must be thousands.

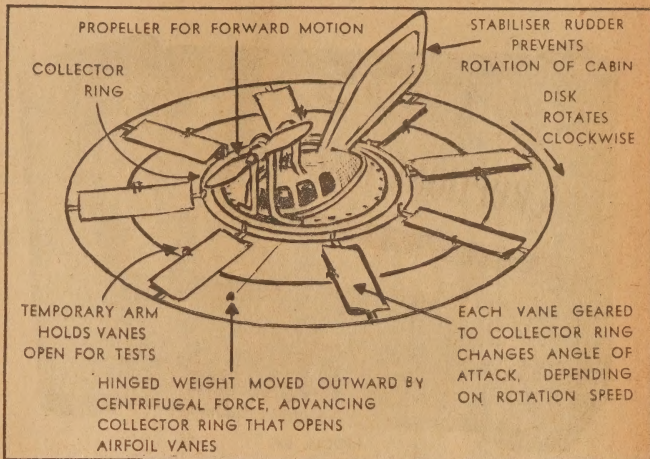One type which has provided successful model flights has been developed by Dr. E. W. Kay, of Glen-



Sketch of the 41 inch model saucer built by Dr. Kay, showing essential points of design.

dale, California, whose approach seems to be quite sound.

He has made a 41in model consisting of an aluminium-magnesium rim built round a central cabin. The rim is spun at 400 rpm by an electric motor through a ring gear. The motor also drives a conventional propeller for forward speed.

Lift is provided by vanes situated radially in the disc, which thus resembles a huge fan. These vanes are adjustable to give varying degrees of lift.


Although the model requires a short take-off run, Dr. Kay believes that a full-sized model, up to 50ft in diameter, could rise more or less vertically, and fly forward at 400

mph. The cabin, of course, would not rotate, and the whole job would be jet powered.

His model, anchored to an 18ft arm, flies round an anchored post at speeds up to 72 mph.

Enormous lift should be possible from a full-scale aircraft, and extreme flexibility likely by appropriate design of the vanes, and their variable angle of attack.

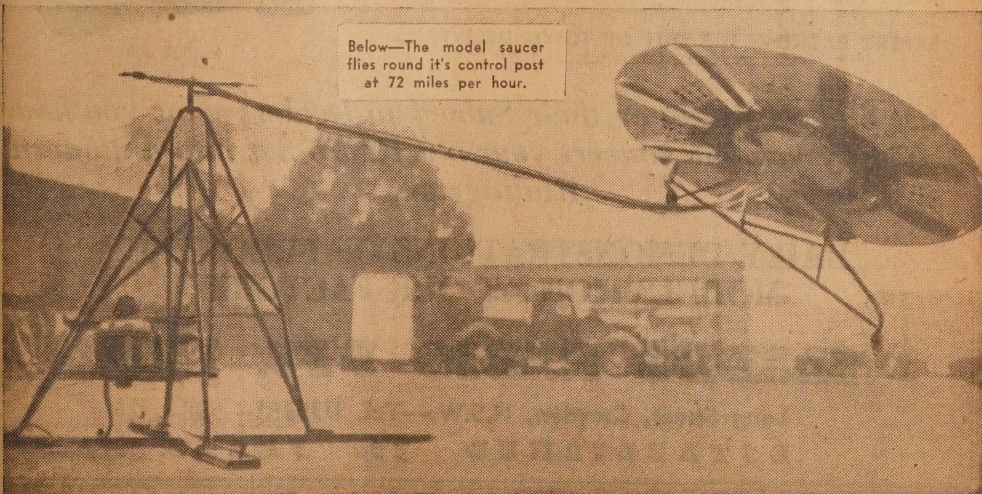The inventor hopes to build an 18ft flying model which would carry a man, and is confident that his idea, which combines the design principles of both the aeroplane and the helicopter, will provide the answer to the search for a highly manoeuvrable, fast aircraft.



Below—The model saucer flies round it's control post at 72 miles per hour.



# Radiogram & Cocktail Cabinets

## *Finest Selection in Australia*



MODEL 508

SLADE'S RADIO  
PTY. LTD.

makes available to  
Radio Dealers and Home  
Constructors a full range of  
Console, Combinette and  
Radiogram Cabinets.

Made from best quality Maple and Italian Walnut Veneers with a brilliant piano finish.


MODEL 508 is suitable for all types of Record Changers.

MODEL 509 is suitable for single motor. Dial fits on front of cabinet, lid being lifted only for record playing.

MODEL 509A is suitable for all types of record changers, same appearance as 509.

MODEL 510 is a Combinette-type cabinet, large enough to take a 5-valve, dual wave set with single motor.

EXPERT PACKING FOR OUT OF TOWN DELIVERIES

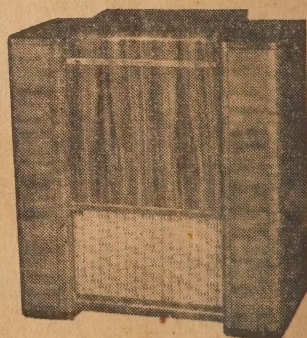

MODEL 509

*Let Slade's Radio or their Suburban Dealers show you how cheaply you can convert your old Radio Set into a modern Radiogram.*

**DAILY DEMONSTRATIONS OF FREQUENCY  
MODULATION AT OUR FACTORY**

**SLADE'S RADIO PTY. LTD.**

Lang Street, Croydon, N.S.W.—Tel. UJ5381—5382.

**ESTABLISHED 30 YEARS.**



# BRITAIN'S HELICOPTER AIR BUSES

British helicopter experts are making plans for inter-city air buses in five years, according to our London correspondent. Their activity foreshadows inevitable development of short haul air traffic which can cope with restricted landing spaces.

THE world's first regular passenger service by helicopter began recently between Liverpool and Cardiff—a major step forward in plans for air-buses travelling between city centres.

The service is conducted by British European Airways.

The first day's flights were booked out, the rush being due to the novelty, needless to say. But helicopter passenger services will not be a novelty long, according to BEA experts.

Big intercity air buses, they believe, may be the regular thing within five years.

Mr. Peter Masfield, chief executive of BEA, has in mind multi-engine helicopters carrying about 30 passengers each. The Westland-Sikorsky S51 helicopters to be used on the Liverpool-Cardiff service carry only three.

But they will be "flying guineas" which will provide a valuable opportunity for working out traffic-handling problems and operational technique which the helicopter mail service—in use for some time—has not supplied.

## PASSENGER SERVICES

And at the same time they will be getting people used to the idea of helicopter travel.

At first sight it would seem that the proposed use of an airfield more than six miles out of the city at Liverpool (it is about two at Cardiff) almost defeats the helicopters' advantages.

But BEA are unwilling to bring the single-engined helicopter into built-up areas even if rotor stations (the name they are giving here to helicopter landing grounds) were available.

If the helicopter proves popular with passengers, however, development of helicopter services on plans ready well in hand will go ahead leaps and bounds.

The mail service has already satisfied all safety requirements, and showed that the helicopter can do a job—and in nearly all weathers.

After experiments in the west of England, which eventually took the form of running a dummy mail service early in 1948, a regular daylight mail run by helicopter was begun in June of that year. It was a 215-miles circuit from Peter-



The Westland-Sikorsky S51 Helicopter.

borough around the Norfolk coast, covering the Broads, or inland waterways, of that county—an area in which the helicopter showed up to particular advantage.

The winter brought that service to a close until further experimental work was carried out and special equipment evolved for night and blind flying to schedule.

Last year a further test with dummy mail, carried at night this time, satisfied the Post Office, and a regular mail service at night was taken up by the helicopter between Peterborough and Norwich last October. It has gone through every night so far—and where the helicopters have been delayed it has

generally been by weather which has upset land services too.

The new Liverpool-Cardiff passenger service is regarded as another stage in this series of experiments with helicopters. It will be operated twice a day each way, taking about 1½ hours to cover the 140 miles distance between the two cities.

Wing-Commander R. Brie is in charge of BEA's helicopter experimental unit and he has already picked four pilots to start off the Liverpool-Cardiff service.

What of the future? Several firms are making helicopters and planning new designs—including a super 36-seater in one case. But the industry cannot tool up for big production unless it can anticipate an equal demand. Meanwhile operational regulations for helicopter services—which will now have to deal with the problem of city landing stations—are under review.

With the possibility of intercity travel in these air buses of the future coming nearer much may depend on how the first regular helicopter passenger service "catches on."

by Ken  
Murchison





# The INDUSTRIES STANDARD


**MADE IN AUSTRALIA**  
**BACKED BY WORLD-WIDE TECHNICAL  
ORGANISATIONS**



**INSULATED** *Metallized*

## TYPE BT RESISTORS

**THE WORLD'S STANDARD RESISTORS**

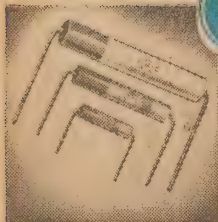

Their ingenious construction, with the time-tried *Metallized* filament, insures lower operating temperatures with proportionately high wattage dissipation in a small, sturdy lightweight fully insulated unit with an **EXCEPTIONALLY LOW NOISE LEVEL**.

Guaranteed accuracy of plus-minus 10%. Proof against moisture—even salt water immersion. 1000 volts insulation to ground.

Available in all standard values, Types BT1, BT1 and BT2, they suit the exacting requirements of the local market.



*Metallized*

## VOLUME CONTROLS

**PERMANENTLY QUIET**



TYPE CS with the time-tested *Metallized* element.

The old bugbear of noise is **PERMANENTLY** eliminated by these IRC EXCLUSIVE features:—

● **SILENT SPIRAL CONNECTOR** which provides continuous electrical connection between centre terminal and volume adjustment arm, eliminating metal to metal contact—the common cause of noise.

● **5-FINGER KNEE ACTION CONTACTS** that ride over the resistance element independently of each other.

Thus, in IRC Controls you have **DOUBLE** assurance of smooth action that is quiet—and **STAYS** quiet. There's **NO SLIDE, NO FRICTION, NO NOISE**. Size—they are only 1½" diameter. Brass spindles. No die casting is used in manufacture, therefore there is no distortion or creeping with the passing of time. Insulated shaft, 1-watt rating. D.P.S.T. or S.P.S.T. switches for mains of low voltage operation.

SOLE AGENTS FOR AUSTRALIA:

**Wm. J. McLELLAN & CO. PTY. LTD.**

Bradbury House, 55 York Street, Sydney Phone: BX 2508



# TWENTY YEARS FROM NOW

Up to the moment the only tangible result of the great scientific achievement of atomic fission has been entirely destructive. "Splitting the atom" has resulted in the deaths of thousands, in scaring hundreds of millions and in making the nations of the world suspicious of each other—not very creditable results for one of the greatest scientific triumphs of all time.

BUT I think that when we look back in 20 years time we may see the use of the atom-bomb just as an incident in the history of atomic energy. Without being cynical, we may take the view that the explosion at Hiroshima was like an explosion in a high-explosive works or a child cutting itself when learning to use a knife.

For in 20 years time I believe that atomic energy will be "harnessed" and supplying us with millions of horsepower of energy a year. I do not rule out the possibility of it being used as a military explosive, but fully developed atomic energy could bring about an industrial revolution hardly less important than the harnessing of steam power.

## RESEARCH WORK

Britain is spending large sums simply on preliminary steps in research on atomic fission for "peaceful" purposes, and other nations are also spending vast sums. In 20 years we shall have the fruit of this research. In the House of Commons, Ministers have been at some pains to damp down the idea that atomic power could lead to the Utopia of a four-hour working day, but the reasons for this are probably psychological.

Of course, there are immense technical difficulties—that is why we are spending millions. But if the result of overcoming these difficulties is not to be a supply of abundant, cheap power, why trouble to tackle them?

The principle by which it is assumed that atomic energy will be harnessed is that atomic piles will be made to run so that they heat water, which in turn will drive gas or steam turbines. Research may show that there are more direct methods by which the energy can be harnessed, just as it is likely to reveal methods of utilising the atomic energy of elements less expensive than uranium, which has hitherto been used.

## DISADVANTAGES

In the light of our present knowledge, the disadvantages of atomic power are: The very high cost of the plant and "fuel"; the fact that in an atomic pile must be large; and, thirdly, the poisonous gases and by-products of atomic fission which have to be disposed of.

The last two disadvantages are taken to mean that it will never be possible to utilise atomic power for transport—the energy generator would be too large except, perhaps,

(Continued from last month)

for a ship, and the impossibility of disposing of the dangerous by-products would make it impossible to use atomic power in street vehicles or even trains.

But it would be wrong to assume that this disadvantage will always exist. Just as we may find cheaper atomic "fuel," so we may find methods of utilising atomic energy indirectly, turning it into a synthetic fuel that could be used by comparatively small power units and with no danger from by-products. You will not, in 20 years, stop at a garage and fill up your car with uranium—radioactive materials are too dangerous to use in densely populated places even when they are in "fool-proof" containers. But you may fill up with a fuel whose potential energy has been derived from an atomic power generator.

## FIRST USE

The first practical use of controlled atomic power, paradoxical as this may sound, is likely to be in countries which are not greatly industrialised. With our present methods atomic power is rather more expensive than power derived from coal. Research will undoubtedly bring down the cost so that atomic power becomes much cheaper than power from coal.

But the fundamental fact remains that, in this generation of electricity and the manufacture of goods, the

by Professor  
A. M. Low

cost of power is only one item. Fuel accounts only for about 40 per cent of the cost of our electricity—as against 60 per cent for distribution and administration. In many manufactures the expenditure on fuel represents only about 10 per cent of the total cost.

It will be seen, therefore, that even if we could get atomic power for nothing, it would not make such an enormous difference. The importance of atomic energy, in my view, lies in the fact that we can look forward to obtaining it in quantities inconceivable for coal or oil derived

power, and that the fuel is comparatively light and easily transported.

This means that we shall undertake gigantic engineering feats that would be impossible with our present sources of power, and that we shall be able to obtain power cheaply in places remote from present industrial centres.

For instance, with atomic power it is possible to consider great irrigation pumping plants in the heart of deserts, where the cost of transporting fuel would at the moment make the use of power pumps quite uneconomic. In the arid regions of Australia and Africa there is water if the boring is deep. Atomic power offers the possibility of getting it.

## GIGANTIC ENGINEERING

We shall be able to contemplate gigantic engineering feats which may change the climate and even the weather. Twenty years ago the idea of removing—or making—mountains in order to change the rainfall seemed ridiculous. Using the power of atomic fission it becomes a practical possibility. We can contemplate melting Polar ice or warming the soil over hundreds of square miles.

The Americans have already talked, even if only half seriously, of diverting the Gulf Stream so that it gave them more warmth. That may become a real possibility. It is in such ways, perhaps, rather than in replacing coal and oil as fuels, that atomic power will be used.

Atomic power may prove to be the key to inter-planetary flight of which I have written in my first article. A few tons of atomic "fuel" will provide more energy than thousands of tons of oil. We may even discover methods of renewing the fuel by making use of the atomic fragments—cosmic rays—which we know are abundant in space.


## DANGER

The difficulties of the dangerous radiation will, I believe, be overcome more quickly than anticipated, and the present tremendous concrete walls may seem as clumsy as mediaeval armor in 20 years. It is worth noting that in the short history of atomic energy the experts have constantly had to revise their ideas of the future.

After Hiroshima they were at pains to say we could expect no peaceful developments for 20 years. Then they began to talk about 10 years. Now they admit that the first "pilot" commercial atomic piles are ready

(Continued on Page 63)



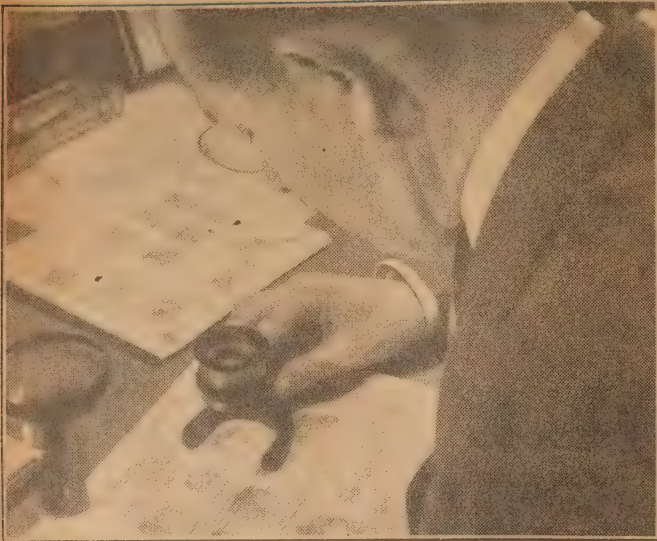

Careful study of prints reveals essential characteristics which go to the building up of individual prints.

the infallibility of the fingerprint system is in connection with the payment of the Veterans of World War I bonus.

Over 3 million ex-servicemen of the USA were obliged to impress the fingerprint from the finger of one hand on their application form.

It was this print which furnished the evidence that the person receiving the payment was identical with the person who served in the forces over 20 years previously and whose record was in the files of the Army.

### IDENTIFICATION

These finger prints also have been the means of identifying the bodies of soldiers, sailors and airmen who have been found dead in civilian clothes.

The litigation which has recently taken place in Australia regarding the alleged mixing of two babies at a maternity hospital may have been avoided had that hospital adopted a method of palm or foot printing

# YOUR PRINTS ARE PERMANENT

There is something sinister in the phrase "He had his fingerprints taken", yet today the use of fingerprints goes far beyond the tracking down of criminals. It is true that most of the publicity regarding fingerprinting has been devoted to its use in criminal investigation and many fantastic stories have been woven around this branch of science.

PERHAPS this is due to the fact that there is nothing sensational in a person stamping his finger prints on a legal document or as a means of identification when he deposits his money (if any) in a bank.

There is an exciting lure for the impressionable in a detective carefully blowing powder on the glass supposed to have been used by the poisoner, in order to bring out the prints. There is breathless sensation in the action of the great sleuth who, regardless of the scorn of the regular police force, manages to find the convicting print on the rough edge of a two shilling piece.

### DACTYLOGRAPHY

But what is exciting about a man stamping his finger on a cheque or a mortgage? Nothing to make a song about. Yet this practice is increasing from day to day.

The science of Dactylography as the science under discussion is called has great value in many places where identification of individuals is called for.

Some of these are the identification of dead bodies, registration of aliens, passports, circular letters of credit, and the identification of infants particularly the newly born

where the mixing of babies can cause much trouble and litigation.


Banking functions and legal documents have already been mentioned. The identification of lost children and people suffering from loss of memory is aided by fingerprinting.

The defence forces of the United States have millions of fingerprints of Service men and women in their files.

One of the instances often cited in defence of



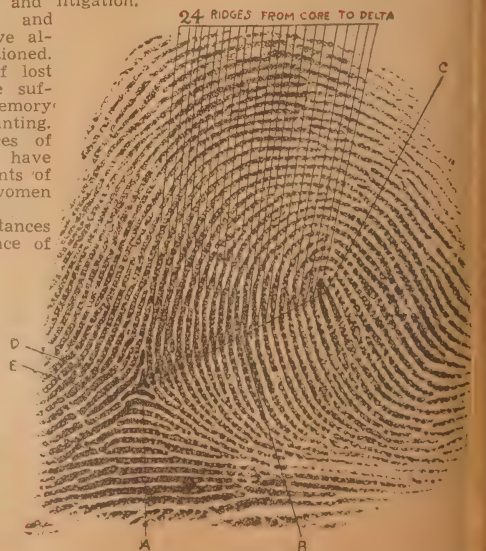This is an Ulnar outer loop having twenty four ridges on the line of count. A—Lower type line. B—Line of count, the shortest possible line from Core to Delta. C—Core. D—Delta. E —Upper type line.





The use of finger prints for identification seems to have been used first by the Chinese. These people used it mainly for legal work.

In early England the thumb print was used by persons who could not write their signature.

Even today a thumbprint on the end of a letter would be of more use than some of the signatures one strikes now and again. It would be a great help to a business firm if some of their correspondents sent their fingerprint together with their alleged signature for filing away so that further letters from the same person could be identified.

It is now a firmly fixed belief that it is absolutely impossible for any two persons' fingerprints to be alike. It is also accepted that a person's fingerprints do not change during the lifetime of the individual.

The skin of the human body consists of two main layers called the dermis or true skin and the epidermis or surface layer.

## THE DERMIS

The Dermis is the under layer of skin and has nothing much to do with our subject. The Epidermis however, has peculiar characteristics and with it we will have to deal.

The skin, aside from being a protective covering for the flesh, acts as a temperature regulator and vehicle for the expulsion of waste products from the body.

If a piece of skin is examined under the microscope it will be found to be permeated with large numbers of very fine holes or pores. These are really outlets from tiny glands situated in the deeper layers. These glands are of two kinds—"sebaceous" and "sweat" glands which secrete an oily substance, and sweat (or perspiration) respectively.

A peculiar thing about sebaceous glands is that they are found over the entire body except on the palms of the hands or the soles of the feet.

Sweat glands are found over every part of the body.

## HANDS AND FEET

The palms of the hands are called the "thenar" surface and the soles of the feet are called the "planter" surfaces.

On these surfaces there is a very peculiar formation of the skin. It is marked with a mass of very fine ridges showing a definite formation or pattern. These ridges are called "papillary" ridges and form the basis of finger print science.

The papillary ridges are formed



A.



B.



C.



D.



E.



F.

A—A plain arch. B—A tented arch. C—An exceptional arch. D—A radial loop. E—An ulnar loop. F—A central pocket loop.



This pattern is known as a whorl.

by small elevations on the under or true skin and it is along these ridges that the pores are arranged in regular rows along the crests of the ridges.

On no other part of the body are these ridges found.

The patterns formed by the papillary ridges remain unchanged throughout the entire life of the individual except when destroyed by accident, and they remain unchanged in every minute detail except that the pattern grows larger as the individual grows. This is natural and reminds one of the story of the man whose wife had

previously been the tattooed lady in a circus. She now has a battleship tattooed on her chest. When he first met her it was only a rowing boat. It is remarkable how far the human skin will stretch without bursting. But this has nothing to do with our subject so let us get on.

These papillary ridges are so unchanging that they persist even after death until the body has reached a very advanced state of decomposition.

When the outside layer of skin is injured it will heal and show the identical ridges as before, unless the under layer of skin has been injured, thus destroying the papillae which form the ridges on the epidermis. A scar will be formed under such conditions and the ridges do not form on scar tissue.

## EFFECT OF INJURY

Sometimes a severe injury will cause distortion of the tissue surrounding the scar, thus rendering comparison of present with previous fingerprints a difficult matter. Needless to say many criminals have resorted to self injury in order to conceal their fingerprints. For this reason prints of criminals are now taken of the entire two hands and sometimes of the soles of the feet. A man would have a job to injure both hands and feet.

The science of dactylography is based on the formation of these papillary ridges. These, to repeat, form certain patterns which have been classified over the years. They fall into well defined groups owing to their geometrical formations.

The patterns are divided into simple patterns and composite patterns. There are certain cardinal points or determining points on a



Left—The core, indicated by the dot at the apex of the inside ridge of the loop. Centre—Type lines, indicated by the blackened curves at right centre. Right—The delta.




# IF IT'S ANYTHING TO DO WITH RADIO

— *It's W.F. for the Best Products — the Best Service* —


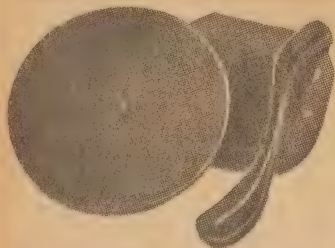
## NEW PHONOVOX MANTEL CABINET

Polished wooden front with enamelled metal body 12" long.  
7½" high, 7" deep --- 63/6  
Blank chassis to suit --- 8/8




## NEW PLESSEY RECORD PLAYER

With Decca high-fidelity pickup.  
Automatically plays 12" or 10" records on selection --- £9/16/3




## ALPHA ROTARY AND TOGGLE SWITCHES

Type R	1 way	S.P. ¾" Neck ..	3/10
Type A	2 way	S.P. ¾" Neck ..	4/4
Type B	2 way	S.P. ¾" Neck ..	6/4
Type C	2 way	Semi-Rotary ..	6/4
Type D	D.P.S.T.	¾" Neck ..	6/4
Type E	D.P.S.T.	¾" Neck ..	8/4
Type F	D.P.S.T.	¾" Neck ..	7/11
Type G	D.P.D.T.	Semi-Rotary ..	9/6
Type H	D.P.S.T.	1" Neck ..	8/5
Type J	D.P.D.T.	1" Neck ..	9/6
Type L	Door Switch	¾" Neck ..	8/7
Type S	Door Switch	¾" Neck ..	4/9

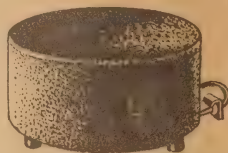
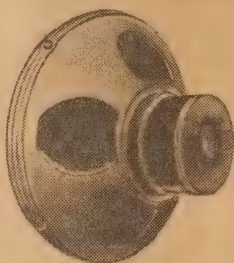
## 'MYTT' DISPLAY TURNTABLES

8" carries 112lbs -- £11/5/-  
12" carries 175lbs . £15/8/-



## GOODMANS HIGH FIDELITY SPEAKERS

New Models.

Axiom 150 15 watt £14/18/-  
Axiom 22 (illust.) 20 watt £25/15/-

## SWITCH POTENTIOMETERS

½ meg. double pole

I.R.C.	"	10/6
Plessey	"	9/3
Egan	"	8/4
Weestat	"	9/-

## SPECIAL

Leatherette covered mantel and personal portable cabinets.

Reduced for this month **10'- ea.** only to



## FERROCART CRYSTAL SETS

Complete with Brown's English Headphones. In Pink, Green, Yellow Plastic cabinets 84/-



## RECORDEX

The new improved Gramo record rack.

- Holds 25 10in. or 12in. records.
- Engraved easy to read index strip.
- Complete with index card and gummed identification numbers for the records .. 25/-



## AMPHENOL MICROPHONE CONNECTORS

Full stocks of all types now available 1, 2, 3 and 4 pin in chassis mounting and for cord connection.

Brown's type X Headphones --- 37/6 pr.  
British Cotton covered Headphone cords --- 5/9 ea.

# WARBURTON FRANKI (MELB.) LTD.

380 ROURKE ST., MELBOURNE, C1. . . PHONE: MU 6355 (8 LINES)

Trade also supplied

Open Saturday mornings



ingerprint by means of which the investigator determines the exact pattern he is studying. The ridges between these cardinal points are then counted, classified and filed.

As mentioned, previously fingerprints consist of a series of ridges. These are produced by first coating the fingers with printers ink and pressing or rolling the fingers on a sheet of paper. The prints show a series of black and white lines.

## CARDINAL POINTS.

The cardinal points are of the most importance in the classification of finger prints and those whose business it is to study prints must be able to recognise them instantly.

These cardinal points are the Core and the Delta.

The Core is shown in the accompanying figure. It is the heart of a simple pattern and is situated inside the point where the inside ridge curves back upon itself.

The Delta is shown in the next diagram. It is called a delta because of its triangular structure and occurs at the point where the ridges in their sweep across the finger, separate and enclose the main pattern.

There is another cardinal point which may be of great significance in classifying complex patterns. This is the "type line" and consists of parallel lines or curves which flow upward and inward to a point where they diverge and form the delta. These are shown in another diagram.

Finger prints are divided into patterns. These consist of arches, loops, whorls and accidentals.

There are also subdivided into categories as follows:

## ARCHES

**PLAIN ARCH.** This is shown in the diagram. It consists of ridges which flow from one side of the hand to another, perhaps rising slightly in the centre.

**TENTED ARCH.** Here the ridges flow from one side to the other, but rise abruptly in the centre giving a tent-like formation.

**EXCEPTIONAL ARCH.** This is similar to the plain arch except that it has one ridge which recurves. This is located at the centre.

## LOOPS

**RADIAL LOOP.** A loop where the ridges turn back and slope downward toward the little finger.

**ULNAR LOOP.** A loop where the ridges turn back and slope downward toward the thumb.

**WHORLS.** A pattern where the ridges form complete circles which give the pattern the appearance of a whirlpool.

**CENTRAL POCKET LOOP.** This is similar to a whorl except that one or two lines or ridges break and turn back at a point in the diameter of the whorl.

**TWINED LOOPS.** Two loops side by side in which the ridges curve

in opposite directions.

**LATERAL POCKET LOOP.** Two loops side by side but with the ridges turning back and coming out on the same side.

**ACCIDENTALS.** Irregular patterns which cannot be classified with any of the others. They are really two or more types in a single print.

All these classifications of finger prints are illustrated in the various



Left—A twin loop. Centre—A lateral pocket loop. Right—An accidental.

diagrams which make the matter quite clear.

Among all these one finds fingerprints whose types correspond, but whose variations are so distinct as to make them recognisable to the expert.

Types of fingerprints are subdivided by ridge counting or ridge tracing. The former method is used when examining a loop type of print while the latter is used in examining whorls.

The method of counting is fairly simple. An imaginary line is drawn from the core of a loop to the delta, then, by means of a fine pointer the number of ridges between these two cardinal points are counted.

## GROUPINGS

It has been found that the number of lines on the fingers fall into well defined groups. There are what are called balance lines which are given numbers.

For instance the balance line on index fingers is the ninth line. This means that there are just as many fingers which have nine lines from the core to the delta as there are fingers which exceed nine.

The balance line on middle fingers is the tenth line. This leads to a further classification of loops into two classes. The loop on an index finger is called an inner loop when the number of ridges between the core and delta count nine or less. When the number of ridges count ten or more it is called an outer loop.

When it is a middle finger loop it is an inner loop when the ridges count ten or less, and an outer loop when the count reveals eleven or more ridges.

Whorls are similarly subdivided into inner and outer whorls. These are determined from the number of ridges between the two deltas.

Out of all the whorls, loops, arches, deltas and accidentals the

finger print expert is able to classify the print, give it a formula and file it away for future reference when needed.

It will be seen that the classification of a finger print is a most important item. By means of this classification which falls within ten general types as outlined above the print can be subsequently identified by further subdivision by ridge counting and tracing.

The grouping of sets of prints so that it may be identified out of thousands and sometimes millions of prints is a complex matter, but today it is so highly organised that no person who commits a felony and whose fingerprints have been previously recorded in the files of the Police Dept. can fail to be identified by a print he has inadvertently left behind at the scene of his crime.

To attempt to describe the methods by which fingerprints are grouped and filed is quite beyond the scope of this article.

It is, however, so interesting that those whose interest may have been aroused by the discussion would do well to study the method through a recognised text book.

The finger print system is so expanding in its usefulness that it holds something as a career for those who make themselves expert at it.

For those who wish to take their own fingerprints to compare with the illustrations given, the method used is as follows.

## MATERIALS

The materials required are a small tube of printers black ink, a small rubber roller, a sheet of glass and some white smooth paper. Place a small quantity of ink on the glass, roll out well with the roller to get a very thin film of ink. Place one edge of the finger on the glass and roll the finger over to the other edge, lightly pressing while doing so.

Now place the finger on edge on the white paper (which should be placed on a hard surface) and roll over to the other edge. This will leave a good print. The finger should be well cleaned before applying the ink. The ink can be washed off afterwards with petrol or kerosene.

Finger print examination is an interesting hobby and can provide endless amusement.




MANUFACTURERS OF  
COMMERCIAL RADIO  
RECEIVERS FOR 12  
YEARS

# CLASSIC RADIO

FOR QUALITY  
WITH  
ECONOMY
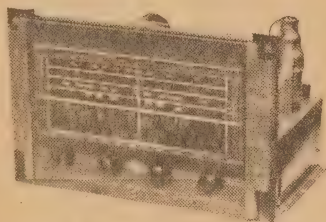
## Complete 8 Valve Radiogram-Unit

- 8 VALVE WORLD-RANGE RADIOGRAM-UNIT
- MATCHED-DUAL SPEAKERS—12" and 8"
- COLLARO ELECTRIC MOTOR (WITH SPRING MOUNTING AND AUTOMATIC-STOP)
- HIGH-FIDELITY COLLARO CRYSTAL PICK-UP
- "GOLDRING" SAPPHIRE JEWEL POINT NEEDLE



**£29**  
FREIGHT EXTRA



### COMPARE THESE FEATURES

Eight valve world range chassis with push-pull output. Uses new Philips ECH33 converter valve for better long distance reception. High gain audio with inverse feed back and tone control gives you the best reproduction from your favorite recordings. Radio-gramo switch combined with short wave switch. A.C. switch incorporated with tone control. Large calibrated edge lit dial with main stations in each State in prominent type, with counterweight drive. Provision for F.M. or television tuner. Permatuned iron cored coils and intermediates.

Large Variety of Combination  
Cabinets Available from £13/10/-

### 6 VALVE RADIOGRAM UNIT

SPECIFICATIONS AS EIGHT VALVE UNIT, BUT WITH SINGLE  
6V6GT OUTPUT VALVE AND SINGLE 12" SPEAKER

**£23**  
FREIGHT EXTRA

# CLASSIC RADIO

245 PARRAMATTA RD.  
HABERFIELD  
PHONE UA2145





# Technical Review

## FURTHER DETAILS OF THE "VIDICON" CAMERA TUBE

The miniature RCA "Vidicon" tube featured last month, uses a very old but a basically different principle from other current types. The story is told by three RCA workers in a recent issue of "Electronics."

**M**OST camera tubes, to date, operate on the principle of photo-emission. In other words, the light rays are focused on a sensitized surface which emits electrons according to the strength of the impinging light. The electrons are utilized in a variety of ways, according to the tube design, but ultimately operate on the output circuit of the tube.

An alternative approach, which was appreciated very early in the art, is represented by photo-conductivity, by which the incident light is made to vary the conducting qualities of the target.

### MORE SENSITIVE

The significant point about this second principle is that it offers vast increase in photo-sensitivity, representing the difference between about 50 microamps per lumen for photo-emission to tens of thousands of microamps for photo-conductivity.

However, while many photo-conducting materials are known, there are practical difficulties in their application and, after considerable work on the principle in the middle 30's, it was again dropped in favor of photo-emission.

Intensive work on photo-emitters during the war, for infra-red detectors, threw much new light on the subject and encouraged RCA engineers to try again. It was realized that, if the principle could be applied successfully in practice, the higher sensitivity would obviate the need for multiplier stages and much of the complication surrounding the present Image Orthicon.

### NO POSSIBILITIES

Alternatively, it would be possible to obtain, with suitable amplification, a degree of sensitivity far exceeding that of the human eye and of the present Image Orthicon, complete with multipliers.

The word "Vidicon" has been coined to distinguish the general type of tube in the RCA range. The 1" model, featured last month, is largely

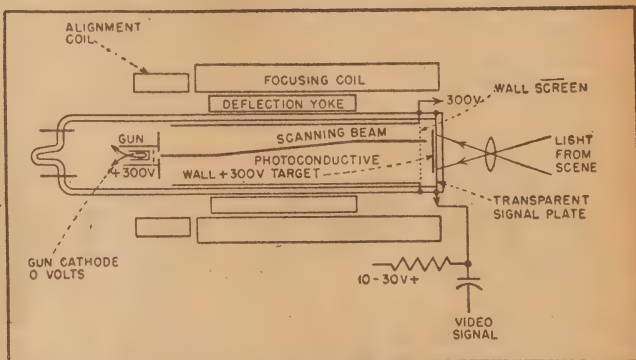


Figure 1. Cross-sectional diagram of an experimental Vidicon photo-conductive television camera pickup tube.

an experimental release, but it shows interesting possibilities.

The circuitry surrounding the tube is more simple than for an Image Orthicon, while the control requirements are also less critical. It is, therefore, envisaged as an excellent tube for unattended industrial applications.

The one-inch Vidicon, with a target sensitivity of 300 uA. per lumen will transmit a noise-free picture using an f/2 lens and a level of light not exceeding that common in factories and laboratories.

Compared with an Image Orthicon tube, the Vidicon has a poorer signal-to-noise ratio at low light levels, it is much the same at medium levels and shows a better signal-to-noise ratio with high intensity of illumination. However, it tends to lose contrast under the latter conditions as compared with the Image Orthicon.

RCA yet has to build sufficient tubes to demonstrate whether the characteristics can be reproduced under commercial production conditions, while problems associated with temperature and tube life also await answer.

### OPERATION

As indicated by figure 1, the operating principle is very simple. A magnetically controlled scanning beam passes first through a "wall screen" and then impinges on a transparent photo-conducting signal plate.

The side remote from the beam has a small positive potential applied and, with the light scene permanently focused on it, storage effects allow a volt or so to "leak" to the inner surface according to incident light values. This is discharged by the flying beam, providing the signal current from the signal plate.

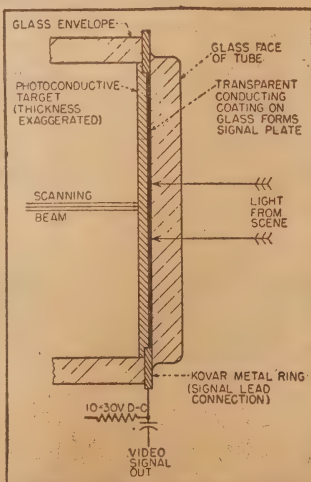



Figure 2. Detail of the target construction in the experimental photoconductive camera tube.



# Homecrafts

PTY. LTD.

## LARGEST STOCKS GREATEST BARGAINS!

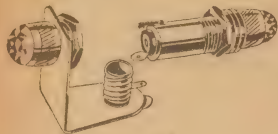

**WARNING & PILOT LIGHT ASSEMBLIES.**

Miniature type 1/8



**CAPITOL PORTABLE ELECTRIC GRAMO UNIT.** English Collaro Motor high fidelity pickup and automatic stops, as illustrated. Only 12 Gns. 52/- deposit, 3/6d weekly.

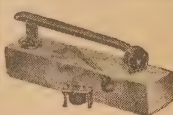
**GOOD NEWS FOR RECORDING ENTHUSIASTS.**




The new Capitol De Luxe Traversing Gear. Overhead traversing gear for recording from 8 to 16 inch discs. Precision engineered. As illustrated. Price, 11 Gns.



**BATTERY CHARGER KIT.** Kit of parts to build a 6 volt 4 amp. Battery Charger. Kit includes an English Selenium Rectifier, transformer, black crackle finish metal case, 2 terminals, hook-up wire and circuit blue print instruction. 12 volt 5/- extra. Price, as illustrated, £4.10.0.



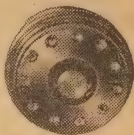**HIGH FIDELITY PICKUP BARGAIN.** English Shefi High Fidelity Moving Coil Pickup Complete with matching transformer. Reduced from £4.19.0 to only 29/11d. As illustrated.



**5 BPI CATHODE RAY TUBE SOCKETS.** Moulded 11 Pin sockets with Silver Plated Contacts. As illustrated, 9/6d.




**MECHANOID CUTTING HEAD.** A low priced Cutting Head (500 ohms impedance) with outstanding performance. Suitable for use with Capitol Traversing Gear. Price, as illustrated, £5.10.0.


**B.R.S. RECORDING BLANKS.** High Grade Recording Discs with highest quality aluminum base. Available in three sizes, as illustrated. 8 inch, 5/2d.; 10 inch, 6/6d., and 12 inch, 8/6d.; 16 inch, 13/6d.



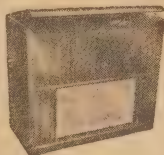
**FOR PROLONGING THE LIFE OF RECORDINGS.** Complete with instructions for application. 4 oz. bottles, 2/9d. 8 oz. bottles, 5/6d.



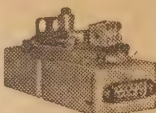**RADIO GRAM CABINETS.** Beautiful walnut piano finish, standard model, £13.19.6. Model with deep well for record changer, £14.7.0. Also available in blonde finish. Standard model £16.9.6. Model with deep well for record changer, £18.17.0. Country and Interstate clients add 15/- packing charge.



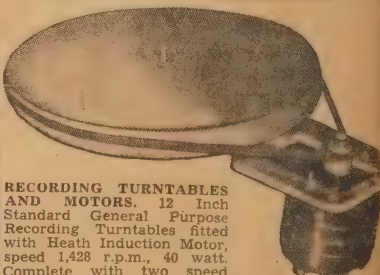**KAR SET.** Radio and Hobbies Car Radio Kit as described in May issue of Radio and Hobbies. Homecrafts offer this kit complete to the last nut and bolt. Price, as illustrated, 18 Gns. including Sales Tax.



**RECORDING TURNTABLES AND MOTORS.** 12 Inch Standard General Purpose Recording Turntables fitted with Heath Induction Motor, speed 1,428 r.p.m., 40 watt. Complete with two speed pulley, direct driving turntable. Price, 16 Gns. complete. Suitable for use with Capitol Traversing Gear.



**TRIPLE SPEED GRAMO MOTORS.** Imported American synchronous type T.S. Electric Motors; 33-1/3, 45 and 78 r.p.m. Complete with Turntable as illustrated. £12.19.6.



**PALEC VIBRATOR POWER SUPPLY.** A.V. vibrator Power Supply from 6 volt DC to 240 A.C.




**CHASSIS HOLE CUTTERS.** Adjustable Chassis Holecutters. Cuts holes from 1" to 3 3/4". Price, 16/7d.

**COUNTRY AND INTERSTATE CLIENTS PLEASE ADD FREIGHT OR POSTAGE.**



**BALRADIO INVERTER**  
£22.13.6.

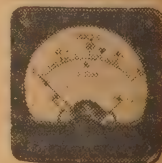

**SUPER METER BARGAIN.** English Moving Coil Meters. 2" scale, 200 ohms per volt. Two models available, 0-20, 0-40 volt. Price, as illustrated, only 19/11d.

**290 LONSDALE ST., MELBOURNE. CENT. 4311**



# RECORDS CUT WITH HOT STYLUS TIP

A new technique, evolved in the US by Columbia Records Inc., employs a hot stylus to engrave the sound track on lacquer-type master discs. A wide frequency range is obtained, together with low noise level, results comparing favorably with the best "wax" technique.

**WRITING** in Audio Engineering the author, W. S. Bachman, points out that lacquer-coated recording blanks are used very widely because of their obvious convenience. They can be handled and played back directly, if necessary, whereas wax-coated masters must be fully processed before any use can be made of the recording.

However, the problems of recording on lacquer type surfaces are quite different from those associated with wax masters.

It was appreciated immediately that styli intended for wax masters have a granular and noisy cut on a lacquer surface and special styli have had to be developed. In general, these are distinguished by the provision of burnishing facets along the cutting edge, as illustrated. With such styli, extremely quiet cuts are possible.

However, against this advantage, it was noted that the discs showed marked loss of high frequency res-

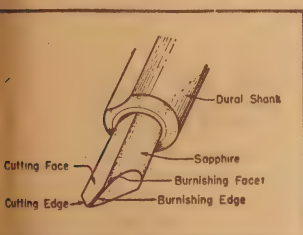


Fig. 1. Perspective view of lacquer cutting stylus.

onse, particularly on the inner grooves of 33 rpm records, where the groove velocity becomes small.

The effect was originally blamed on the inertia of old-style pickup and its effects on the softer recording medium. While there was some justification for this, considerable loss was still evident with lighter, high-compliance reproducers.

## LIMITATIONS

It was also suggested that a limit as being set by the relationship of a recording stylus dimension to the radius of curvature for high frequency waves recorded with limited groove speed. However, this could be disproved by geometric analysis, provided that the amplitude is kept below a certain critical figure.

Seeking another explanation for

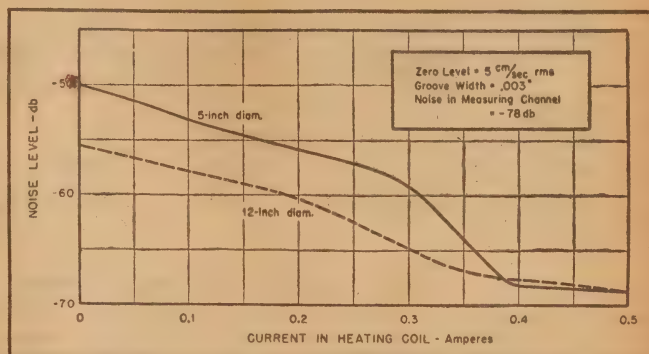


Fig. 2. Curve showing noise level in unmodulated groove vs. current in stylus heating coil. The noise is measured with a playback channel having uniform velocity response over a frequency band extending from 500 to 8000 cps.

the effect, an exhaustive series of cuts was made, using a variety of styli, recording materials, frequencies and groove speeds. These indicated that styli treated with facets did, indeed, show a marked high frequency loss, which was comparable with aperture losses in photographic recording or with the effects in magnetic recording of having the tape displaced from the magnetic head.

## NOISE PROBLEM

Attention, therefore, turned to methods of combating noise, while retaining the type of stylus used for cutting wax masters.

The theory was advanced that the smooth cut on wax was partly the result of locally generated heat "flowing" the wax and smoothing the sides of the groove as it was cut. The effect could not take place in lacquer because of its high melting point and harder initial characteristics.

It seemed, therefore, that heat could be applied artificially to the stylus and allow it to have the same effect on the lacquer surface. Accordingly, a small heating coil was provided and further test cuts made. An immediate improvement was noted, indicating that the theory was well founded.

Figure 2 is a plot of the noise of a cut made with a sharp edge cutting stylus, with varying heat currents applied. The noise was measured on a velocity basis over a band extending from 500 to 8000 cps. The 500 cps limit was chosen to eliminate hum and rumble vibration from the measurement, and

the 8000-cps upper limit was chosen to avoid response in the region where the dynamic mass of the reproducer at the stylus tip might resonate with the compliance of the groove which it engages.

Since these measurements were made on a velocity basis, it is evident that a further reduction in the measured noise would be obtained with roll off of the high frequencies, such as that used to equalize for pre-emphasis in recording. Even so, reductions of as much as 18 db in the background noise are readily effected, giving a resulting noise level 68 db below the NAB standard recorded programme level.

## HEAT USED

The actual temperature attained by the stylus was not measured, but based on the resistance of the coil, the power supplied is in the order of one watt. With values of current in the order of 0.4 to 0.5 amperes, the heat is sufficient to give equivalent results in respect to noise and high frequency loss. Data obtained with heat of this order agrees very closely with curve E of Figure 5.

This development, which was undertaken in the laboratories of Columbia Records Inc., now makes possible the cutting of lacquer discs with very low background noise and a minimum of high-frequency response loss. All of the advantages which formerly were peculiar to wax are realised, without sacrificing the convenience and utility of lacquer discs for direct playback and processing.



# HMV FREQUENCY RESPONSE RECORDS

## ED1189 Side 1

50, 100, 250, 1000, 3000, 4000,  
5000, 7000, 9000, 11,000, 13,000,  
15,000, 17,000, 19,000 cycles.

## Side 2

70, 160, 500, 2000, 3500, 4500,  
6000, 8000, 10,000, 12,000,  
14,000, 16,000, 18,000, 20,000  
cycles.

## ED1190 Same both sides

35, 50, 70, 100, 140, 250, 500,  
1000, 2000, 3000, 4000, 5000,  
6000, 7000, 8000, 9000, 10,000,  
11,000 12,000, 13,000 cycles.

**Graphs showing character-  
istics will be supplied with  
each record.**

**Each recording 9/- plus postage. Packing  
charge 1/6 for country and mail orders.**

## DECCA *ffrr* RECORDINGS

EURYANTHE OVERTURE - - - - K 1154  
AMARILLI - - - - - K 2070  
(LA RONDE DES LUTINS)  
ZEPHYR OP 35 - - - - K 1799  
LA SCALA DI SETS - - - - K 2123  
ADAGIO AND FUGUE IN C MINOR  
Griller String Quartet - - - - K 2224  
THE WALTZ DREAM OVERTURE  
THE CHOCOLATE SOLDIER—March - - K 2231  
SWAN LAKE BALLET—National Symphony  
Orchestra - - - - AK 1308/  
JOHN IRELAND SONATA IN D MINOR—  
Frederick Crinke - - - - AK 14003/  
HAYDEN SYMPHONY No. 88 in G  
MAJOR - - - - AK 1472/4  
BRANDENBURG CONCERTO NO. 4  
IN G—Boyd Neel - - - - AK 1616/7  
SYMPHONY NO. 5 IN D MINOR OP.  
107 (Reformation) - - - - AK 1715/8

CONCERTO IN ONE MOVEMENT  
FOR VIOLIN AND ORCHESTRA - - AK 1822/3  
SLEEPING BEAUTY BALLET SUITE—  
BBC Theatre Orchestra - - - AK 1524/5  
MOTHER GOOSE SUITE — National  
Symphony Orchestra - - - AK 1342/3  
LA FOLIA (Variation Serieuses) - - AK 1670/1  
ELIZALDE: CONCERTO FOR VIOLIN  
AND ORCHESTRA - - - - AK 1777/9  
SCHEHERAZADE - - - - AK 1966/7  
MOZART SONATA IN G MAJOR —  
Eileen Joyce - - - - AK 1800/1  
SCHEHERAZADE SYMPHONIC SUITE AK 1980/5  
BRANDENBURG CONCERTO NO. 5 IN  
D MAJOR - - - - AK 1889/91  
MENDELSSOHN: Concerto in E MINOR for  
Violin and orchestra—Alfredo Campoli AX290/2

**Each recording 10/6 plus postage. Packing  
charge 1/6 for country and mail orders.**

### TRADE INQUIRIES INVITED

**For our full range of Amplifiers, Record Players and accessories.**



**Audio Engineers Pty. Ltd.**

422-424 KENT STREET, SYDNEY. Phones: MA9537 - MA9538.

**OPEN ON SATURDAY MORNINGS**

Victorian Factory Representative: John L. HARROWER, 71 Little Lonsdale St.,  
Melbourne. Phone Central 8519



# HOW IT WORKS—MAKING PLASTICS

This may be said to be the age of plastics, for during the 20th century industrial chemists have produced a whole range of new substances that are not only utilitarian but attractive and they have replaced traditional substances in many fields. Still there is no sign of an end to the range and complexity of the new plastics.

NO longer is it necessary to use a natural substance such as wood or metal simply because it is the nearest thing available to meet the requirements. Now the customer can state the properties required and the chemist will probably get very near to meeting all of them with a "new" substance.

Use of plastics has revolutionised production methods in many instances, for the plastic material is, as the name implies, capable of being moulded.

A recent American survey showed that plastics now exceed most of the non-ferrous metals, including aluminium, in annual tonnage. In the past decade production has leaped upward to a 600 per cent overall increase, American figures show. In the United States, there are now 15 major types of plastics in production, of which seven were introduced or reached major status only since the end of World War II.

## WIDELY ACCEPTED


These recent strides have been made largely because plastics are no longer regarded as substitutes, but as materials in their own right. The term "synthetics" is no longer valid.

It is more than 80 years since the first plastic was produced. It was celluloid, made from guncotton and camphor by Alexander Parkes, of Birmingham, in 1864.

Only minor improvements were made until early this century, when Dr. Leo Baekeland, a Belgian chemist working in the United States, made "bakelite" from carboic acid and formaldehyde. These substances are both liquids, yet when they are heated together they become a solid which can be moulded before it sets. Bakelite is a "thermoset" plastic — one formed and fused by heat and pressure into a final and irreversible shape.

Another group of plastics has been developed which can be formed under heat to harden upon cooling, and then can be remelted and re-formed at will. These are known as "thermoplastics."

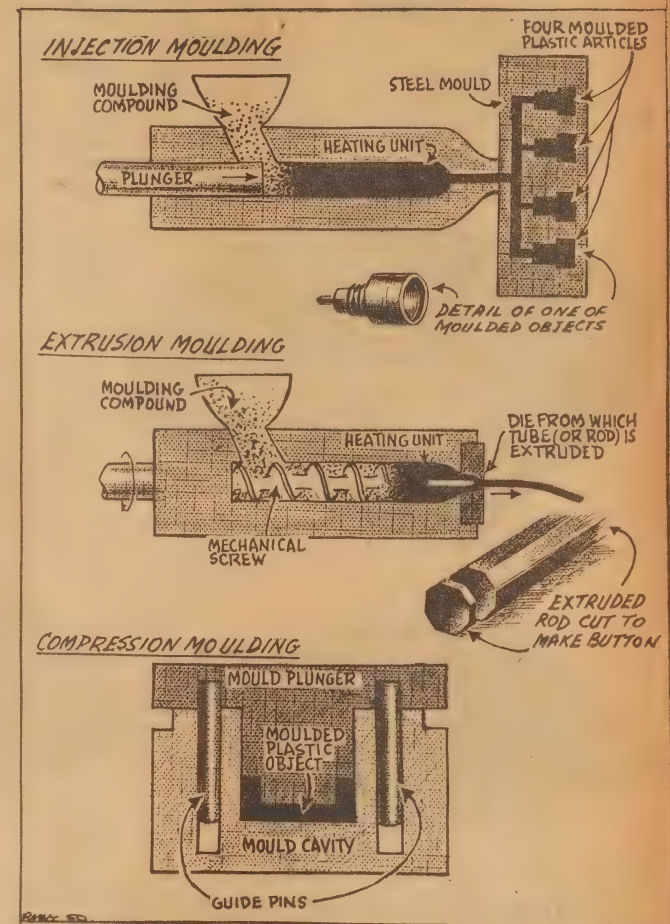The thermosets are harder, more stable and more durable, and they are the plastics of heavy industrial uses. The thermoplastics fall within two



main groups—the "cellulosics," based on cellulose, and the "synthetics," based entirely on chemicals.

The number of plastics with different properties is now so great that fabricators are having difficulty in keeping pace with them.

## MOULDING METHODS

The sketches here show the three main forms of fabrication — injection, extrusion, and compression moulding.

Injection moulding, the leading technique in all forms of thermoplastics production, is performed by a variety of machines. The operation is shown in diagram form, with the moulding powder feeding from a hopper into a long heating chamber. The powder softens and forms into a solid but pliable substance under the heat, and in this form it

is rammed out by a plunger into a mould, where it cools and sets.

Extrusion moulding is used in the fabrication of most thermoplastics. It is used in forming continuous tubing, rods, webbing, and so on, and from the extruded rods sections may be cut to produce buttons, buckles, and other similar articles. A garden hose is extruded in its finished form. The technique is broadly similar to that of the injection moulding, except that in extrusion moulding the process is continuous. Pellets of the moulding compound are fed from the hopper into a heating chamber by the pressure of an endless screw. As the material is heated it melts and it then passes out through a forming tube.

Compression moulding, used in the production of thermosets, calls for

(Continued on Page 49)



# RADIO DEALERS!

EQUIPMENT MEANS  
RECORD NEW SALES



AVAILABLE  
WITH  
MICROGROOVE  
ATTACHMENT




## R.33 PORTABLE RECORDER AND PLAYBACK UNIT

Two recordings and playback speeds—78 and 33 1-3 r.p.m. A single head, with excellent frequency response, performs both cutting and playback operations—plays ordinary commercial recordings, too! R.33 cuts records of high quality up to 12" in diameter at standard or microgroove pitch. Amplifier is of original and progressive design. It has been built by engineers for engineers and men who recognise superior technical skill. The R.33 is an ideal unit for sound film applications.


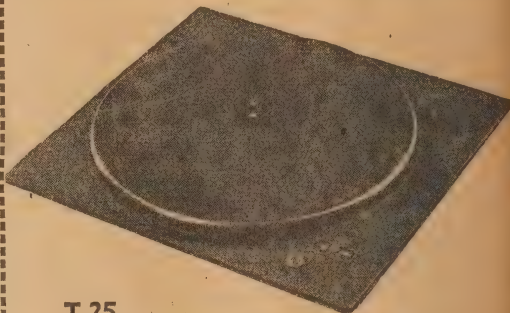
## R.12.D RECORDER AND PLAYBACK UNIT

This is the same unit as incorporated in the R-33 and is intended for installation and connection to your own radio or sound projector amplifier.



## T.25 SUPER SILENT TURNTABLE

A professional type turntable for amateur use, available with or without pickup. The T-25 will rotate at constant speed. As a result, "wow", "flutter" and "rumble" so often found in ordinary turntables has been completely eliminated. Wide margin of reserve power and inertia of the cast turntable overcome the common tendency to slow down on the heavier passages and more violent transients. The motor, mounted on floating buffers, is synchronous and gives constant correct speed, at either 78 or 33 1-3 r.p.m.

MANUFACTURED BY

### INTERSTATE REPRESENTATIVES:—

WM. J. McLELLAN &  
CO. PTY. LTD.  
55 York St.,  
Sydney. BX2508.

CARLYLE & CO. LTD.,  
915 Hay Street,  
Perth. B9371.

A. E. HARROLD,  
123 Charlotte Street,  
Brisbane. B2729.

NEW ZEALAND  
SWAN ELECTRICAL CO.  
LTD.

Wellington, Christchurch,  
Auckland, Dunedin.

L. S. WISE & CO.,  
14 Pirla Street,  
Adelaide. Cent. 818.

GILES & ELLIOT LTD.,  
Wellington.



# BYER INDUSTRIES PTY. LTD.

8 Dorcas Street, South Melbourne,  
Victoria.



# NEWS AND VIEWS OF THE MONTH

## The "Tron Family"

WHETHER first coined the word "electron" also gave to the English language its most over-worked suffix. Since that memorable day, any electrical device put on the market has automatically qualified, it seems, to have the four magical letters t-r-o-n tacked onto its name.

Irrespective of time, race and creed, the list continues to grow and, to save you from "tronning" on someone else's corns, an American magazine has come out with an alphabetical list of the 200 words they happen to know about.

We learn, for example, that the "Acratron" is a "self-balancing" a-c potentiometer-type electron recorder. The "Charactertron" is a C.R. tube displaying a series of numbers, while the "Orgatron" is an electric organ.

The Japs contribute "Detectron" for a line of radio tubes while the Swiss have their "Zyklotron," a special high frequency tube.

But the game still goes on, for the "Calutron" is "an electromagnetic type of uranium isotope mass separator"—a device which certainly sounds up to date.

The problem will become really sticky when the number of new electronic devices catches up with the possible letter combinations which can be posted ahead of the suffix. At the rate things are going, that won't be long.

## Plastic Embedded Circuits

WE are fairly used now to the idea of printed radio circuits, in which connections, resistors, and condensers are actually printed on the insulating material which forms the "chassis" of the equipment. This technique is now quite freely used, mainly for special devices where a high repetition rate and compact assembly is important.

A new development, not actually on the printed circuit idea, but applicable to small assemblies, is that of imbedding completely wired assembly in a solid block of insulating material.

Naturally, this material must have good insulating properties, and for this reason, polystyrene is often used.

The components included in the moulded plastic block include even the valve, as for assemblies such as this, miniature valves and sub-miniatures are frequently used. The latter have no socket, only wires

which solder into the circuit. Where the "bridgework" of component and connections has been put together, it is then embedded to form a permanent unit, which must be discarded when faulty.

Although quite good results seem to have been achieved by normal compression or injection moulding, difficulties are met with, as might be expected, through the use of high temperatures and pressures which injure components.

For this reason, special polystyrene casting resins have been produced which are used under the polymerization process, in which an initial liquid is transformed into a solid at low temperatures and pressures. The process is actually a chemical one in which distinct molecules react with one another or form a larger molecule. Various chemicals are used to hasten the solidification as catalysts.

One obvious application of embedding units is for the control of guided missiles, in which the assemblies are called upon to withstand very sudden and violent move-

## RADIO CROSSWORD PUZZLE, No. 36

### ACROSS

4. Dip in resonance.
8. Negative ions.
9. Valve elements.
10. Two element valves.
11. Urge forward.
12. Diaphragm attachment.
13. Unit of pressure.
19. Angle of .....
20. Screen.
21. Navigational aid.
24. Part of a circle.
25. Wave radiator.
26. Change resonant point.
27. Without magnetic property.

### DOWN

1. Condensers.
2. Single wire aerials.
3. Morse recorder.
5. Balancing circuit.
6. Aerials.
7. Transmitter.
13. Transmission unit.
14. Amateur's gear.
15. Radioactive element.
16. Loudspeaker.
17. They affect hearing sense.
18. Crystal detector.
22. For measuring.
23. Against.

## BELOW—LAST MONTH'S SOLUTION

B	R	A	N	L	Y		M	A	S	T	E	R
O		S		Y	G		N		E			E
O	P	T	I	C	A	L		T	E	S	L	A
S		I		E		A		E		T		M
T	A	R	G	E	T	S		N	I	E	C	E
S						S		N		R		R
	A	T	O	M	S		G	A	U	S	S	
C		R	O		D							M
A	N	I	O	N			I	M	P	U	L	S
R	O		I				O	L		A		G
C	A	D	E	T			D	R	A	P	I	N
E		E		O			E		T		R	E
L	O	S	E	R	S		S	E	N	D	E	R

1	2	3	4	5	6	7						
8												
				9								
10												
12							13		14			
											15	16
	17		18		19					20		
21										22		
							23		24			
25												
										26		
27												



# MORGANITE


# RESISTORS

**TYPES  
T and R**

These moderately-priced BRITISH Resistors combine high performance with unusually small size. They are made accurately to their stated resistance values and are consistently stable.

The simple construction of Morganite Resistors provides small, robust, light weight components of high power dissipation and low operating temperatures, and are colour coded to RMA Standard.


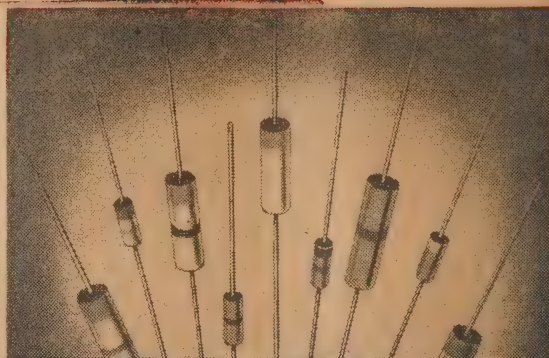
Stocked in preferred Standard values, viz., 10—12—15—18—etc., values rising in 20 per cent steps (approx.). Morganite Resistors Preferred Value Ranges are standardised in U.S.A. and U.K., and are now available in Australia.



# MORGANITE

MINIATURE

# POTENTIOMETERS

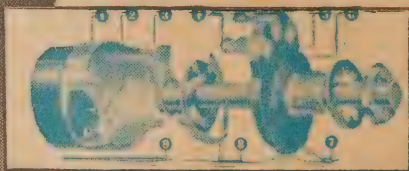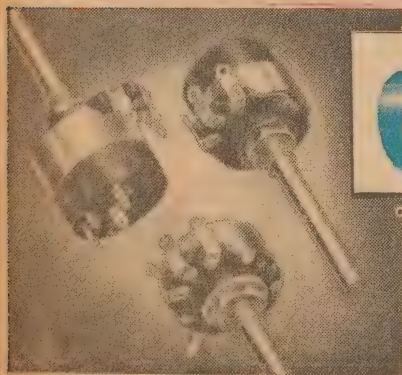

New in design ... British made ... and fully incorporates the traditional Morganite standard of quality.

Radio engineers will appreciate not only the small compact size of the Morganite Potentiometer, but the fact that it is available with a single or double pole switch of proved Morganite reliability.

## SPECIFICATIONS

- 1 Overall diameter 1 1/8".
- 2 Double pole or single pole switch operated from shaft.
- 3 Pressure diecast rotor and shaft for accuracy and strength.
- 4 DOUBLE CLENCH TERMINALS eliminate noisy joints.
- 5 Same track design for switch and non-switch type enables interchangeability. Switch type converted to non-switch by interchanging covers.
- 6 The renowned MORGANITE RESISTOR TRACK LOW noise, hard wearing, wide range of standard resistance values and gradings. Rating 1 watt.
- 7 Standard position fixed lapping available.
- 8 Double prong SPRING CONTACTS, in special non-furnishing metal for resistor sweep, maintains correct pressure for minimum noise without wear.
- 9 The switch withstands the most rigorous operating conditions. Rating: 2 amps, 240 volts.
- 10 Instrument QUALITY at LOW Prices.

**THE MORGAN CRUCIBLE CO. (AUSTRALIA) PTY. LTD.**

BOURKE ROAD ALEXANDRIA, N.S.W.

TELEPHONE MU1171

CABLES & TELEGRAMS "MORGANITE" SYDNEY



ments. In many other cases, small units must operate under adverse humidity and temperature conditions, all of which may be greatly reduced in their effect by sealing up the unit as a whole.

### ★ ★ ★ Miniatures

TALKING of small assemblies, it seems pretty certain now that the valve of the future will be of the miniature type as against the larger, moulded based types we have known to date.

It is a fairly obvious development, of course, as the whole centre of radio communication is now sliding down the frequency scale to such a degree that more valves are likely to be used on the high frequencies than on the broadcast band. In fact the poor old broadcast band is becoming less and less the star piece of radio, as all kinds of marvels unfold themselves in the electronic field up to thousands of megacycles in frequency.

Not all the new valves are capable of working efficiently at more than two or three hundred megacycles but there will be plenty of activity below this point which will include television stations and many growing communication links. Unless the modern valve can work well at these frequencies, it is certain to be marked down as "replacement only."

In any case, radio sets have been too bulky for years. There's no reason to make anything larger than it need be, any more than there is any reason to make things too small.

### ★ ★ ★ Canadian Television

IT is announced by the English Marconi company that the Canadian Broadcasting Company has ordered two outside broadcasting vehicles for its television system now in the course of construction. Marconi is already supplying the equipment for two studios in Toronto and Montreal.

Each vehicle will be a three-camera station, and be fitted with full video, audio, and radio link equipment.

The new order is worth 180,000 dollars.

Thus the complete studio and mobile side of Canadian television will be British made.


### ★ ★ ★ Protecting Foodstuffs

PHILIPS ELECTRICAL, of London, have devised a speedy system to examine foodstuffs for foreign bodies.

An X-ray system is devised which projects on to a fluorescent screen an image representing the largest possible area of the test piece. If any foreign body is present, the uniform image is marked by a darker area. The inspector, by means of a trigger mechanism rejects the spoiled sample.

To concrete instances typify the procedure's efficiency. Pieces of glass only .125in (.3 cm) in diameter were easily detected in bread 6in (15.2 cm) thick. Biscuits were examined at an hourly rate of 5000 packages.

## BUY SIMPLE SPEEDY SOLDERING WITH

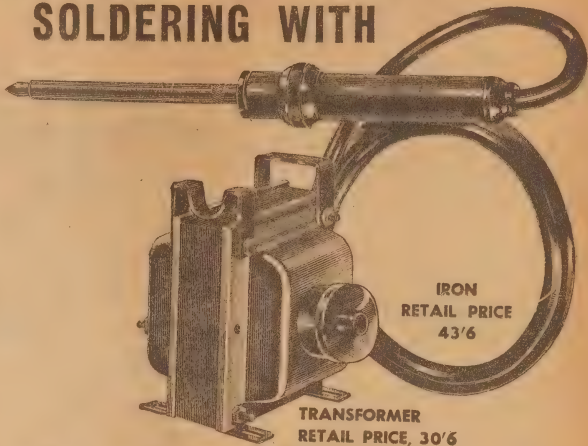

## SCOPE THE SOLDERING IRON THAT HEATS FOR CONTINUOUS USE IN 6 SECONDS

Scope is a new type soldering iron that gives amazing soldering speeds while operating from low voltages, even on the biggest jobs of work. To really appreciate the value of Scope you should see it demonstrated. It may be connected to a 6-volt car battery or, through a suitable transformer, to 240 volts A.C. To use, you merely push the switch ring forward with a light thumb pressure, and in six seconds the soldering tip is hot—ready for use with an efficiency equal to that given by other irons with ratings up to 150 watts. Scope gives modern efficiency and low cost, long-life soldering. See it demonstrated and you, too, will agree it is the best soldering iron value to-day.

### CHECK THESE FEATURES!

- Operates from 2.5/6.3 volts A.C. or D.C. or from mains with transformer.
- Heats up from cold to ready-for-continuous use in only 6 seconds.
- Has an efficiency equal to that of irons rated up to 150 watts.
- Weighs only 3½ ounces and is 10 inches long.
- Can be used in conjunction with a transformer from A.C. mains, or from any suitable car battery.
- Has low operating cost—no current is consumed when not in use; no frequent cleaning and tinning of the bit.
- Extremely suitable for heavy or delicate soldering—heat is applied only where and when it is required.
- Simple to operate—merely press switch ring forward and the iron is hot in six seconds.
- Maintenance is simple—elements and replacement tips are fitted easily and without delay. Replacements are screwed in and cost only a few pence.
- Fully guaranteed for three months from date of purchase. A maintenance service is available at all times.

You should see and test Scope for yourself. If you do this, you will agree it is the soldering iron you should and must have. Ring, write or call for illustrated pamphlet and a demonstration.

Australian and Overseas Agents:

## Wm. J. McLELLAN & CO. PTY. LTD.

Bradbury House, 55 York Street, Sydney. 'Phone: BX 2508.

MANUFACTURED BY SCOPE LABORATORIES, MELBOURNE, VICTORIA





# Let's Buy An Argument

It may be Sydney's recent weather, it may be the effect of old age or it may be the reaction from trying to live an ordered, respected life. Whatever the reason, I find myself sour, ill-tempered and resentful. I want an argument and what better subject could a Technical (?) Editor select than things that, to me, are the product of misguided technical enthusiasm.

**T**AKE direct-coupling, for instance. I can't recall any other subject about which so much technical twaddle has been written. To listen to some enthusiasts, or read their literary efforts, one would think that the elimination of a poor inoffensive coupling condenser offered a cure for all the ills that ever beset an electronic amplifier.

They go off into rhapsodies about "mysterious somethings," "magical qualities" and "amazing this and that's" ad nauseum.

## WHAT IS D-C?

To me, the irksome point is that so many so-called direct-coupled circuits are really not that at all.

To be sure, their promoters managed to tie a grid to a plate but they overlook the bypass condensers in the "earthy" coupling between the two cathodes. They overlook, too, the main HT bypass, forming the return path for the audio plate currents.

And if, perchance, a speaker field coil is connected to the output valve cathode—we have seen this arrangement too—there's inductive as well as capacitive reactance in the coup-

ling system and all the elements of a delightful tuned circuit!

If this is direct coupling, then I'm a Polynesian!

I did take the matter up once with a very insistent barracker for this type of circuit. He "proved" his point to his own satisfaction—by demonstrating how superior the direct-coupled arrangement was to a quickly substituted R/C network.

There certainly was a difference but a few minutes work with valve curves showed why. With the valve and coupling network used, the voltage amplifier simply could not drive the output valve without itself overloading.

## BALANCING

The demonstration, therefore, proved once and for all that direct coupling was better than badly-designed R/C coupling—a rather shattering conclusion!

Of course, I would do a gross injustice to many designers if I were to suggest that all claims could be "shot down" as easily as this one.

By resorting to push-pull, it is possible to obtain a degree of balance in the cathode and HT circuits

and thereby render bypass condensers much less significant in their effect. But other difficulties remain, notably the critical operating voltages required by high Gm tubes.

With valves like the 6L6, 807, KT66 and so on, the bias is critical within a volt or so. Too little wears out the tube, too much cuts the power and lifts the distortion. Since direct-coupled circuit amplify conditions along with the signal, the valve ahead of a power tube should exhibit a rock-steady plate current—and that's a lot to ask of any tube!

## NEED FOR METER

But there it is. If the initial stage doesn't happen to draw the current allowed for, it shifts the grid voltage of the output tube. Built-in compensating effects (if any) must be mighty good to keep the operating point in the centre of the curve.

As far as I can see, the only way to be sure of a direct-coupled amplifier is to run it all the time with a milliammeter in the output plate circuit. The alternative of twiddling a knob "till it sounds right" is about

as rough as the proverbial corksack.

And what is gained from all this fuss and bother? One school points to extended bass response, right down to zero cycles, if you like.

That's just the point. Most of the acoustic devices we know give up the ghost between 20 and 30 cycles, including loudspeakers, ears, drawing-rooms and grand organs.

## UNWANTED BASS

The only possible use for a response below that is to amplify cabinet feedback, rumbles, and motor-boats of the electronic variety.

Our friend D. T. N. Williamson, of amplifier fame, is an eloquent witness to the truth of this statement. Having built up a really "hot" amplifier he—and we—found it almost impossible to connect the necessary preamplifiers and compensators ahead of it without running into troubles I have mentioned.

We got around it by extraordinary measures of decoupling and stabilising. Williamson, on the other hand, suggested a high-pass filter arrangement to eliminate deliberately the excellent response which the ampli-



ties exhibited between about 1 and 20 c/s.

So much for this sub-sonic "bass!" Then there's a story about phase rotation and we'll enlarge upon this presently.

Direct coupling of the right kind will keep the phase straight between two stages at the bass end but it doesn't offset the things that happen to phase in the output transformer over the very same frequency range. Nor has it the slightest effect on phase rotation at the top end.

Our friend Williamson used it between two stages because it helped him apply nearly twice the normal amount of feedback from output to input. It was this feedback, together with the "sooper-doooper" output transformer that accounted for the special characteristics of his amplifier.

### TREBLE LOSS

As for the rest, direct-coupled amplifiers suffer treble loss just as much as any other, as the result of shielding, bypass condensers and "Miller" effect.

Precisely the same limitations apply in regard to power output, harmonic and overload distortion, sensitivity and so on.

Last, but not least, the method of coupling has no effect on the impedance characteristics of the output stage. In the case of pentodes, it's as important as ever to use feedback or otherwise damp the loudspeaker, to preserve the transient response.

Need one say more?

But just before you reach for the sword, remember that I haven't said direct-coupled amplifiers should be forgotten once and for all. They are valuable in television circuits, control gear and so on but, in audio, well...? A rather awkward way of doing nothing in particular.

I haven't suggested, either, that your direct-coupled amplifier doesn't sound tops. Maybe it does! But for heaven's sake be realistic and admit that the performance is due to a variety of other well-arranged circumstances—not just the omission of a sixpenny component.

### WILLIAMSON'S CIRCUIT

I trust you have not gained the impression that I worship at the Williamson shrine, just because his name has been mentioned and much publicity given to his circuit.

His original 807 triode amplifier (or the various versions of it) are about the best which ever got into home-builders' hands, and also the most expensive! If you overlook the difficulties of adding extra stages for gain and compensation, the end result is hard to fault. But the point is, how does the listener know it's so good?

To be quite practical, the distortion of a commercial record pickup combination can be written down at say 10 per cent. I know I haven't specified the kind of distortion or the waveform or the frequency, but

the figure will do as a mental reference.

Then there's the speaker which puts all kinds of beats and peaks into the response, being aided and abetted by practical baffles, by random reflections and by standing waves in the room. Let's put all that down as another 10 per cent.

How the deuce, then, is the listener going to judge whether the am-

plifier introduces a mere 2 per cent or 0.2 per cent as its quota, representing the difference between a "good" and a "very good" job.

As I've said in other places, I don't think at this stage of the game that the amplifier is nearly as critical as all that, once a certain degree of performance has been achieved. When record companies and broadcasters have pulled up their technical socks, a more rigid approach may be warranted.

In the meantime, the real problem is to clean up the devices fore and aft and make the wide-range stuff even tolerable to listen to!

Which brings me to another point. Two separate trade identities recently upbraided me no end for apparently ignoring a certain type of amplifier circuit. One, who should know better, even confessed to abandoning the Williamson circuit because this one sounded "flatter and cleaner."

What utter rot!

If there was such a difference, then I can only say that the original job must have been operating very badly for it to be apparent.

Apart from sheer pig-headedness, there is some such reason, I feel, behind most of these "one sounds better than the other" reports. Faulty components, mistakes in the wiring and oscillation effects can eternally damn the best circuit in the eyes of a home constructor. Or the preference may be based on different gain characteristics, or the ease with which it happens to attach to some other device.

And let me say this in hushed tones. Even the great can be deluded into voting for an amplifier or other gear with poor response, because of its ability to suppress the not-appreciated distortion in a programme source.

Ears are notoriously unreliable when it comes to judging sound quality. They can pick obviously restricted range or obvious distortion but, once that stage is passed, you can kid them up a hill and down dale.

### PEAKS

Listen to a pickup with a 10 kc. peak for a while and you're willing to swear that a flat pickup, played immediately afterwards is lacking in highs.

Or try compensating speaker response while listening to a musical programme. After the first half hour you'll swear that black is white.

I know only one approach that really works. You set up the speaker on one side and as many instruments as you can muster on the other. Then, like the old road sign, you Stop, Look and Listen!

It becomes apparent that No. 1 pickup sounds brighter than No. 2, mainly because No. 1 has a peak up near the top end. You find out that No. 3 sounds heavy, because the input transformer is poor. You find that conventional crystal pickups are lacking in the top register, despite, emphatic, but ill-informed statements to the contrary. So it goes on, ad infinitum!

I can only stand amazed at those who quite seriously suggest that

by W. N.  
Williams





# *performers!*

## The—KINGSLEY—“Standard”—Line

### Type No. CLASSIFICATION:

### OPERATIONAL:

KC1	AERIAL	GENERAL PURPOSE. HI "Q", GAIN & SELECT
KC2	R.F.	GENERAL PURPOSE. HI "Q", GAIN & SELECT
KC3	OSC-6J8GA	455 Kcs. DESIGNS FOR ANY CONVERTER. WINDING TECHNIQUE DEVELOPED BY KINGSLEY PRODUCES NEAR UNIFORM OSCILLATION OVER TUNED BAND.
KC4	OSC-6BE6	
KC5	OSC-ECH33, X61M, 1R5	
KC6	OSC-6AN7	
KC7	OSC-6A8G, 1C7, 1A7GT	175 Kcs. — REPLACEMENT COIL HI Z TAPPED PRIMARY, HI "Q" SECONDARY GENERAL PURPOSE T.R.F. HARTLEY CIRCUIT
KC8	OSC-AUTODYNE	
KC9	REINARTZ	
KC10	RF WITH REACTION	
KC11	B.F.O. 455 Kcs	SERVICEMAN'S REPLACEMENT UNIT
KIF1	455 Kcs No. 1 Autodyne I.F.T.	SERVICEMAN'S REPLACEMENT UNIT
KIF2	175 Kcs No. 1 Autodyne I.F.T.	HIGH GAIN, IMPEDANCE & SELECTIVITY
KIF3 & 4	455 Kcs No. 1 & No. 2 I.F.T.	STANDARD GAIN, IMPEDANCE & SELECTIVITY
KIF5 & 6	455 Kcs No. 1 & No. 2 I.F.T.	LOW GAIN, LOW NOISE, TWO STAGES
KIF7 & 8	455 Kcs No. 1 & No. 2 I.F.T.	DOUBLE CONVERSION CHANNELS
KIF9 & 10	1900 Kcs No. 1 & No. 2 I.F.T.	TECHNICAL DATA (BANDWIDTH, ETC.) AVAILABLE ON APPLICATION TO OUR LABORATORY
KIF11	10.7 Mcs F.M. I.F.T.	
KIF12	10.7 Mcs F.M. DISCRIM.	
KIF13	10.7 Meg. F.M. RATIO DET.	

\* SPECIFY KC1, KC5, KIF3 & KIF6 FOR "KIT NUMBER 2"

# KINGSLEY

THE GREAT NAME IN AUSTRALIAN RADIO

KINGSLEY RADIO, 3 CORNELL PLACE, CARLTON



the road to good sound must not be barred by such infernal things as distortion meters, inter-modulation tests and CRO's.

Ears are like women. They react favorably or otherwise but they seldom know why!

A while ago I mentioned phase rotation and the way some folk turn handsprings at the thought of it. But have you ever stopped to think what a completely random thing phase is?

Down there, in the orchestra, there are 20, 50, 100 instruments playing away, all slightly out of tune and each string, or reed, or air column, vibrating quite independently of its neighbor. The sound waves get out into the auditorium and proceed to bounce hither and thither with gay abandon, ultimately reaching the listener's attentive ear—or the microphone.

PHASE ROTATION

Let the microphone swing slightly or the trumpeter sway forward, and you get, not only a complete rearrangement of phase, but a bit of "Doppler" effect into the bargain! This being so, I can't for the life of me see what harm a bit more phase rotation can do in the amplifier, provided that nothing else goes on at the same time.

I'm well aware that the great have been arguing this question from the days of my callow youth. But the weight opinion now seems to be that phase rotation is essentially an alternative manifestation of the same factors which ultimately limit response.

At high frequencies, for example, the presence of shunt capacitance is likely to cause phase rotation before it operates sufficiently to make a noticeable difference to the gain/frequency characteristics. Similarly, at low frequencies, coupling and bypass networks and transformers, produce their own quota of phase shift.


In a multi-stage amplifier, phase shift from various causes will tend to add or cancel and one can't draw much in the way of conclusion from a phase loop pattern on the CRO screen. In fact, it appears to have no practical significance, provided that frequency response conforms to the required pattern, the distortion is low and feedback paths don't become positive rather than negative at any frequency that matters—taking the last phrase in its wider sense.

COMPENSATION

There seems to be some self-contradiction here, I admit, because the best amplifier would apparently be one exhibiting the least phase shift, and Williamson's effort stands vindicated.

In the laboratory sense, that is perfectly true but just so long as it is necessary to cope with other than perfect motors, records, programmes and speakers, so long will it be desirable to impose clear limits on amplifier response. And in so doing, some phase rotation is a moral certainty.

All of which brings me to the next

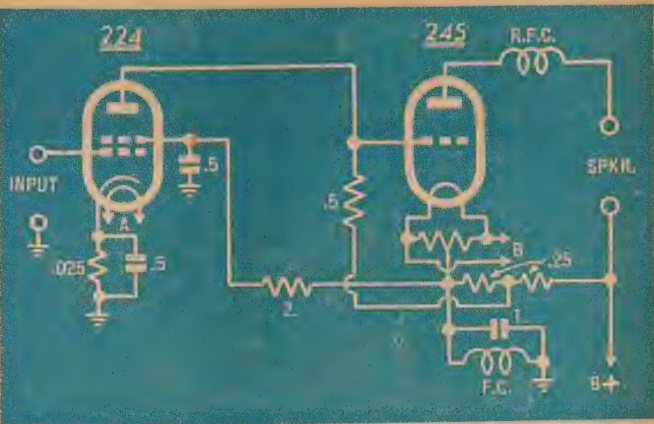

A typical direct coupled circuit as referred to in this article. It was taken from one of our very early issues—hence the ancient valve types.

point. Every once in a while, I am assailed by an enthusiast who, with puritanic fervor, refuses to have anything to do with artificial doctoring of frequency response. He won't touch filters, compensators and tone controls of any kind.

Some adopt the approach of a misguided purist. Others rant and rave about phase distortion. But let's have a crack first at the purist who reasons like the cotton field Negro—"If the good Lord made sound that way, then that's the way it should stay."

All of which is pure bunkum! In an effort to get more playing time on a given disc, recording engineers deliberately taper off the bass response below a figure which may be anything from 250 to 1000 c/s, depending on who the engineer works for. In addition, he may boost the treble by a certain amount above a certain frequency, again depending on local standards.

Every pickup on the market is a compromise between conflicting design factors, and no two of them have the same frequency curve. The same applies to speakers. The purist is left in the ridiculous position of faithfully reproducing and jealously guarding a signal containing a very

large amount of frequency distortion.

When the same records are played over a radio station, a suitable compensation (we hope) is applied, anyhow, to the bass register and the top, lopped off according to the ideas of the engineer and the diligence of his control operator. If it's a live programme, then the frequency law is likely to vary somewhat with the lines, the microphone, and the physical distance from the performer.

You can attribute all this to providence if you like—but not this child! If I know that frequency distortion exists, then I want to compensate for it. And if human weakness subjects my ears at times to guttural groanings or sizzling distortions, a want to be able to take some action, on my own account.

RECORDING END

Phase rotation I regard as an inevitable by-product of any circuit with a changing frequency law. In other words, you can't have tone compensation, tone control and so on without phase rotation.

But just before you ban it on this account, remember that, back at the recording studio, or wherever the programme originated, the de-emphasis and pre-emphasis applied to the signal must likewise have produced phase displacement. What's more, there's a good chance that measures you apply to correct the frequency response will also tend to restore the original phase-relationships.

Once again, the purist is in the position of eliminating phase shift in his own gear, but jealously guarding the quantity inserted by those who handled the signal before him.

If you don't agree, I can only leave you to the heroic defence of something which I hope you can define. Frankly, I can't.

Just to round all this off, I must bring in our contributor to the last issue—I refer to Mr. S. V. Hosken, of stations 3LO-3AR.

(Continued on Page 63).

RIGHT OR WRONG?


DO you think Neville is right or wrong?

Apart from the fact that he has shamelessly purloined a couple of my pet ideas, I intend to be neutral and will publish the best of your replies to him if you'll write and say so—no holds barred! And if you also have a few pet ideas or "notes"—them as well. What about triodes sounding better than pentodes with feedback? That one should bring out some really good discussion. So grab your pen and paper, and let me know!

THE EDITOR.



# two of the best...

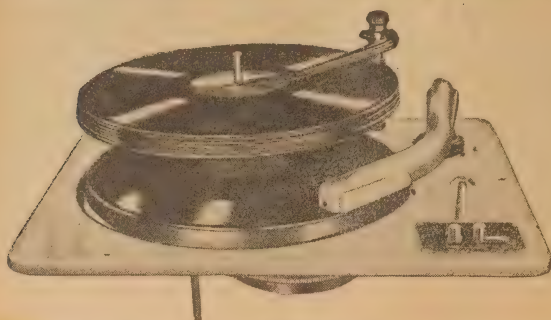

★ *SIMPLICITY is the secret  
of COLLARO success.*

## RC500 "COLLARO" the world's best record-changer

*Check these outstanding COLLARO advantages against any other record-changer.*

- |  |   |
|--|---|
| <ol style="list-style-type: none"> <li>1. With only three moving parts the COLLARO always remains in adjustment and cannot jam.</li> <li>2. Plays nine records, either 10" or 12" as selected.</li> <li>3. Amazingly quick and easy... to load... to play singles... to reject... to unload... to stop.</li> </ol> | <ol style="list-style-type: none"> <li>4. Crystal or high fidelity moving pick-up</li> <li>5. Incredibly light needle pressure.</li> <li>6. Twin ball-race pick up mounting.</li> <li>7. Triple twin-spring mounting of entire unit.</li> </ol> |
|--|---|

And when you hear it, add to these 7 big features the true fine reproduction of COLLARO — England's finest record-changer.

## The best on record...

*Also available in straight and  
midget light-weight types.*



Sole Australian Agents

## ELECTRONIC INDUSTRIES IMPORTS Pty. Ltd.

(Division of Electronic Industries Limited)

666-670 Chapel Street,  
South Yarra. BJ1227.

52 Bowen St.,  
Brisbane. B7161.

147-149 Castlereagh Street,  
Sydney. M6031.

90 Grote Street,  
Adelaide. Cent. 1780.  
EI/2655



# FROM THE SERVICEMAN WHO TELLS

AS it is, we content ourselves with occasional glances at the leaden skies and reflect that it can't go on forever. Some day the rain must cease, the mud must harden and the radio gear dry out again.

I had only just finished my last article when I came across an item in a daily paper headlining the trouble people were having with hearing aids as a result of the humid weather. Apparently the moisture is affecting the miniature microphones and earpieces with which these things are fitted and upsetting, too, the values of the tiny high-resistance components.

Whatever the ultimate details, the owners were advised to obtain a quantity of silica gel crystals, put them in a cloth bag and shut them up overnight with the hearing aid in a screw-top, airtight jar. There followed the same explanations that I gave about the color of the crystals when wet and dry:

I felt at the time, that my story might seem to be something of a "ring-in" but it obviously had a wider application than I imagined when it was written. Thus assured, I can safely go ahead with this next anecdote.

## MORE HUMIDITY TROUBLE


Most of my routine voltage measurements are done on a pocket-type multimeter, which has become as much a part of me as my trousers. Whenever I want to measure volts, this handy little device always seems to be on hand.

If more accurate readings are required, I refer to an imposing instrument which I built many years ago in a moment of youthful enthusiasm. Most of its life has been spent screwed to a support near the wall and its continued accuracy has always been a point of personal satisfaction.

However, I noticed the other day that the "ohms" range was not coming to zero. Assuming that the pot. had failed, I merely made a mental note of it and turned back to the little portable fellow.

Figure 1. A start-ling but completely factual result of the recent high humidity. Leakage paths through the bakelite panel and the wiring shunted the voltage multipliers and ruined the accuracy of reading.

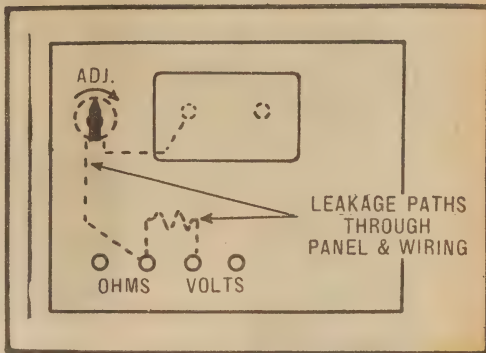But a few hours later, the big meter gave me such a fantastic voltage reading that I knew something



It's still raining in Sydney as I write and the score in points and inches is creeping up to an all time rainfall record. I'm hearing more and more stories about the effect of moisture on radio and similar gear and it is obvious that, if local rainfall were always on this level, something would have to be done about it.

had really gone amiss. Just to check the point I measured the mains voltage, to receive a reading of just on 300! Whatever else the mains do at my place, they never get up that far.

The meter was ultimately taken from its case and what a sight greeted my incredulous gaze. Every one of its pre-war cotton-covered leads was sprouting a crop of fungus, known as "lettuce" in better-informed circles. The same lush growth was apparent on every one of the paper labels.

It took me quite a while to get all the goo wiped off and the multiplier resistors were then stripped out for a check. Much to my surprise, there was only one of them off value and this happened to be the 5000-ohm resistor for the 5-volt range. All the others were right on the mark, as far as I could see.

The parts were duly wired back into the meter and the readings checked. Believe it or not, they were still hopelessly high.

I didn't discover why until after most of the wiring had been lifted free from various this and that and

careful checks made with a VT voltmeter. Believe it or not, the parallel resistance values upsetting the readings were across the bakelite panel itself. Between two pin-jacks mounted an inch apart, I could read just 7 megohms. Is that moisture or is that moisture? It took me a whole day's treatment in front of a fan and a radiator to get that panel back into shape — electrically, I mean. After that the inside of the wooden-cum-leatherette case had to be cleaned, dried and re-stained to get rid of the fungus. I wonder how many other servicemen have had similar experiences?

## TELEVISION TROUBLES

Whatever experiences might be forthcoming, they can hardly rival those which are becoming commonplace to US servicemen handling television receivers. I can't resist the temptation to repeat a couple picked up from a current issue of the contemporary journal *Radio Electronics*.

The first case quoted involved a woman in Manhattan who complained that the television receiver was intermittent on channel 2 — whatever that means in terms of frequencies and call-signs. The serviceman, one Ed Woolman, found the set operating but the picture disappeared as he removed a large vase from the top of the cabinet.

Inspection showed that the vase had a metallic ring weight on the underside which was apparently self-resonant at the frequency of channel 2. By some process of absorption or re-radiation, it was interfering with the normal operation of the VHF-tuned circuits in the receiver.

Then there was the case of Al Friedman who was faced with a

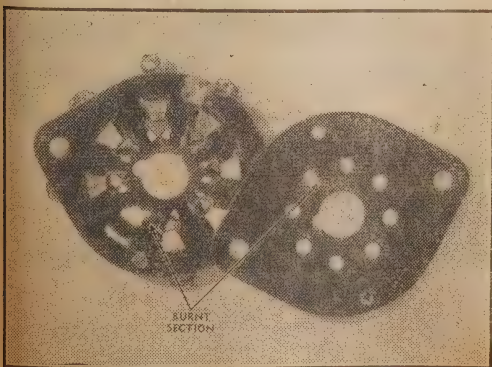


Figure 2. "Exhibit A," or the result of flux in a wafer socket combined with high voltage. Only charcoal remains between the plate and heater pin positions.



# BRAND NEW BENDIX 17 VALVE AUTOMATIC RADIO COMPASS TYPE MN26S

Freq. range 150-1500 Kcs. Comprising 12-valve receiver, remote control tuning, box-type MN28, automatic loop aerial type MN36, automatic azimuth indicator type MN37. 5-valve automatic loop control unit type MN31 and all necessary plugs and bowden cable. Operates from 24-28 volts D.C.


## COMPLETE WITH ORIGINAL INSTRUCTION BOOK

Containing 100 pages, plus 50 diagrams, circuits, etc. in original manufacturers' cartons.

Price, F.O.R. . . . .

Also available, new Bendix 15-valve BC-433 compass receivers on application.

**£39/10/-**

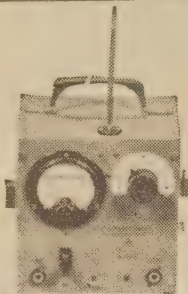

**FIELD STRENGTH  
METER-MONITOR**  
TYPE 88

Frequency range 100-130 mcs. or can be converted to any other freq. range by altering one coil. Complete with IN5G valve, imported 3-inch 0.1 MA meter and chrome-plated telescopic aerial, Jack provided for using meter for external measurements, also necessary plug and lead. Batteries encased within the unit. Size 6½ x 7 x 7 inches. Supplied in portable carrying case.

Price, New, Complete, **£4/10/-**  
less batteries, F.O.R.

Weight packed, 15lb.

## DISPOSAL VALVES, TESTED

1K7G	8/6	954	12/6
3Q5GT	10/-	955	12/6
6AC7	10/-	956	12/6
6AG7	20/-	9001	10/-
6H6GT	7/6	12A6	10/-
6SH7	8/6	12SG7	10/-
6SH7GT	8/6	12SK7	10/-
6SL7GT	12/6	12SR7	10/-
6V6G	12/6	EA50	7/6
7193	8/6	CV6	8/6
852	25/-	VT90 Micropop	10/-


## NEW VALVES

1D8GT	15/-	7C7	11/6
6B8	15/-	7F7	11/6
6F6	15/-	83V	11/-
6C8G	12/6	811	70/-
6H6	10/-	828	35/-
6J5G	11/-	837	25/-
6J7G	12/6	866A	25/-
6K9G	12/6	879/2X2	15/-
6S7	12/6	1293	11/6
		1294	11/6
6X5GT	12/6	VR54/EB34	5/-
7A6	10/-	VR65A	5/-
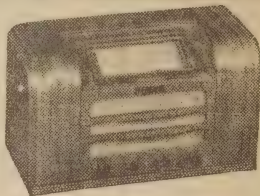
## COAXIAL CABLE

Polystyrene Insulation

PS 11/M 72 ohm, 60ft. lengths. Only 5/16 inch O.D.  
Price per length **30/-**  
Packing and postage: N.S.W., 1/6; Qld., Tas., Vic., 2/6; S.A., W.A., N.T., 3/6.



Weight packed, 70lb.

BRAND NEW

## BREVILLE 5-VALVE DUAL WAVE RECEIVER


With 5 spare valves and vibrator cartridge FREE.

6-volt vibrator operated. Attractive walnut cabinet. Brand new, in original packing case. Ex-Amenities. 12 months written guarantee. Large, straight line tuning dial. Instruction sheet supplied with each model. 7-inch permagnetic speaker. Local, interstate and overseas reception.

USUALLY PRICED AT £45/17/6

OUR PRICE, F.O.R. **£29/10/-**

## U.H.F. A.S.V. RECEIVERS AR301

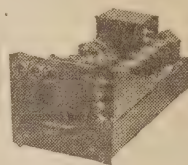

Complete with 11 valves: 2—R.F. stages, 954 acorns; mixer and oscillator, 2—955 acorns; 30 mcs. L.F. channel, 4—6AC7's detector 6H6 cathode follower 6AC7 rectifier 5V4G

Coaxial switching motor. 2-volt D.C.

Frequency range, 160-190 mcs.

Weight unpacked, 30lb.

Suitable with minor alterations for conversion to F.M. Band (58-108 mcs.). Television Band (175-200 mcs.), 144 to 288 mcs. amateur bands.

Complete with valves as above in vented metal case, size, 7½ x 8½ x 18 inches. Price, **£8/15/-**, F.O.R.

## 4W FLUORESCENT LAMPS


Colour: Blue. Length, 5½ inches. Ideal R.F. indicators.

Price, each . . . . . **2/6**

Per doz. . . . . **25/-**

Packing and postage 6d each.

## TWIN METER CONTROL UNIT

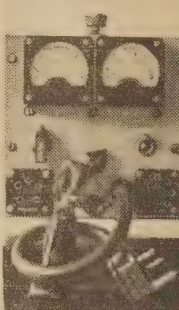

Comprising 2 imported 2in. flush mounting meters, 0.5 mA., D.C. and 20V. D.C.; 2 7500 ohm potentiometers; 7 position, 10 amp. rotary switch; S.P.-ST toggle switch; plugs, sockets, shock mounts, etc.

Price, ea.

**37/6**

Packing and Registered

Postage: N.S.W., 1/9; Qld., Tas., Vic., 2/9; S.A., W.A., N.T., 3/9.

## METERS

0-30 mA. D.C. 3-inch round flush	25/-
0-30 volt D.C. 3-inch round flush with datum indicator	30/-
0-300 mA. thermocouple. New	15/-
0-3 Amp. R.F. thermocouple. New Imported 2" square flush	17/6
20 mA. D.C. 300 amp. scale, 3in. round flush	25/-
20 volt D.C. 2in. square flush, imported	20/-
40 volt D.C. 2in. square flush, imported	20/-
40 amp. D.C. 2in. round flush, imported	30/-
20 volt and 200 volt D.C. 2in. round dual reading with leads	20/-

Packing and postage, 1/6 each.

## GENERATORS

24 volt 60 amp. D.C. **£11/10/-** (F.O.R.). Each  
Ideal for home lighting plants, battery charging, plating, etc.

## PUSH BUTTON SWITCHES

5-pole each, 2 pair of contacts. Made in U.S.A. Ideal for receivers, meters, etc.  
Price, **12/6** each  
Packing & Postage N.S.W., 9d; Interstate, 1/6.



# ELECTRONIC EQUIPMENT CO.

Please add exchange to all cheques. Make money orders and postal notes payable at Lewisham. Sorry, no C.O.D.

**LM3555—29b West St., Lewisham, Sydney.**

OPP. END OF LEWISHAM HOSPITAL  
(ADJOINING RAILWAY LINE)

**LM3555**







# Serenade your Sweetie

## WITH A PORTABLE...

Spring is in the air, the holiday spirit is afoot. Make it a really happy time with a portable radio. Get the added thrill of building your own.

### BUILD IT YOURSELF!


It's quite simple, provided you build to a tested and tried circuit and use only the very best components. Electronic Parts kits are compiled to specifications laid down by "Radio & Hobbies" and only the very best quality components are used. **EVERYTHING** necessary to build a first class portable is included with each kit.


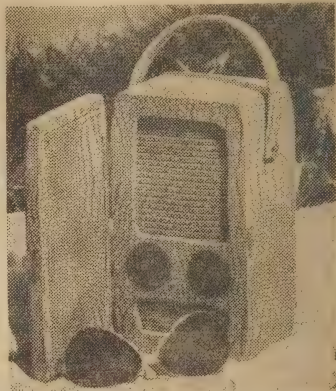
### CARRY SET

The smartest in small portables. This 4-valver is extremely simple to construct and is most efficient in performance. Note the smart lines of cabinet, size of which is  $8\frac{1}{2}$ " high x  $4\frac{1}{2}$ " wide x 4" deep. Originally described in "R. & H.", October, 1949.

Price for Kit complete with Valves, Cabinet and ALL necessary parts, £11/19/0 (Plus Postage).




### SENIOR PORTABLE

Originally described in "R. & H." for December, 1948, this 5 valve B/C portable, with R.F. Stage uses either 6" or 7" speaker. A kit of parts for an A.C. power supply is also available. Cabinet size of portable  $12\frac{1}{2}$ " x  $8\frac{1}{2}$ " x  $6\frac{1}{2}$ ".


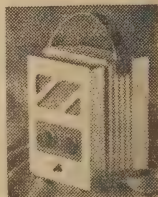
### HANDIE-TALKIE

("R. & H." Oct., 1947, and Dec., 1947). The smallest possible 5 valve portable. Ideal for distance-getting, combined with compactness. A four valve version also available in the same cabinet. Size 7" x  $4\frac{1}{4}$ " x 5".



### SPRINGTIME PORTABLE

("R. & H." Oct., 1946). A sturdy 5 valve portable with R.F. Stage which will take any amount of hard work. Cabinet size, including hinged lid, 13" x 8 5-8" x  $5\frac{1}{2}$ ".



### MULTI-TALKIE PORTABLE

("R. & H." July, Aug., 1948). As its name implies, this is a multi unit portable. It is available as a small 4 valve B/C portable and, in addition, an A.C. power unit can be built to enable it to operate from the A.C. mains, or a vibrator unit can be built to enable it to operate from a wet battery. Size of portable cabinet 7" x  $4\frac{1}{4}$ " x  $5\frac{1}{4}$ ".



Send coupon for free price list of these portable kits, which includes over 50 different varieties of radio kits (battery sets, A.C. sets, car set, grammo-comb, vibrator sets, 32-volt set, etc. etc.).

To ELECTRONIC PARTS PTY. LTD.,  
206 Broadway, N.S.W.

Dear Sirs,

Please send me without obligation on my part, price list of your portable kits. (Enclose stamp to cover postage.)

Name .....

Address .....

**ELECTRONIC PARTS  
PTY. LTD.**

E. S. and A. Bank Building,  
BROADWAY, SYDNEY, N.S.W.

Phone: MA 1661

Telegrams: ELECPTS, SYDNEY

**KIT  
SET**

**SPECIALISTS**



# PUTTING YOUR C.R.O. TO WORK

Once the operator understands the possibilities of the CRO all kinds of jobs can be found for it, over and above the routine testing procedures which have been described. This article discusses the behavior of output transformers and the use of the CRO for hum tests.

THE function of an output transformer is to change the load impedance to an effective value which will suit the particular output valve. Ideally the transformer should not produce any loading effects of itself.

In practice, most inexpensive output transformers have insufficient inductance to meet this requirement so that, at low frequencies, the actual load is heavily shunted by the inductive reactance of the output transformer windings. A considerable mismatch occurs, and the ultimate result is that distortion rises and the power transferred to the load is seriously reduced.

The core, too, is commonly of limited dimensions so that any attempt to transfer large audio power causes the iron to saturate on peaks and introduces severe distortion in the output waveform. The effect is particularly noticeable at the low frequency end of the spectrum.

Distortion due to these and other closely related causes is frequently encountered during amplifier tests, either by design or accident.

## OUTPUT TRANSFORMERS

To evaluate properly the limitations of an output transformer, it is essential that both the load and the CRO be connected across the secondary winding. Resistive loading allows maximum-power tests to proceed in silence but, to obtain the full story, it is often necessary to operate into speaker load and at the maximum power which the amplifier will be called to deliver in normal operation.

Naturally, too, the speaker system must be of such a size and so baffled

that it can safely handle the requisite power at low frequencies.

One might begin the test with a signal at 1000 c/s, setting the controls so that the amplifier is on the verge of overload. Power output can be determined by actual voltage measurement or simply noted by observing the height of the pattern on the CRO screen with the vertical gain control in a certain position.

It is often found that somewhat higher peak power can be obtained at 2000 or 3000 c/s, due in part to a peaking in the transformer efficiency, and also to a tendency for a drooping top response to discriminate against harmonics of a high frequency fundamental.

## CRITICAL REGION

Conversely, as the frequency is reduced, it is often found that the maximum undistorted power also diminishes, due to inadequate inductance, magnetic effects in the iron and poor coupling factor between the windings.

The critical region is generally below 100 cycles, where the maximum "undistorted" power output tends to fall away very rapidly. At from 50 to 30 c/s, the available power without distortion may reduce to a small fraction of that available in the middle register.

If the signal voltage is boosted in an effort to obtain high power at low frequencies, the output wave-shape from a poor transformer can assume a fantastic appearance, ranging from triangular and square effects to a completely random envelope, having no relationship to the original sine wave input.

While there is some connection

between maximum power figures and frequency response, the two quantities are not identical. It does not follow that a "flat" amplifier has a flat output power characteristic.

Frequency response runs are usually taken at quite low power levels in order to avoid overload effects and they do not take into consideration the maximum power limits of the output transformer in particular.

A frequency run might therefore indicate that an amplifier was substantially flat to say 30 c/s whereas, in actual fact, it may only be able to deliver one half the total peak power at 50 c/s, as compared with 1000 c/s.

The point must be considered in relation to amplifiers employing bass boost and/or negative feedback, and, especially, those in which the feedback is taken from the output transformer secondary to an earlier point in the circuit. Feedback or boosting can level a response curve, but neither can overcome the power limitations of a small output transformer.

The implications of these statements should be obvious to any enthusiast who requires plenty of output power at low frequencies.

## TYPICAL CASE

As a matter of interest, oscillographs are shown which indicate the performance of an ordinary speaker transformer handling the output of two moderately-run 807 valves. The waveform at 1000 c/s is good, but, for the same output power it is hopeless at the lower frequencies.

An oscillograph is very useful on occasions for tracing and eliminating hum in amplifiers.

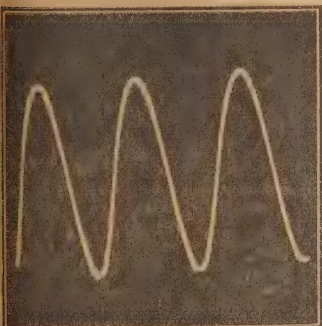


Figure 1. The output waveform from an inexpensive output transformer handling high power at 1000 c/s. Input power to the primary would approximate 15 watts.

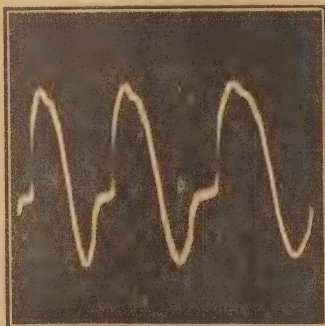


Figure 2. The same order of output from the same transformer, but at 100 c/s. Note the severe distortion, due to transformer limitations.

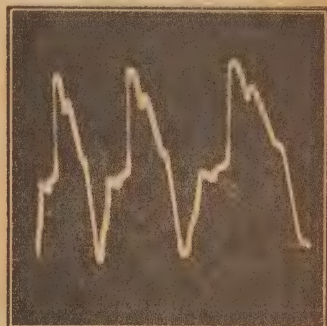


Figure 3. The output waveform at 50 c/s. Bass boost, negative feedback, &c., can level the response curve, but cannot eliminate overload distortion such as this.



# New!

## CONNOISSEUR PICK-UP HEAD

The pick-up coil is of high impedance, being 1300 ohms at 100 CPS. The output direct from pick-up is 1 volt from a standard recording of 12 db up on the zero reference level 1 cm/sec. RMS velocity.

With the connoisseur special coupling transformer the voltage across the secondary will be approximately .5 volts.

### Frequency response:

Taking 1000 CPS for our reference level, the output falls steadily and at 8500 CPS the loss is 5 db at 12,000 CPS the cut is 9 db down.

The response from 1000 CPS down to 50 CPS remains level. Bass resonance, which gives a steady lift from the 50 CPS mark and is of approximately 4 db's occurs at 25 CPS.




Obtainable from  
Selected Distributors throughout Aust.

## J.H. MACRATH & Co.

PTY  
LTD

208 LT. LONSDALE ST., MELBOURNE *Phones* CENT. 3688 4414
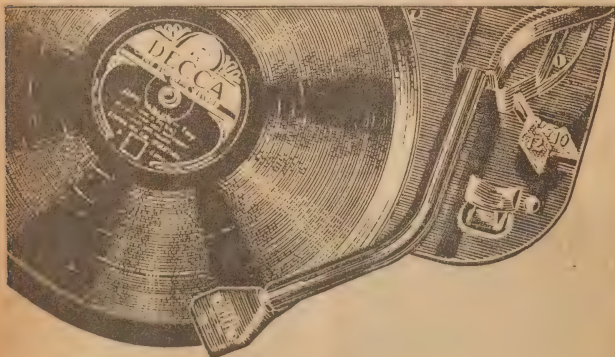
## ffrr - Full Frequency Range Re~production



## Plessey

### RECORD PLAYER

- The only Record Player featuring the patented automatic push-button start.
- The only Record Player which gives a choice of Decca ffrr, Acos Crystal or Magnetic pickup.
- The only Record Player which will increase your turnover and give years of trouble free service.

Distributed by:

## UNITED RADIO DISTRIBUTORS PTY. LTD.

RADIO-ELECTRIC WHOLESALERS

Showrooms: 175 Phillip Street, Sydney. Offices: 183 Pitt Street, Sydney.

TELEGRAMS & CABLES: URD, SYDNEY

TELEPHONES: MA 9251, MA 1563

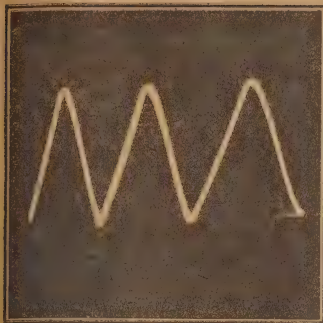


Figure 4. A hum pattern measured across the first filter condenser of a 4/5 valve superhet. The ripple is equivalent to an RMS measured voltage of approximately 10.

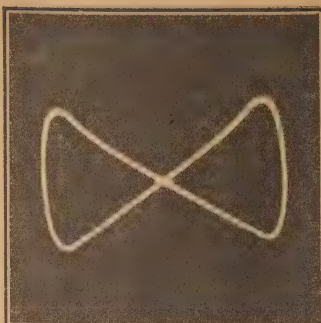


Figure 5. The same hum voltage, but using a 50-cycle horizontal a-c sweep. The figure 8 conformation indicated that the hum is predominantly 100-cycle in character.

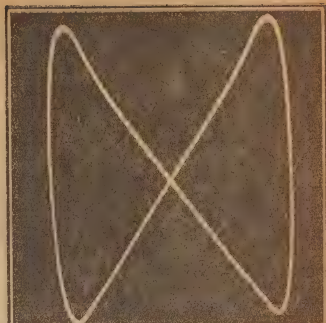


Figure 6. Showing the increased hum voltage apparent when one of the two filter condensers is removed. Such patterns show clearly the effect of extra filtering.

If one is prepared to go to a little trouble, it is possible to establish by ear what can be regarded as the maximum permissible hum level in particular types of receivers and amplifiers observing the height of the pattern on the CRO screen with the amplitude controls at certain settings.

## INTERPRETATION

Some interpretation of patterns is still necessary, however, because a hum with a high-pitched component is often more objectionable than one which is more or less pure and of very low frequency. Furthermore, the efficiency of speakers and baffles at the bass end can make all the difference between a hum being objectionable or otherwise. Many old-style receivers get away with less filtering than modern sets purely because they use speakers of low acoustic efficiency.

The more usual application of a CRO in hum tests is as a purely comparative indicator. It relieves the ear from the strain of listening to a low hum and trying to evaluate the effect of various corrective measures. The effect on a CRO pattern can be observed very accurately, whereas listening tests are uncertain and often inconvenient, particularly in noisy

locations.

By setting the sweep to a very low frequency, it is possible to view the hum as a wave train, but the resultant image is seldom a very pleasant one to watch for any length of time.

The alternative is to feed a 50-cycle voltage to the horizontal deflection amplifier and, for this very purpose, many instruments make a few volts available on the panel from one of the filament windings.

Since the hum is invariably related to the mains frequency, the use of a 50-cycle sweep naturally produces a steady pattern on the screen. The shape of the pattern is significant, and can give a clue as to the content and source of hum voltage.

## HUM SOURCES

Hum commonly originates from heater-cathode leakage, from chassis currents or from the filter system. The first two tend to produce a predominant 50-cycle component, while the third produces a predominantly 100-cycle component, representing the output from a full-wave rectifier.

When posed against a 50-cycle sweep, a predominantly 50-cycle hum voltage will tend to produce an irregular loop or circle. Faced with such a figure, the operator can largely ignore

filter problems and concentrate on sources which are likely to inject a 50-cycle component into the circuit.

## WAVEFORM

Such components can be relatively pure or just the reverse, according to the method of injection. Eddy current or heater-cathode effects often produce a substantially pure 50-cycle hum but, by way of contrast, figure 9 represents a highly complex pattern. This corresponded to a high-pitch buzz produced by capacitive coupling between heater wiring and a low-level grid circuit. The pattern shows evidence of both 50 and 100-cycle components, but freely decorated with high order harmonics, representing the "buzz" component.

Figure 4 shows the hum voltage measured across the first filter condenser of an old 4/5 valve superhet—one which happened to be on the bench when the patterns were being examined. The internal sweep was set to produce three waves on the screen but the flicker was unpleasant for continuous viewing.

Figure 5 shows the same hum voltage plotted against a 50-cycle

(Continued on Page 99)



Figure 7. The ripple voltage across the second filter condenser with horizontal amplifier gain set at maximum. Comparative measurement showed it to be equivalent to .04V. RMS.

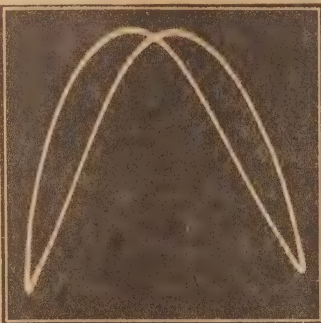


Figure 8. A pattern derived from the same point of the circuit, but with the first filter condenser disconnected. The value of the input condenser is immediately apparent.


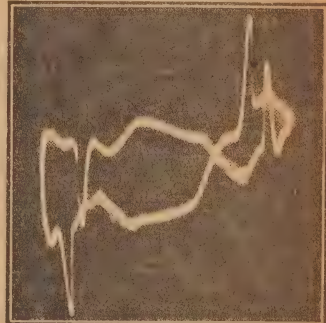


Figure 9. A highly complex pattern produced by the "buzzing" type of hum well known in high gain amplifiers. A basic 100-cycle pattern is evident in addition to the high order harmonics.

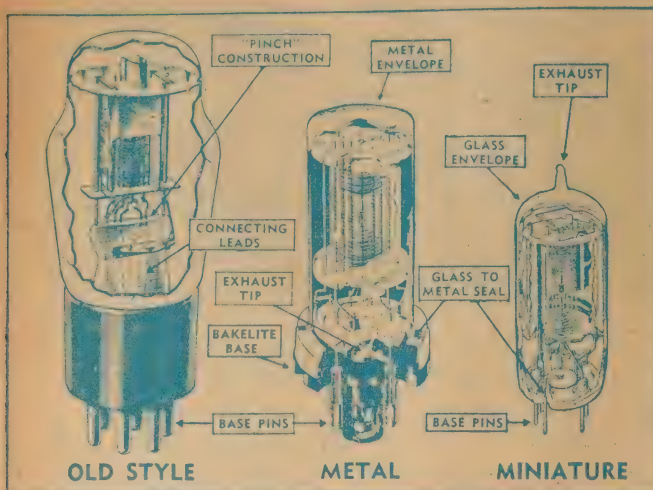



This diagram shows the mechanical evolution of the modern miniature valve.

turers managed to shorten the overall length to produce the "GT" series and so on.

However, through all these now familiar developments, the pinch construction was retained, basically because it remained the simplest method with available techniques and machines. Unfortunately, it has a number of fundamental limitations, which can readily be appreciated.

1. Electrode structures mounted on a pinch are supported along one plane only. To prevent the structure from sagging or vibrating sideways, elaborate support micas are necessary at the top, bearing against the glass bulb. Any looseness in the electrode support or mica produces mechanical rattles and microphony.

2. Cemented bases often come unstuck from the glass and the soldered lead wires do not take properly to the plated pins.

3. The length of lead trailing down inside the valve pinch and base is excessively long, between two and three inches in many cases. Capacitance between adjacent wires is too high and there are also dielectric

# NEW (RADIO) LAMPS FOR OLD

During the past few months, one new valve after another has been released on the local market. Special types are planned for local manufacture, while last month's issue carried details of a new batch of imported miniatures. Are these valves better than the older types? Are they as reliable? Can they be used in broadcast sets? Questions like these must have passed through the minds of many readers.

**T**O be sure, the number of valve types current in the world today is nothing short of stupendous. While local designers and enthusiasts may at times, have cursed the forces which denied them a particular valve, there is really something to be thankful for in the trade and tariff restrictions on the types with which we have to reckon.

## LONG LIST

Even so, the list is sufficiently long to fill an imposing manual and it is still growing, as witnessed by the recent announcements.

Some valve groups have been introduced, in the past, on rather flimsy grounds and proper planning on a world scale could have cut the number of different types to a fraction of their present total. The new miniatures, however, are the logical outcome of special requirements and completely new manufacturing techniques.

To understand the implications of this statement, it may be wise to trace briefly the developments and the factors which have changed valves from the big 4-pin lamps of the past decade to the present highly efficient miniatures.

One can quite understand the re-

action of engineers, in the early days, faced with the problem of producing the first commercial valves. Quite naturally, they turned to techniques and machines already in use for a closely related product—the familiar electric light globe. From this source they inherited what was commonly known as the "pinch" type construction.

This involves sealing a number of support wires in the flattened end of an inner glass tube—the pinch. Inside the envelope, the wires are trimmed and bent, then spot welded to the various support rods and leads from the electrode structure.

Underneath, other leads trailing from the support rods pass down into hollow pins set in a bakelite base. This base is cemented on to the glass envelope as the final step in manufacture.

## MASS PRODUCTION

Mass production cleaned up some of the obvious crudities of the earliest valves. Big, unlovely glass bulbs gave place to smaller and more becoming domed bulbs. The heterogeneous collection of bases, 4-5-6-7 pin, American, Continental and so on gave place to a more universal basing system, namely the octal. Manufac-

losses in the ordinary base material.

Objections 1 and 2 can be minimised by careful production control, but 3 remains as a source of electrical loss at frequencies beyond a few megacycles.


Engineers designing short-wave receivers find that too much of the L, C and R in their tuned circuits is concentrated inside the valve and socket, where it becomes a liability. Thus, ordinary types are fair enough to 15 Mc, poor to 30 Mc, and becoming progressively more hopeless after that.

## METAL VALVES

Appreciation of these problems led to the development of metal valves, as a partial answer. Though many of these are designedly interchangeable with glass equivalents, they employ a new construction principle, as will be evident from the illustration.

The pinch is replaced by a ring of individual glass bead seals, each one carrying a support wire which passes straight down into the base pin. The leads are shorter and careful positioning minimises troublesome capacitance effects.

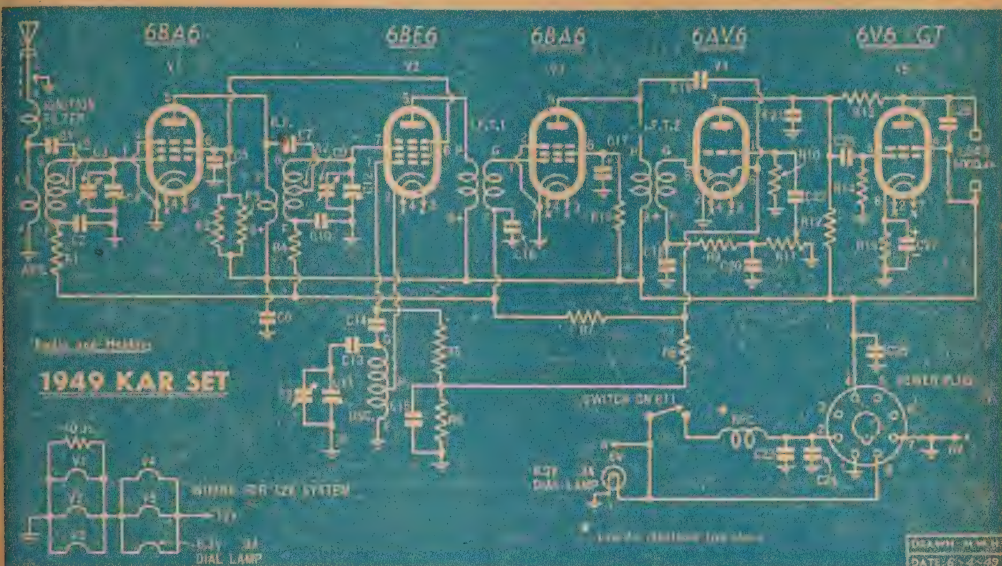Inside the valve, the ring wires give better support to the electrode structure.



Our popular car radio is a good example of how to use new valves. Older types could have been 6U7, 6A8, 6U7, 6BE and 42.

A significant development from the metal valve and its base was the American 8-pin "Loktal" and the European 9-pin equivalent, as used on the well-known EF50.

In these valves the support wires themselves become the contact pins, thereby eliminating the mechanical problems and losses associated with a bakelite base. The base on the Loktal series is purely a metal shell which supports a centre locating spigot.

To produce the present miniatures, designers succeeded in accommodating an equivalent electrode structure inside a much smaller glass envelope and the whole is sufficiently light to obviate the need for any form of artificial base. The wires supporting the electrodes simply protrude straight through the bottom of the envelope and plug into the socket.

## MINIATURE BASES

There are two standard miniature bases. The first a 7-pin "button" base, best known to date by its use in the miniature 1.4 volt battery valves. However, it cannot properly accommodate double triodes, converters and other complex types needing more than seven connections.

The alternative is the 9-pin "noval" base, best known in this country because of its adoption by the Philips organisation for their "Innoval" series.

Neither base is radically new, the 7-pin button type having been used for special VHF valves like the "900—" series. The "new" aspect is their application to mass production for valves of all kinds, whether required for VHF work or not. There are miniature rectifiers,

for example, miniature voltage regulators and miniature output valves.

Several important factors have brought this about, the most important having already been mentioned—the need for better performance on high frequencies.

The new miniatures greatly reduce lead length and capacitance inside the valve, thereby allowing the provision of more efficient tuning circuits at high frequencies. Basing losses are eliminated and there is a general tendency to reduce the electrode structure itself to smaller dimensions, giving a further boost to high frequency performance.

The average a-c miniature can be used successfully to 100 Mc. odd, while specially designed types more than double this figure.

However, quite apart from electrical characteristics, small valve dimensions are important in most VHF equipment, notably pack sets, mobile radio of all kinds, radar, FM and television. In some cases, the need for portability is obvious. In others, the problem is one of packing a necessarily large number of valves and circuits into a chassis of reasonable dimensions.

All this has a very important bearing on future operations, but how does it affect the designer of an ordinary domestic receiver?

## MANTEL SETS

If the set in question happens to be a mantel job, the answer is obvious. The use of smaller valves makes possible a more compact layout. Or, if smaller overall dimensions are not the object, a cleaner and less crowded layout can be effected.

For console receivers it is pretty much of a toss-up. The new miniatures provide something of a talk-

ing point in themselves but, by way of contrast, a miniaturised chassis in a large console can look very insignificant to the uninformed purchaser.

However, the desire to standardise types will probably lead to the ultimate and general use of miniatures for all sets, though many will stick to the well-known "GT" types for the time being.

The same trend will doubtless be evident in our own circuits—a gradual change-over to the miniatures of one type or another.

This will pose some problems for the home constructor. You will have to learn to handle the new sockets, to make cleaner, smaller soldered joints, using less flux. You will have to sort out in your minds the new pin arrangements and get away from the "heater to pins 2 & 7" complex. Reliance will have to be placed in basing diagrams, for the pin connections are likely to vary quite a deal, according to the requirements of the type.

## NEW CONNECTIONS

A few years ago, readers felt the same way about the then new octal base. The lugs looked smaller and dangerously close together. We had to retin the iron tip and clean up soldering methods. We dearly missed the two thick pins for the heaters.

It's just the same story over again and, after the first few experiences, home-builders will handle the new sockets and connections with the same familiarity as the old.

Another problem, of course, concerns the interchangeability of types. Can circuits using the new valves be built up around some of the older types which readers will certainly have on hand?



# UCC

# INFORMATION BULLETIN

## MICADISCS


This type of "Micadisc," a smaller version of the larger transmitting types, is designed especially for radio receiver application.

They are of stacked foil construction, contained in a circular-plated brass case. The case is provided with three lugs so that the capacitor may be mounted directly on the chassis, the lugs bent over and soldered. The other terminal is formed by a tag-eyelet at the centre of the disc through which a lead may be passed, soldered and continued on if desired, as depicted in the illustration at left.

Due to the peculiar construction, the current enters and leaves the capacitor radially. With the method of mounting, this achieves in effect a capacitor bush with extremely low inductance and operational characteristics to better than 200 Mc/s, which is ideally suited for bypass and decoupling functions in television and other U.H.F. applications.



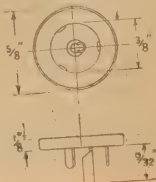Standard capacity values: 200, 300, 500 pF.  
Capacity tolerance:  
(a)  $-0 + 50\%$   
(b)  $\pm 20\%$   
Working voltage: 350 at 71°C.  
Test voltage: 1000 D.C.



## UNITED CAPACITOR CO. PTY. LIMITED

53 CARRINGTON RD., MARRICKVILLE, NEW SOUTH WALES.  
POSTAL: Box 49, Marrickville.

PHONE: LL 3211.



Associated with Tecnico Limited of Australia and Telegraph Condenser Co. Ltd., British Insulated Callender's Cables Ltd. and United Insulator Co. Ltd. of England

65/HP3

## "The YORK"

4 VALVE BROADCAST MANTEL

## KIT SET

### "The York" features:

Attractive Bakelite Cabinet (as illustrated); size 10 $\frac{1}{2}$ " x 6 $\frac{1}{2}$ " x 6 $\frac{1}{2}$ ". Also available in cream.

Rola 5 inch speaker.  
R.C.S. Intermediates.

Valves, 6J8G, 6G8G, 6V6GT, 6X5GT.

Full vision Dial.

A proved circuit with full instructions, easy to follow.



Complete to the last nut and bolt, including valves.

### Price

**£15/19/-**  
**retail**

Attractive Discounts to the Trade.

Build your own Radio Set and save pounds.



**BLOCH & GERBER LTD.**

WITH WHICH IS ASSOCIATED

**THE WELDON ELECTRIC SUPPLY CO.**

40-48 YORK STREET, SYDNEY

TELEGRAMS: "LESAB" SYDNEY

0X4221 (110 LINES)

Also supplied as a Foundation Kit Set—a boon to the small manufacturer. Prices on Application.

Years ago, when we began to specify the 6.3 volt valves, a goodly proportion of the circuits were actually built up by readers using the older 2.5 volt types. In the same way, there was a lag between the conventional types and the octal-based equivalents, when these latter became standard.

With some limitations, the same interchanges can be effected between the miniatures and the full-sized types.

One such limitation is purely mechanical, in that more chassis space is required by the larger valves and it will not be possible to duplicate compact layout arrangements. The other point is that the larger valves are virtually useless beyond about 30 Mc. and tuning circuits for operation on these frequencies or above rely entirely on the use of suitable types.

## MINIATURE GROUPING

Apart from these special features, the miniature valves can be grouped into the same classes as the older types. You can take your pick of two converter valves, the 7-pin 6BE6 or the 9-pin 6AN7. If a variable-mu R.F. pentode is required, there is the 7-pin 6BA6 or the 9-pin 6BD7, the latter having two diode plates incorporated for multiple-purpose operation.

For the audio end there is the 7-pin 6AV6 duo-diode triode, or the 9-pin type 6BD7. The 6AU6 is available as a pentode voltage amplifier, while there are two output valves to choose from, the 7-pin 6AQ5 and the 9-pin 6M5.

To make you feel more at home, the 6AQ5 has similar characteristics to the 6V6-GT, while the 6M5 is equivalent to the EL3-NG. Similarly, the miniature 6X4 rectifier is equivalent to the well-known 6X5-GT.

One could mention still other types which are either available immediately for commercial use or approaching release. Details of these types are best culled from published charts, as the need arises. After all, there are so many type numbers to be reckoned with that no one can be expected to remember them all, let alone details of socket connections and operating characteristics.

The main point, it seems, is to realise that these are just ordinary valves, more versatile perhaps, reduced in size but along familiar lines for all that.

## FIRST VARIABLE-MU

To underline the development, you may remember the first variable-mu R.F. amplifier—leastwise the first to be used in this country on a large scale. Who will forget the famous old '35?

In the process of time, the 35, with its transconductance of 1050, gave place to the sleeker 58 and a transconductance of 1600. Then came to us the 6B6, a 6.3 volt version of the same valve, followed by the 6U7-G with its octal base. About the same time, we were greeted by the metal 6K7 and its glass equivalents, all with much the same characteristics as the 6U7-G.

## "R. & H." GUIDE TO POPULAR A-C VALVE EQUIVALENTS

CLASS OF VALVE	OLD STYLE 2.5V.	OLD STYLE 6.3V.	OCTAL-BASED EQUIVALENTS	METAL VALVES	"GT" & SINGLE-ENDED TYPES	MINIATURE TYPES
DIODES	—	—	—	6H6	6H6-GT	6AL5
TRIODES	27, 54	37, 74	6C5-G, 6J5-G	6C5, 6J5	6SJ7-GT (Triode Conn.)	6CA, 6R4*, 6Q4*
TWIN TRIODES	53	6A6	6N7-G, 6C8-G	6N7	6SN7-GT	6J6*, 12AT7*, 12AU7, 12AX7
DIODE-TRIODES	2A6, 55	75, 85	686-G, 6Q7-G 6R7-G, EBC3	6Q7, 6SQ7	6SQ7-GT	6AV6, 6BD7 6N9 (Triode Conn.)
DIODE-R.F. PENTODES	287	687, 687S	688-G, 688-G EBF2, EBF32	688, 6SF7	6AR7-GT	6N8
VARIABLE-MU R.F. PENTODES	35, 58	6D6, 78 39	6K7-G, 6U7-G	6K7, 6SK7	6K7-GT, 6SK7-GT	6BA6, W77
SHARP CUT-OFF PENTODES	24, 57	6C6, 77 36, 1603	6J7-G	6J7, 6SJ7	6SJ7-GT	6AU6, 6AM6*, Z77*, EF91*
POWER OUTPUT VALVES	45, 47, 59 2A3, 2A5	42, 41 6A3	6F6-G, 6L6-G 6V6-G, K161, EL3 EBL1, 6K6-G	6F6, 6L6, 6V6	6V6-GT	6AQ5, 6M5 6AM5
FREQUENCY CHANGERS	2A7	6A7	6AR-G, 6K8-G, 6J8-G, X61M, ECH35, EK2	6AR, 6K8 6SA7	6SA7-GT	6BE6, 6AN7
RECTIFIERS	80, 523, 83V, 83	—	5Y3-G, 5V4-G, 5U2, 5U4-G, 5R4-GY	5Z4, 6X5	5Y3-GT, 6X5-GT	6X4

\* For future V.H.F. applications.

Last but not least in this line came the metal 6SK7 and its glass equivalent 6SK7-GT, with slightly "hotted up" characteristics and a transconductance of just over 2000. This is the valve designers would use who do not want to go over to the smaller valves.

But coming to the miniature series, we find the 6BA6 with a transconductance of over 4000 for much the same figures of plate and screen current.

In this respect the 6BA6 reflects a general trend in the design of these miniatures, namely, higher transconductance for the same orders of plate current. This is an essential feature of any valve which is to give good stage gain at high frequencies and this need, coupled with improved manufacturing techniques, account for the unusually high figures of transconductance.

## INCREASED GAIN

It follows that this increased gain will be evident when the same valves are used for normal broadcast work. As such, it is not particularly important, since it is possible to obtain plenty of gain anyway from low frequency circuits. The problem is rather to avoid trouble with instability due to excessive gain!

In the "Karsat," there was no such trouble but the remaining components were also miniatures designed for the purpose. Furthermore, the operating voltages were deliberately restricted in the interests of economy.

However, the set-builder who puts a 6BA6 in the R.F. and I.F. stages of an ordinary superhet, with high gain coils and I.F. transformers, should not be surprised if it oscillates from the word "go." Much will depend on the details of layout, &c., but there is a limit to which valve gain can be taken with ordinary components.

The same objection does not apply to converters and audio stages, of course, or at least not to the same extent.

We have not, as yet, had reason to combine the miniature high-slope types with familiar components and it is impossible to be more specific. However, when such designs do appear, you may expect to see gain deliberately cut back for low frequency work or, alternatively, a warning that "medium gain transformers must be used in this circuit."

Thus far, we have concentrated on types which are now readily available in this country and designed to meet immediate needs for mantel receivers, mobile radio-telephones, radar I.F. channels, and so on. These same valves will be cheap enough and plentiful enough to use also in conventional console receivers, along the lines already indicated.

The problems of television receiver design, however, have produced a variety of other types, some of which have been imported for local use on a restricted scale. Some of these were mentioned in the last issue.

There is the 12AT7, for example, a 9-pin miniature twin-triode, which can be used at frequencies up to 300 odd Mc. It will serve as a cascade R.F. amplifier or as a mixer/oscillator. Other twin triodes are intended for cascade or separate stage operation, allowing one tube to substitute for two. There are miniature voltage regulators, miniature high-performance R.F. pentodes, and so on. The enthusiast, at this stage, needs only to be aware of trends in this direction, because the day of the television receiver is still well removed from the present.

## VHF VALVES

In the meantime, amateurs and their associates will welcome the opportunity to purchase VHF valves at moderate prices for use on their 144- and 288 Mc. bands.

Some may be wondering, too, about the battery valves, which were really the first miniatures to make an impact on the local market.

They are miniatures, in the sense (Continued on Page 95)



# STANDARD FERGUSON RANGE

## POWER & VIBRATOR TRANSFORMERS

A.C. Vibs.				Retail
Code No.	Prim.	HTV	M.A.	Filaments
PF 122 240	12250 40	6.3V @ 2A		33/6
PF 125 240	61250 60	6.3V @ 2A		43/-
PF 119 240	6125125	6.3V @ 4A		62/-
PF 182 240	12200 40	12.6V CT @ 1A		33/6
PF 126 240	12250 60	12.6V CT @ 1A		47/6
PF 146 200,30,40	12 325 150	12.6V CT @ 2.5A		67/-

## FILTER CHOKES

Induct D.C. M.A.				Retail
Code No.	Prim.	HTV	M.A.	Filaments
CF 100 100 Res.	10			18/-
CF 101 30 870 25				18/-
CF 102 15 300 60				12/-
CF 103 30 420 80				26/-
CF 104 30 580 75				31/-
CF 105 15 250 80				24/-
CF 106 12 200 100				24/8
CF 107 30 360 100				34/8
CF 108 12 135 150				38/-
CF 109 20 225 150				43/8
CF 110 12 100 200				45/10
CF 111 16 165 200				46/2
CF 112 10 70 250				

## SPECIAL CHOKES

Code No.	Prim.	HTV	M.A.	Filaments
CF 113 .5 70 250				50/6
CF 114 1.1 23 375				24/-
CF 115 .017 .6 12 amps				10/-

## OUTPUT TRANSFORMER TO VOICE COIL

Full Frequency Range (30-15000)				Retail
Code No.	Prim.	HTV	M.A.	Filaments
OP24	5000 SE	8.4, 2.1, with feed		44/10
OP23	3250 SE	12.5, 8.4, 2.1		65/1
OP19A	5000 PP	12.5, 8.4, 2.3		102/10
OP31	4500 PP	15.5, 12.5, 8.6, 2.8, 2		36/9
OP63	10000 PP	15, 3.75		100/-
OP64	10000 PP	12.5, 8.4, 2.1		100/-
OP65	10000 PP	8.4, 2.1		100/-

## OUTPUT TRANSFORMER TO VOICE COIL

Special Full Frequency (20-30,000)				Retail
Code No.	Prim.	HTV	M.A.	Filaments
OP25/40	10000 PP	40, 10		130/-
OP25/16	10000 PP	16, 4		130/-
OP25/15	10000 PP	15, 3.75		130/-
OP25/12	10000 PP	12, 3		130/-
OP25/10	10000 PP	10, 2.5		130/-
OP25/8.4	10000 PP	8.4, 2.1		130/-
OP66	5000 PP	8.4, 3.7		130/-
OP67	5000 PP	15, 6.5		130/-

## OUTPUT TRANSFORMER TO LINE—

Full Freq. Range.				Retail
Code No.	Prim.	HTV	M.A.	Filaments
OP22	3250 SE	1500, 255, 8.3		65/1
OP19b	5000 PP	500, 250, 125		102/10
OP21	8000 PP	500, 250, 125		82/10
OP62	10000 PP	500, 125		100/-

## OUTPUT TRANSFORMER TO LINE—

Special Full Freq. Range				Retail
Code No.	Prim.	HTV	M.A.	Filaments
OP25/500	10000 PP	500, 125		130/-
OP25/250	10000 PP	250, 62.5		130/-

## VIBRATOR TRANSFORMERS

Code No.	Prim.	HTV	M.A.	Filaments
VT 100	32200	40 .005	Sync.	27/-
VT 101	6 90	15 .008	"	19/6
VT 102	6150	25 .005	"	23/10
VT 103	6250	50 .005	"	25/-
VT 104	6250	60 .005	"	25/-
VT 105	12250	60 .005	"	37/-
VT 106	6300	75 .008	"	37/-
VT 107	6250	60 .005	Sync. Low Rad.	30/6
VT 108	12 90	15 .008	Sync.	21/8
VT 109	24 30	15 .008	"	21/8
VT 110	12150	25 .005	"	23/8
VT 111	24150	25 .005	"	23/10
VT 112	12200	50 .005	"	26/6
VT 113	24200	50 .005	"	26/8
VT 114	12300	75 .008	"	54/2
VT 115	24300	75 .008	"	55/6
VT 116	24250	60 .005	"	30/-
VT 117	12250	60 .005	Non Sync. Low Rad.	31/-
VT 119	32150	25 .005	Sync.	25/6
VT 121	6180	30 .005	"	25/4
VT 122	6400	50 .005	"	20/-
VT 123	12320	125 .005	Sync.	83/3
VT 124	32250	60 .005	"	30/-
VT 127	6200	50 .005	Sync. Low Rad.	29/8
VT 128	12250	60 .005	Sync. Low Rad.	38/-

## RECEIVER POWER TRANSFORMERS

Code No.	Prim.	HTV	M.A.	Filaments	Retail
PF 185	240	150	506.3V @ 2A		24/-
PF 106	240	325	45.6.3V @ 2A, 5V @ 2A		30/-
PF 198	240	285	50.6.3V @ 2A, 5V @ 2A		30/-
PF 151	200,30,40	285	60.6.3V @ 2A, 5V @ 2A		34/-
PF 165	200,30,40	385	60.6.3V @ 2A, 5V @ 2A		34/-
PF 170	200,30,40	285	80.6.3V @ 2A, 6.3V @ 2A, 5V @ 2A		39/10
PF 168	200,30,40	385	80.6.3V @ 2A, 6.3V @ 2A, 5V @ 2A		39/10
PF 130	200,30,40	285	100.6.3V @ 2A, 6.3V @ 2A, 5V @ 2A		46/-
PF 160	200,20,40	385	100.6.3V @ 2A, 6.3V @ 2A, 5V @ 2A		46/-
PF 152	200,30,40	285	125.6.3V @ 3A, 6.3V @ 3A, 5V @ 2A		56/-
PF 181	200,30,40	385	125.6.3V @ 3A, 6.3V @ 3A, 5V @ 2A		66/-
PF 174	200,30,40	285	150.6.3V @ 2A, 6.3V @ 2A, 5V @ 2A		60/-
PF 175	200,30,40	385	150.6.3V @ 2A, 6.3V @ 2A, 5V @ 2A		70/-
PF 173	200,30,40	425	175.6.3V @ 3A, 6.3V @ 3A, 5V @ 3A		110/-
PF 140	200,30,40	385	200.6.3V @ 2A, 6.3V @ 2A, 5V @ 3A		111/-
PF 171	200,30,40	385	250.6.3V @ 4A, 6.3 @ 3A, 5V @ 3A		144/-
PF 201240		225	5016.3 @ 2A		29/11

## LINE TO VOICE COIL TRANSFORMERS

Code No.	Prim.	HTV	M.A.	Filaments	Retail
MT111	500		12.5, 8, 2.3	10	36/9
MT100	500		4, 3	15	36/9
MT101	500		15, 15	15	36/9
MT124	500, 500		4, 3, 2.7, 2.3, 2	23	66/-
MT125	500, 500		15, 12.5, 8.4, 6.5	25	66/-

## MODULATION TRANSFORMERS

Code No.	Prim.	HTV	M.A.	Filaments	Retail
MT118	8000, 6000 PP		10000, 7000	25	85/-
MT119	8000, 6000, 3800 PP		5000, 10000, 7500, 6500	50	111/-
MT120	500 to 20000 in steps.		5500, 4500, 3500	50	200/-
MT121	500 to 20000 in steps.		500 to 30000 in steps.	125	276/-

## Output Transformer To Voice Coil—P.A. Range

Code No.	Prim.	HTV	M.A.	Filaments	Retail
OP1	5000, 2500 SE		12.5, 8, 2.3	10	39/10
OP54	5000, 2500 SE		15, 12.5, 8.4, 6.5, 4, 3, 2.7, 2.3, 2	10	45/8
OP39	5000, 2500 SE		15	10	39/10
OP33	5000, 2500 SE		5, 2.7	10	39/10
OP41	5500 SE		3.7	10	46/-
OP35	30000, 20000		2.7	10	36/9
OP2	5000 PP		12.5, 8, 2.3	15	65/1
OP55	5000 PP		15, 12.5, 8.4, 6.5, 4, 3, 2.7, 2.3, 2	15	73/10
OP3	6600 PP		12.5, 8, 2.3	15	65/1
OP56	6600 PP		15, 12.5, 8.4, 6.5, 4, 3, 2.7, 2.3, 2	15	73/10
OP4	10000 PP		12.5, 8, 2.3	15	65/1
OP57	10000 PP		15, 12.5, 8.4, 6.5, 4, 3, 2.7, 2.3, 2	15	73/10
OP5	10000, 6600, 5000 PP		12.5, 8, 2.3	15	65/1
OP58	10000, 6600, 5000 PP		15, 12.5, 8.4, 6.5, 4, 3, 2.7, 2.3, 2	15	76/2
OP59	10000, 6600, 5000 PP		15, 12.5, 8.4, 6.5, 4, 3, 2.7, 2.3, 2	25	93/8
OP60	10000, 6600, 5000 PP		15, 12.5, 8.4, 6.5, 4, 3, 2.7, 2.3, 2	32	116/8

## OUTPUT TRANSFORMER TO LINE—P.A. Range

Code No.	Prim.	HTV	M.A.	Filaments	Retail
OP1A	5000, 2500 SE		500	10	39/10
OP44	5000, 2500 PP		500, 250, 125	10	47/-
OP34	5000 PP		600, 300, 200, 150, 130, 100	15	81/4
OP6	5000 PP		75, 50	13	65/1
OP7	6600 PP		500, 250, 125	15	65/1
OP80	3000 PP		500, 250, 125	15	126/-
OP8	10000 PP		600, 300, 120, 60, 30	15	65/1
OP8M	10000 PP		500, 250, 125	15	71/3
OP9	10000, 6600, 5000 PP		500, 250, 125, 100, 83.5	15	65/1
OP10	5000 PP		71.5, 62.5, 55.5, 50	25	81/10
OP11	6600 PP		500, 250, 125	25	81/10
OP38	6600 PP		500, 250, 125	25	102/10
OP12	10000 PP		600, 300, 250, 200, 170, 150	23	140/-
OP13	10000, 6600, 5000 PP		76, 50, 36, 27, 12.5, 7.5, 3.6	25	81/10
OP33	10000, 6600 PP		500, 250, 125	25	81/10
OP14	5000 PP		500, 4000, 8.4, 2.2	32	102/10
OP48	6600 PP		500, 250, 125	32	102/10
OP15	6600 PP		140, 70	32	102/10
OP13M	6600 PP		500, 250, 125	32	102/10
OP16	10000 PP		500, 250, 125	32	102/10
OP17	10000, 6600, 5000 PP		83.5, 71.5, 62.5, 55.5, 50	32	104/1
OP18	3800 PP		500, 250, 125	32	102/10
OP13	3800 PP		500, 250, 125	60	108/7
OP37	6400 PP		100, 75, 25, 10, 5, 3	60	108/7
OP49	8800, 6000 PP		500, 250, 125	60	133/8
OP20	11600, 8400 PP		500, 250, 125	105	210/-

ALL PRICES SUBJECT TO ALTERATION WITHOUT NOTICE.

# A COURSE IN TELEVISION

## PAST 16—VIDEO AMPLIFIERS

Continuing the discussion of video amplifiers, the purpose of this article is to examine the factors which limit high frequency response and suggest measures by which the response can be extended. The same provisions can be applied to oscilloscopes and other test equipment where extremely wide range amplification is required.

As we have already pointed out, the video amplifiers in a television system must be capable of providing even gain over a range of frequencies extending from a few cycles per second to several megacycles. The top limit depends initially on the standards of the system, ranging from about 2.5 Mc. for medium definition systems to about 5 Mc. for the proposed Australian system.

### PICTURE TUBES

A practical limit, however, is set by the quality of the picture tube. In small, inexpensive receivers the trend is often to design both the IF and the video channel for increased stage gain and reduced bandwidth on the assumption that the resultant loss of detail will not be apparent on a small screen.

This assumption does allow certain compromises to be made on occasions but, for more ambitious receivers, the theoretical requirements must be more nearly satisfied.

The limitations on the high frequency response of a resistance-coupled amplifier are set by capacitances which are "accidental" in the sense that they never appear on the circuit diagram. However, there is nothing imaginary about their effect on results.

Figure 1a is a traditional schematic circuit in which some of these shunt capacitances are shown dotted.


### GRID-GROUND CAPACITANCE

Referring first to the grid circuit, there is inevitably some capacitance directly between grid and ground, due to the proximity of wiring and components to the chassis. Some capacitance is contributed also by the signal source, whether it be another video amplifier or the filtered output from a detector.

Of this, no more can be said, save to stress the importance of arranging the layout and circuitry to minimise length of leads and stray capacitance effects.

Additional shunt capacitance exists within the valve itself, from the control grid to the cathode on one side and to the screen on the other. It remains a constant problem for valve designers to produce valves with close electrode spacing in the interests of efficiency, while trying at the same time to reduce the extra capacitance which close spacing between electrodes tends to produce.

By way of example, the 6AC7, one

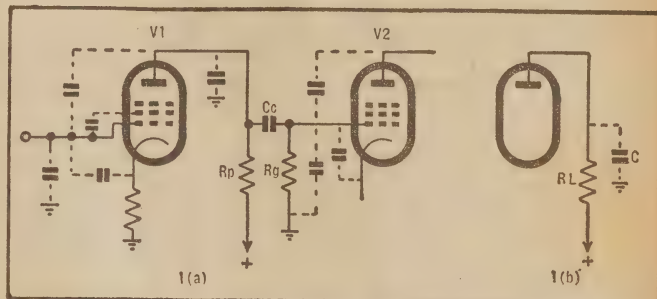

Showing effective capacities existing in a video amplifier.

of the older television pentodes, exhibits a total input capacitance of 11 pf.—this being additional to capacitive effects in the wiring and socket.


The condenser shown dotted between the grid and plate is significant as the source of the so-called "Miller Effect" in amplifier tubes.

Without elaborating on the subject at this stage, it can be shown that an amplifier with resistive plate load acquires an input capacitance which is equal to the total grid-plate capacitance multiplied by the stage gain plus one. In other words:

$C_{in} = C_{g-p} (M+1)$ , where  $M$  is the stage gain figure.
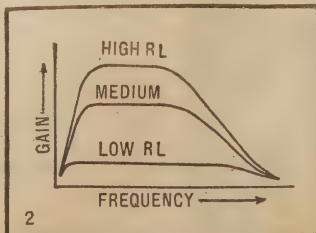
### MILLER EFFECT

Miller Effect makes triode valves rather unattractive for video work, because their grid-plate capacitance figures are necessarily a great deal higher than for pentodes. With pentodes the internal grid-plate capacitance can usually be kept small enough to render Miller Effect unimportant.



Effect of load resistance on gain and frequency response.

Coming to the plate circuit, the output capacitance of the valve itself will amount to several pf., to which must be added the inevitable capacitance to ground of the wiring and components.

This is virtually in parallel with the input capacitance to the following stage, which may duplicate the characteristics of the preceding valve.

The effect of all these capacitance values on high frequency gain is related directly to the effective impedance of the circuit across which they are connected. Thus, loss of gain in a high impedance circuit is greater than in a low impedance circuit.

The impedance of the coupling circuit in Figure 1a, between V1 and V2, is largely set by the parallel resistance of  $R_p$  and  $R_g$ . In practice, it is usual to make  $R_p$  much lower in value than  $R_g$ , both to ensure a reasonable plate voltage for V1 and also to set up a favorable a-c to d-c load ratio. In most cases  $R_g$  is so much greater than  $R_p$  that its effect on the net impedance can be ignored.

### SIMPLIFIED CIRCUIT

This being so, the problem of interstage video coupling can be simplified to figure 1b, in which the load  $R_L$  determines the circuit impedance and  $C$  is the total shunt capacitance to ground. Coupling circuits from the detector and into the picture tube can be treated on the same basis.

For purposes of reference it is usually considered that an amplifier is flat between points which are 3db. down in relation to what can be termed the "middle frequency" response.



Your 1950

# PENTAGRID 4

will operate better with—


## R.C.S. components

This fine little battery 4-valver, building directions of which are contained elsewhere in this issue, will naturally give its best performance with the very latest developments in quality components—and naturally enough they will be R.C.S. components. Obtain a price list of all R.C.S. components from your local radio retailer or write direct to R.C.S. Radio Pty. Ltd. This comprehensive price list will show you how to get peak performance from your Pentagrid 4 and at the same time save money on your overall building costs.


### OTHER R.C.S. COMPONENTS INCLUDE—



Audio transformer.

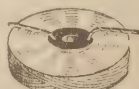

Radio frequency choke.

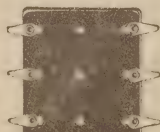


Connector strips.



Low loss coil laquer.
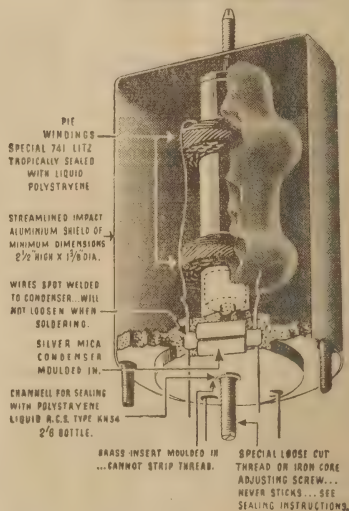
### Cross section of R.C.S. intermediate transformer



If you are unable to obtain R.C.S. components from your local dealer, write us for a copy of our price list and we will arrange for your dealer to obtain supplies of R.C.S. components immediately.

**R.C.S.**  
RADIO PTY. LTD.

174 Canterbury Road,  
Canterbury, N.S.W.

It must be remembered, however, that all such losses are accumulative and that a 3db. loss at a given frequency in each of three stages adds up to a total of 9db. Accumulative effects are particularly troublesome in the original programme and transmitting circuits, where the signal has often to pass through a variety of shapers, channels, mixers, faders and so on, before final application to the transmitter.

Referring to a single network (as figure 1b) it can be shown that the response will be down by 3db. at the frequency where the capacitive shunt reactance is equal to the load resistance.

It might be assumed that the total shunt value of "C" is about 40 pF. At 5 Mc. this represents a reactance of less than 1000 ohms, which simply means that RL must be of the same order to give a "flat" response to 5 Mc. If the accumulative effect is to be taken into consideration, the load value would have to be even less.

### EFFECT OF LOAD

The effect of load resistance on gain and frequency response can be illustrated as in Figure 2.

With high values of load, as used for audio work, the frequency response is confined to a relatively narrow band, but the gain is high.

A progressive reduction in the load value widens the response but reduces the gain. Unless pains are taken to choose the right class of valve and to minimise the shunt capacitive losses, the gain can deteriorate to less than unity before the desired bandwidth is achieved.

As an approximation, the gain of a pentode amplifier stage is equal to the product of transconductance and load resistance, the one being in amps per volt, the other in ohms. By way of example, the gain of the familiar 6J7-G with, say, an 800 ohm load, would be:

$$\begin{aligned} M &= G_m \cdot R_L \\ &= 1.225 \times 800 / 1000. \\ &= 1 \text{ (approx.)} \end{aligned}$$

The futility of providing amplifier stages with unity gain is obvious.


Since there is a practical limit below which "C" cannot be reduced, there is also a practical upper limit for RL. Therefore, reasonable stage gain can only be obtained by using valves with specially high figures of transconductance.

### THE 6AC7

The 6AC7 mentioned earlier comes into this class with a transconductance of approximately 9 mA./V. Assuming the same order of load, the stage gain rises to just over 7 times. Even this is low, of course, compared with the 100 to 200 times gain expected from pentode valves in audio equipment.

Referring generally to video pentodes, it is usual for types having high transconductance to show some increase in output and input capacitance. Too steep a rise in these latter values can necessitate a reduction in plate load and cancel some of the advantage gained by the high transconductance.

Thus, a rough "figure of merit"

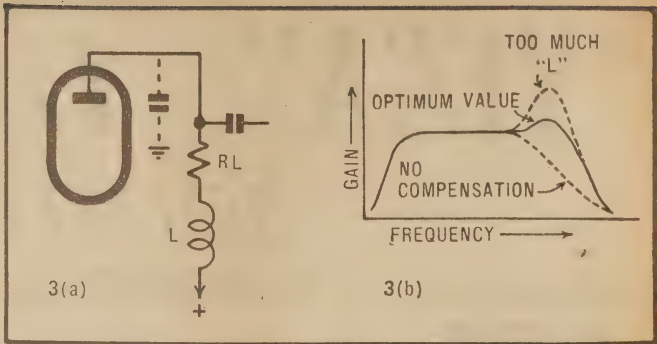

Effect of added series inductance in the plate load on frequency response.

emerges for video amplifier valves based on the ratio of transconductance to inter-electrode capacitance. The relationship is not a simple one, of course, because the valve capacitance is only part of the whole. However, if two valves have the same order of transconductance, the one showing lower inter-electrode capacitances must have the advantage.

In the face of these problems, it has become common practice to employ methods of high frequency compensation, the simplest scheme being to include a small inductance in series with the plate load, as indicated in Figure 3. The inductance tends to resonate with the total "C" in the circuit in the region where the response would otherwise fall away.

### CRITICAL VALUE

The value is fairly critical and must be established for a particular set of conditions. If the inductance is too high, the resonant peak rises to a considerable amplitude, the effect being further heightened by any similar compensation in other stages.

Too little inductance gives poor compensation, the right amount just serving to square off the tapering high frequency characteristic without introducing a noticeable peak. The principle is illustrated in Figure 3.

As a guide to requirements in regard to the value of "L" a simple procedure is to plot the frequency response of an uncompensated stage

and then note the frequency at which it is 31b down. It can be assumed that the capacitance reactance is then equal to the plate load and, knowing these two values, it is possible to estimate the effective value of "C."

Another form of compensation is in the series-peaking toplift circuit, as illustrated in Figure 4. Its operation can be explained roughly as follows:


The presence of the inductance L virtually isolates the two valves and their attendant capacitances. Thus C1 in Figure 4a pertains only to the plate circuit and, for a given bandwidth, RL can be increased with a consequent increase in stage gain. The response in this section of the circuit could be illustrated by curve 1.

The output is fed to L and C2, which together should form a series circuit resonant at a point beyond the normal cut-off of RL.C1 (curve 2). The voltage across C2 is maximum at resonance so that the overall response is as illustrated by the solid curve 3.
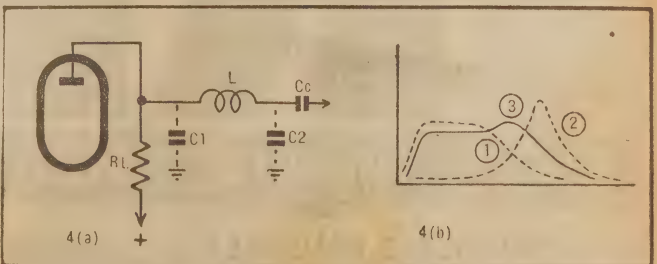
### GAIN IMPROVEMENT

In terms of gain a stage using shunt peaking may give an improvement of about 1.5 to 1 over an uncompensated stage for the same bandwidth. With series peaking the improvement in gain may approximate 2:1, while still higher ratios can be obtained with more complex methods of compensation combining shunt and series peaking.

Despite the improvement in gain offered the general tendency seems to be to avoid the more complex com-



The use of a series-peaking circuit on response.



# "VEGA" little wonders!



## Miniature I. F. TRANSFORMERS & COILS



ALL STAR  
PERFORMERS

(as used by leading Manufacturers)

Giant in performance — dwarf in size —  
"VEGA" miniature I.F.s give you the greatest  
GAIN in radio . . . RETAIL 13/9 ea.  
Miniature coils are also available. Aer. RF.  
OSC (Specify mixer tube) . . RETAIL 8/9 ea.

MINI CAR RADIO KIT (matched) 57/6  
AER, R.F., OSC, 2 IFT'S and "HASH" Coil

### IMPORTANT!

If your usual supplier is unable to supply your requirements of "VEGA" Products, enclose remittance —plus postage and order direct from our Mail Order Dept.

TRADE SUPPLIES: Usual discounts are available.—Prompt Delivery.

CRANCH PRODUCTS & TRADING CO.  
17 BOND STREET, SYDNEY

Phones: BU3879. BW7746  
Telegrams: "Cranlay" Sydney.

### MAIL THIS TODAY

Please place my name on your mailing list for free issues of "Vega" Technical and Data Sheets



NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
9 RH.

## AEGIS Leads in Coils and I.F.'s...

The only complete range of quality components including Coil Assemblies with and without R.F. stage, also the new KC4 four Band-Spread Kit.
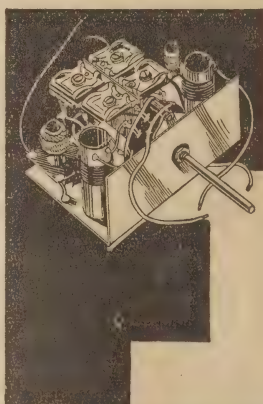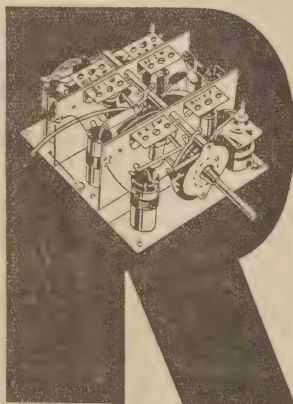
### ★ K2 KIT

R.F. Dual Wave Assembly. Permeability Iron cored both B/C and S/W Coils, 7-22 meg. S/W, 550-1600 KC B/C band. Special cadmium sub-chassis. A.W.A. Air Trimmers. Fixed Mica B/C and S/W Padders fitted. All assemblies pre-aligned on special tester before leaving factory. All coils treated with Trolital. A.V.C. resistors and condensers, de-coupling resistor in R.F. stage. Easy and comprehensive colour - code and aligning instruction sheet supplied.



### ★ K1 KIT

A dual-wave assembly incorporating permeability tuned Aerial and Osc. Coils for B/C (550-1600Kc) and S/W (7-23 Mc.) Trimmers and Padder (fixed) condensers fitted. Iron - Core adjustment is made from above chassis (Trimmers from beneath) —Suitable for "III & "A.W.A." Gang. Measurements: 2 1/2" long, 3 1/2" wide, 1 7/8" high. Available for converters 6J8, 6A8, ECH35, EK2, 1C6. "Oak" Type Switch built in with 3" long x 1" shaft.

## AEGIS MANUFACTURING COMPANY

208 LITTLE LONSDALE ST., MELBOURNE

Phone { Cent 4414  
Cent 3688

pensating networks in favor of simple shunt or series peaking. The additional components, under mass production, can easily produce undesired resonance characteristics, while the net gain is not always as great as might be expected at first glance.

The additional compensating components and the associated wiring itself involves greater capacitive losses, tending to cancel somewhat the advantages gained.

Attacking the problem along other lines, there remains the opportunity of obtaining some compensation from the cathode circuit.

It will be remembered from previous discussion that there is considerable difficulty in effectively bypassing the cathode of a video stage to earth while preserving its response to the lowest frequency component likely to be handled. In terms of repetition rate this may be 25 or 30 c/s but, since a particular color value may be sustained for the full duration of a line, the time constant of coupling and cathode circuits must be capable of handling a signal equivalent to a few cycles per second.

In view of the obvious difficulties of arranging a cathode bypass on this basis the tendency has been to omit the bypass altogether and to put up with the resultant loss of gain due to degeneration.

#### SMALL VALUE

However, the cathode can be bypassed with a deliberately small value such that the degeneration is removed at frequencies where the response elsewhere, due to capacitive losses, tends to fall away. In other words, the time constant of the cathode circuit is related to that of the output circuit.

By careful choice of component values the use of cathode compensa-

tion can often allow the plate load to be increased above what would otherwise be its optimum value, so that degenerative losses on the cathode circuit are partially offset.

Allowing for the various forms of compensation, video stages are commonly found with plate load values of from 1000 to 3000 ohms, depending largely on the exact bandwidth required.

Other possible forms of compensation include "loss" networks of the type commonly employed with gramophone pickups, with values proportioned to meet requirements. However, these are not widely used in practice by reason of their inherent insertion losses.

#### OUTPUT STAGE

The final remarks concern the last video stage, feeding the picture tube. In a small receiver this might well be the only video stage.

To fully modulate the electron beam of a picture tube a peak-to-peak signal voltage of between 20 and 40 may be required, depending on the sensitivity of the tube.

All the requirements for video amplifiers in general apply to the final stage, so that its load also may be only a couple of thousand ohms. It follows that, to develop a voltage of, say, 30 peak-to-peak across a load of this order requires a peak current swing of 15-odd milliamps. Since the valve should not work over the non-linear portion of its characteristic, it follows that the standing plate current of the final video amplifier must be substantially higher than one-half the peak-to-peak current for full modulation. What is often required, therefore, is a tube with characteristics similar to a moderate power tube but with good high frequency performance.

### An unsolicited letter

"Walton,"  
Elizabeth Street,  
Berala.

FN RADIO-TELEVISION CO.,  
265 Military Road,  
CREMORNE.

Dear Sirs,

The Williamson Amplifier built by you for me exceeds my expectations as far as performance is concerned.

With the speaker mounted on a 3' x 3' baffle board, the clarity and truth of reproduction is exceptional, absolutely everything on the record being reproduced naturally.

I have been a lover of good music for a long time and have hoped to own a means of bringing it into the home in undistorted form. My particular liking is for piano music and I find, contrary to my previous belief, that, as well as other forms of sound, can be played without any distortion on my amplifier.

In spite of the fact that my "not-so-modern" permag speaker is not mounted in a vented enclosure, the amplifier reproduces sound, to my children, at a frequency of 17,000 cycles (HMV ED1187).

Thanking you for your very good job.

I am,  
Yours faithfully,  
J. M. VICKERY.

The above "untouched" letter, is just one of the many similar letters taken from our files, and may be seen at our office at 265 MILITARY ROAD, CREMORNE.

FN RADIO-TELEVISION CO., is the only firm who is able to offer YOU, that **PERSONAL ATTENTION-SERVICE-SATISFACTION**. Why not consult them for all your **AMPLIFIER** requirements?

#### ANNOUNCING the "TELE-TAPE"

A high class professional type Magnetic Tape Recorder, combining every desired feature.

- Easy to operate.
- Low Noise.
- Low distortion.
- High Quality.
- Versatile.
- Durable.
- Portable.
- Smartly Designed.

For further particulars, contact us at our Head Office, CREMORNE.

#### ALSO NOW AVAILABLE

A complete library of programme on TAPE... giving you 30 minutes full uninterrupted recordings... These programmes are available immediately from stock, and may be heard at our Head Office in CREMORNE...

For EVERYTHING in RADIO  
**FN RADIO-TELEVISION**  
Pty. Ltd.

265 Military Road, CREMORNE,  
N.S.W. Phone: XY5063.  
Same Day Mail Order Service.

## HOW IT WORKS—MAKING PLASTICS

(Continued from Page 23)

the use of large fabricating machinery, as large pressures are used. The mould itself consists of two parts—one with a cavity in it representing the outside form of the article, and the other, a solid piece of steel, of which the outside represents the article's inside form. This inner part of the mould is slightly smaller than the mould of the outside, so that the space between represents the article itself. The thermoset moulding powder, mixed with some strengthening fillers, as required, is placed in the mould cavity. The press then rams the heated mould closed, fusing the powder to shape in a matter of minutes.

In practice, the moulding of plastic articles involves many delicate and intricate processes, and the apparently easy, straightforward way of making things of complicated shapes depends on very special machinery. The machines are automatic in their operation, or nearly so, and they incorporate many devices, such as an automatic measuring contrivance to dole out the amount of powder required in individual moulding processes.

In the production of some plastic

articles, metal parts for a variety of purposes—such as screws and bushes—can be incorporated in the moulded articles. The metal parts to be inserted can be securely anchored in the moulding and their position accurately controlled.

### HANDY DRILLING HINT

WHEN using a hand drill to bore holes in thin material such as hard metal or hard board, the sudden breaking through sometimes causes the chuck to mar the finish of the work. To prevent this, slip a rubber grommet over the bit before drilling. The grommet will provide a cushion between the bottom of the drill chuck and the surface of the material.

Naturally, this will call for a number of grommets of varying sizes suitable for the sizes of drills normally used. An alternative approach would be to cut a slit or pierce a small piece of an automobile inner tube. The one piece will then easily force on to most sizes of drill bits used in the average home workshop.





# Here's your answer, Tom!

Tom is worried by a question which faced most of us when we first took up radio as a hobby. He can understand signals being conveyed along a wire, but can't for the life of him see how they can be induced to travel through space. We'll do our best to explain. Whether we succeed or not is another matter.

**J**UST before proceeding to our role as paternal father, we must hang our paternal head in shame and confess to making a most elementary "blue" in a recent article.

A correspondent takes us to task for gibing at plumbers and points out that "spirits of salts" is not sulphuric acid. Most plumbers understand fluxes, he says, and know a lot more about soldering than the average radio enthusiast.

The answer to both comments is "quite true." Maybe we were

We'll start right at the beginning. You probably know that the electricity supply to your house is AC or alternating current. Leastwise that's what it is in most Australian homes.

By the term "alternating" we mean that the current flows back and forth, in this case at a rate corresponding to about 50 complete cycles each second.

If a small portion of the energy were fed to a loudspeaker instead of to the radiator, the speaker would emit a low-pitched humming sound, equivalent to a very low audible (or, "audio") note.

## NEED FOR WIRES

If we could persuade the lighting authority to step up the speed of the generator and therefore to increase the frequency of the alternations, the pitch of the sound in the speaker would gradually increase to a whine. Actually, by other means, it is possible to generate alternating current of a much higher frequency—in fact, so high that it passes beyond the range of our ears at about 15,000 cycles per second.

Alternating currents with frequencies of this order can travel only in wired circuits. In other words, if you want to convey speech or music impulses directly from one place to another, you must run wires between the two places. The Postmaster-General and his cohorts are the experts in this field of operations. They provide the wires and you provide the tuppences.

Therefore, when you use the phone your voice is changed into corresponding electrical impulses having frequency components running up to a few thousand cycles. These are fed along the wires, into your girlfriends' earphone and thence into her ear. They may or may not have the desired result, according to the effectiveness of your technique!

However, as a by-product of your amorous outpourings, some odd electrical effects are going on. As the minute electrical currents flow in the wire, they create minute magnetic fields around it and the fields build up and collapse again very rapidly—in fact, at the same rate as your voice impulses.

But here's the point, the magnetic lines of force build up around the

wire and collapse into it again, so that they are never apparent except in the immediate vicinity of the wire.

But, if by some cunning means, the frequency of the impulses in the wire is increased beyond the audible range and up to about 50,000 cycles per second and beyond, an entirely new set of circumstances comes about.

Just imagine an impulse travelling one way for a tiny fraction of a second. It builds up magnetic lines of force around the wire, which tend to collapse back into the wire when the impulse stops or changes its direction. But the lines don't collapse quickly enough and before the process is complete the impulse repeats its original cycle and generates new lines of force which push off the ones previously generated.

The process, in a way, is like a snake rapidly shedding its seasonal skins (if snakes actually do that). The wire continuously sheds lines of magnetic force which are pushed outward into space.

In other words, Tom, part of the energy in the wire is "radiated." By selecting the frequency of the impulses and making the wire a certain length (in other words "resonant"), it is possible to radiate quite a lot of energy into space.

Technically, the explanation may



thinking of the amateur plumbers we've seen in action in our time. And it's so long since we endured the regular "stinks" (i.e. chemistry) period in high school that a slight mental aberration is perhaps excusable.

In point of fact, "spirits of salts" is hydrochloric acid—the stuff, which froths and gives off choking fumes when applied to galvanised iron.

After all that, we can proceed with the first question:

## CARRIER WAVE

What really is a radio wave and what is a carrier wave? Is it a form of atmospheric conductor or something else? Also, how is it actually generated and received?

Well that's quite a question, Tom, and one that's going to require most of the page to dispose of. But let's heed the old saying . . . "Nothing attempted, nothing done" . . . or whatever it is.

We better take the question one part at a time.

First of all, what is a radio wave?



be rather loose but you have probably caught on to the idea. Radio waves are not just conductors in space, in the sense that you apparently visualised. Rather are they electromagnetic and electrostatic fields which are radiated through space from an aerial system.

At the other end, they can be intercepted by another aerial system fed to a receiver and amplified.

The big catch, of course, is that a

radio wave as such is useless. It cannot be heard, nor does it convey any sense to the listener in its original form.

The pioneers got over this by inserting a "key" in the transmitting system which interrupted the carrier according to a certain pattern of dots and dashes. Someone at the other end, knowing the significance of the dots and dashes, could read the code and translate it into words and figures. This is a very roundabout way of mentioning what we know as morse code.

But morse is a most uninteresting thing to listen to and engineers found a way to impress speech currents on a radio wave in such a way that they varied its character, just as positively as does the morse key. The process of impressing speech (or music) impulses on a radio wave is known as "modulation."

## RECEIVER FUNCTION

At the other end, it becomes the function of the radio receiver to pick up the radio wave, subtract the audible speech or music impulses and impress them on the loudspeaker or headphones.

We thus have a very happy mating of phenomena. Speech currents cannot be sent through the air, but they can be impressed on a much higher frequency "radio" wave. This latter can be made to travel through space, carrying the intelligence, and it is referred to commonly as the "carrier" wave.

Over and above that, there's a lot of extra theory. Speech and music impulses can be impressed on the carrier in various ways, giving rise to expressions like amplitude modulation, frequency modulation, pulse modulation and so on.

The radio waves can have a fairly low frequency, as for our normal broadcast stations, a much higher frequency, as for short-wave stations, or an extremely high frequency as used for F.M. stations, television, radio-telephone and so on. But, maybe you know all that.

The second part of your question reads like this:

## THE RADIO WAVE

How is it (the radio wave) generated and received?

In the days when radio was very young as a science, radio waves were generated by partially mechanical means. However, the systems were very elementary and cumbersome and have been superseded by those using valves.

The basic idea is to set up a rugged tuned circuit which is resonant at the frequency on which it is desired to transmit. A large valve is coupled to this, capable of supplying pulses of energy to the tuned circuit. This valve, in turn, is driven from other smaller valves and tuned circuits, so that it supplies pulses at the appropriate instants.

The net result is that large oscillating or circulating currents are set up in the final tuned circuit—

the one we mentioned in the first place, and it becomes the focal point for large radio frequency voltages and currents.

The tuned circuit is coupled, by suitable means to an aerial system, which radiates some of the energy into space as radio waves. The process of modulation is effected in the final or one of the preliminary valves, so that the "carrier" has the intelligence impressed on it.

Now comes the final part of the question. How is it received?

Imagine an aerial stuck up in the air—that should be quite easy, Tom. Along come a series of radio waves and our aerial suddenly finds itself suspended in what is a huge alternating magnetic field.

By basic electrical theory, a stationary wire in a moving magnetic field must have a voltage and current induced in it, and this voltage is communicated by the lead-in wire to the tuned circuit of a receiver in the house.

Of course, there may be dozens of signals in the air at the one time, and they go shooting down the lead in like water down a drain. But the tuned circuit (or circuits), in the receiver is responsive only to the signal which happens to correspond to its own resonant frequency. It's up to us to tune the receiver so that the right signal is selected.

After that, the signal may be amplified and applied to a detector stage, which extracts the audio components and passes it on for more possible amplification and then application to the speaker.

## MATTER OF TERMS

Well that's that. That question has the distinction of being the longest ever to be answered in these columns. Let's hope you're a little wiser after it all!

Can you please tell me what "umhos" stands for? I have often seen it in articles and valve books.

First, Tom, we must get the term right. Actually the letter "u" is only a valiant attempt on the part of typesetters to simulate the Greek letter "mu," which looks like our "u" with a tail in front. The expression can be written in full and pronounced as "micromhos." As such, it is the unit which expresses the transconductance or mutual conductance of a valve.

This property is fundamentally the ratio between a small change in milliamps of plate current for a certain valve to the grid voltage which caused the change, all other potentials remaining fixed. It is expressed in terms of milliamps per volt.

An alternative method of expression is obtained by multiplying the number of milliamps per volt by 1000, and calling the result "micromhos." Thus, a valve having a mutual conductance (or transconductance) of 3 milliamps per volt (3mA/V.) can be said to have a mutual conductance of 3000 micromhos. Conversely, a valve with a transconductance of 6000 micromhos can be said to have a transconductance of 6 mA/V.

## RADIO ACCESSORIES

We specialise in Radio Parts and stock all reliable brands. We can supply: Coils, I.F.s, Transformers, Resistors, Tubular Condensers, Valves, Wires, Flex, Meters, Testing Equipment, Radio Manuals, Irons, Toasters, Pressure Cookers, Jiff Toasting Irons, Trimmers, Padders, Gang Condensers, Cabinets, Motor and Pickups, Record Changers, Solder Irons, Solder and Electrical Accessories, 4 and 5 Valve Mantel Sets—Portable Sets, Console Radio and Radiograms, etc. Mantel Console and Radiogram cabinets, TECNICO Electric Lawn Mowers, TECNICO PHILIPS and TELEVERTA Radio Sets.

## DAVIS RADIO CO.

Wholesale Radio Distributors

1st Floor—Wembley House,  
841 George St., Sydney.  
Phone M3917


(OPEN SATURDAY MORNINGS)

## Special Offer!

TELECOND
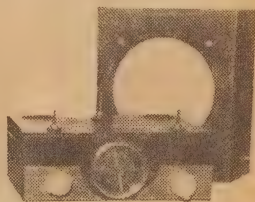
## CAR RADIO

Cabinets, with chassis (27" x 8" x 6"), speaker-power supply box (8" x 7" x 3 3/4"), dial unit to fit: (as illustrated).



The lot, in brown brocade finish,  
only £2/15/-  
(no discounts)

Kit sets, incl. valves,  
from £15/10/-

FINISHED RECEIVERS

## CAR or CAR-LECTRIC


from 25 Gns., incl. car aerial, etc.  
Order early, 7 day delivery.

## P. STEVENS RADIO

21 Fletchers Ave., Bondi. FW6157. NSW.



**RADIO & HOBBIES**  
**KIT SET NO. 2**

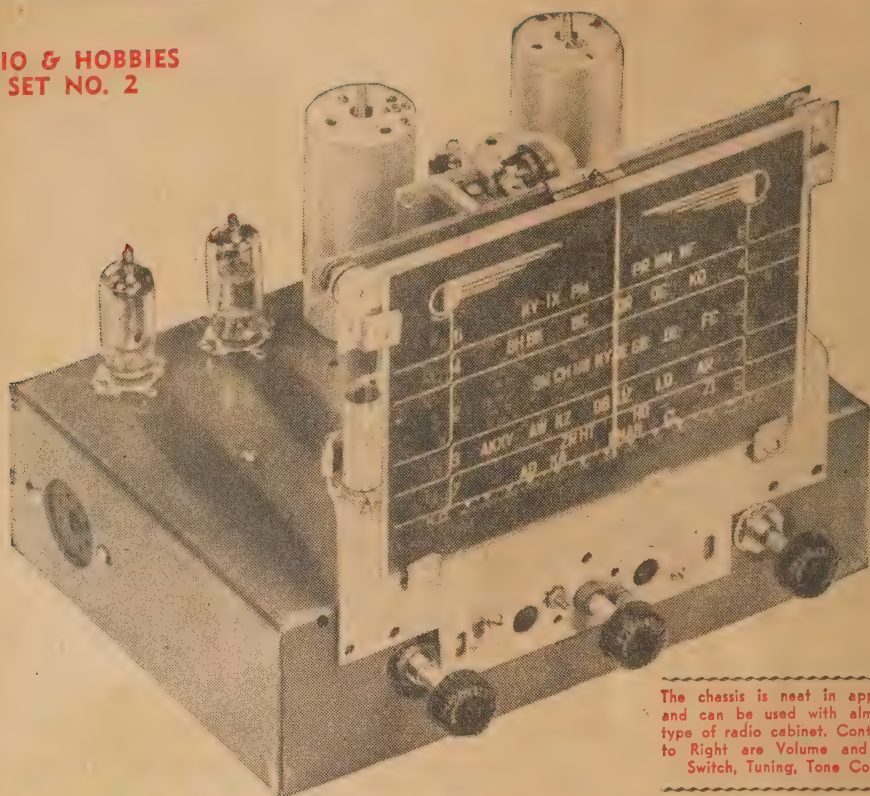

The chassis is neat in appearance and can be used with almost any type of radio cabinet. Controls Left to Right are Volume and Battery Switch, Tuning, Tone Control.

# THE 1950 PENTAGRID FOUR

Carrying on the tradition of the famous "Pentagrid" series, this new set is one of the nicest little four valve jobs we have ever described. It is cheap and extremely simple to build, the current drain is light, while performance is little short of amazing for so modest a design. The compact chassis can be fitted into a console or a table cabinet, or even into a kitchen setting, if your tastes run in that direction.

THE idea behind the introduction of the "Kit" series was covered in the article on the Kit No. 1 in the July issue. Briefly, it is to cater for those readers who want to build something larger than the simple one or two valve set, but who have lacked the confidence to tackle a larger set.

Articles on these sets do not go into a technical discourse on design. Rather, the space is devoted to a "ball-for-ball" description of what components go where, with comments on points to watch and pitfalls to avoid.

All this is supported by an under-chassis wiring diagram and photographs of the set so that nobody

should have any fears of not wiring the set correctly.

So much for that. As far as this set is concerned, you need have no doubts either about its performance. Provide the set with a good outside aerial and an earth and it will do as well as, and in many cases better than, any other standard four-valve

battery set. In our tests we were able to listen to quite a number of country stations in the middle of the day, even through the electrical noise prevalent in a large city.


However, to get down to the business of constructing this set, let's make the first point about tools. There are tools which are essential and others which are handy. You can settle for a medium-sized screw-driver suitable for 1-8th or 5/16 bolts, a pair of side-cutting long-nosed pliers, a sharp knife and a small soldering iron.

A conventional electric soldering iron will be out of the question in many cases unless you have on hand one which is suitable for use with a home-lighting outfit or from a car

by *Raymond Howe*


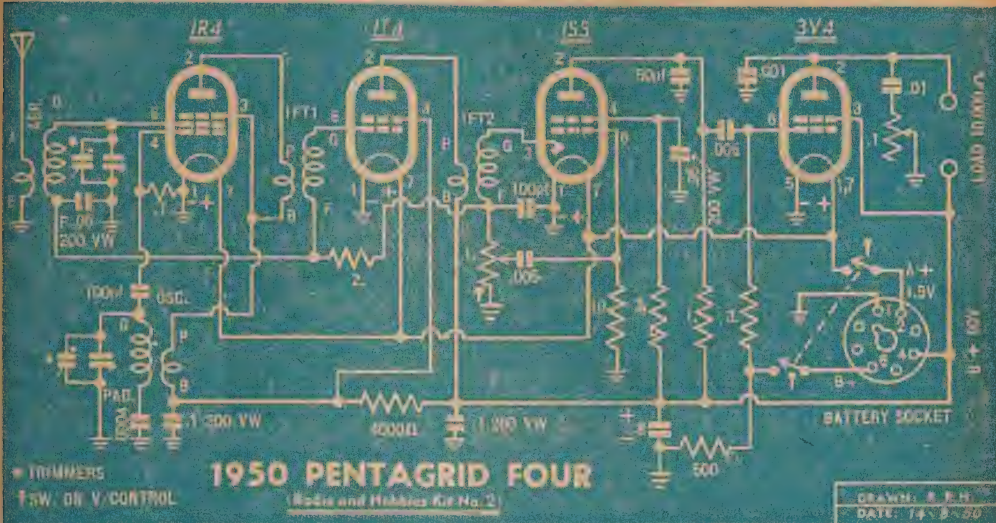
### CIRCUIT DIAGRAM OF 1950 PENTAGRID FOUR



The circuit has been carefully worked out to combine performance and simplicity.

accumulator. Mostly, it will be a case of heating the standard copper bit over a primus or suchlike. If so, use a small bit, as it does not need to hold the heat for very long in order to make one connection at a time.

Use a recognised "radio" soldering paste or flux, together with resin-cored solder. Be sparing with the flux to avoid having it run into the miniature valve sockets or under the heads of bolts holding the solder lugs.

The chassis of this set is somewhat similar to that used for the "All Battery Five" and the "Economy Five" and, in this form, should be available from the larger distributors.


Actually, we intend to supersede the original blueprint of this chassis to take in the modifications embodying new mounting holes for the two-gang tuning condenser, a dial cut-out, speaker socket and odd minor holes.

The two holes at the right-hand front end of this chassis are unused with this set and, if desired, can be covered with a plate. There was little point in changing the design of the chassis for this set just to avoid these two blank holes. The adaptability of a chassis to a number of sets is always a good point in its favor.

NO POWER SUPPLY

As there is no power transformer or filter choke in a battery set to worry about, we can go right ahead with the mounting of the valve sockets. Note that with these miniature valve sockets there are seven

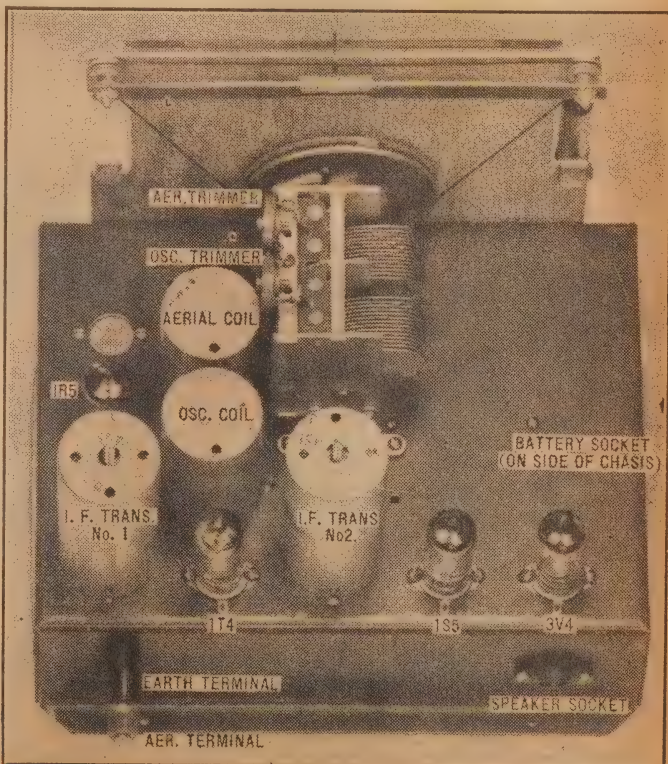Here are the components above the chassis.





**GOOD NEWS!!**

# SUPPLIES ARE IMPROVING


OF

## Australia's Smallest Dual Wave Bracket

Available  
for 550-1630  
KC B/C Band, 16-  
50 Metres, Short  
Wave Band, it comes  
in types to cover all  
popular converter valves,  
INCLUDING TYPE 6BE6.


It's good value too,  
both SW & BC  
padder condensers  
being wired in.

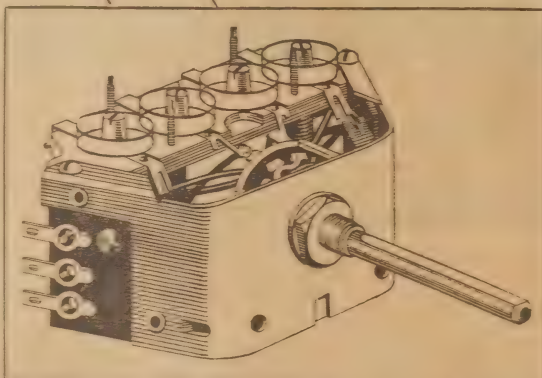Watch for other "Q-  
Plus" 1950 releases  
—Support Australia's  
progressive Radio  
Components firm—  
First with midget  
coils, etc, and first  
with all worth-while  
developments.



*Illustrated approximately life  
size—the new "Q-Plus" midget  
Dual Wave Bracket*

### NOW AVAILABLE

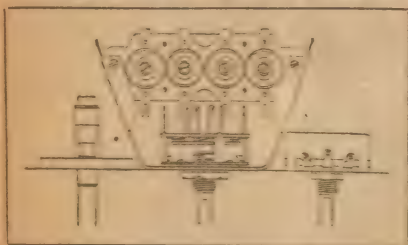

*Showing how the volume control and dial  
spindle fit snugly into position with this  
"Really designed" dual wave bracket.*

Specially shaped to fit into personal portables,  
portables, midget AC sets or just standard radios  
—nothing could be finer—**permeability tuned**  
using special **"SPHERICAL CARBONYL"**  
**Ferro- magnetic cores**, spherical for perfect

high frequency  
insulation, Poly-  
styrene insulat-  
ed - trimmers  
mounted along-  
side cores for  
ease of align-  
ment. Fully  
tropic - proofed  
—in short every-  
thing that a  
1950 coil brack-  
et demands.

**Retail Price 49/6**

Type DW4 — 6J8  
DW5 — ECH35,  
33 or — X61M  
DW6 — 1R5  
DW7 — 6BE6

*NB: This unit  
now replaces  
all earlier  
models.*


Also being released  
shortly, a **SPECIAL**  
**NEW INNOVAL**  
**CONVERTER TYPE**  
**6AN7**

**"Q PLUS" TESTED COILS ARE AVAILABLE FROM ALL  
GOOD RADIO STORES**

*Manufactured and Guaranteed by*

**R. W. STEANE & CO. PTY. LTD. AUBURN, VIC.**
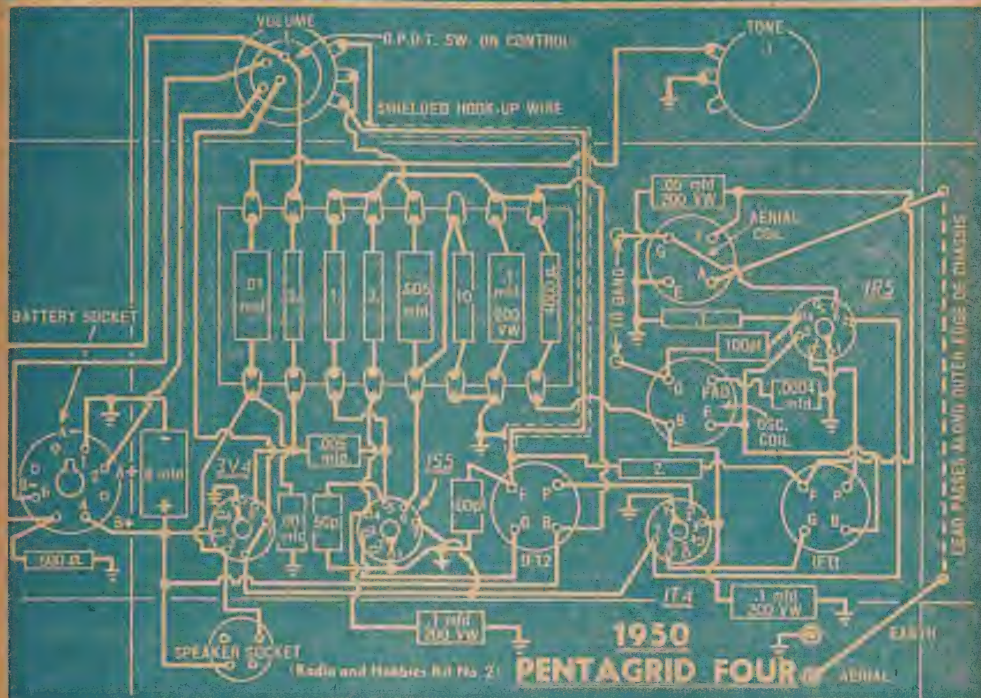
## UNDER-CHASSIS WIRING OF 1950 PENTAGRID FOUR



This diagram has been drawn especially for the use of less experienced constructors.

battery socket has a keyway which will point toward the front of the chassis.

Shielding of the valves is not necessary from the electrical point of view, and we, therefore, did not use the combination miniature socket and shield. The only advantage to be gained from using these would be physical protection of the valves. As you will doubtless have your own ideas as to where the finished set is to be housed, we can leave the further choice of valve socket to you.

Mount the aerial and oscillator coils and the intermediate frequency (I.F.) transformers No. 1 and 2 in the same way as illustrated in the wiring diagram for the same reason as mentioned for the valve sockets.


To make contact with the chassis at the appropriate points use solder lugs under the following bolts. Considering the underside from the position depicted in the underchassis wiring diagram, place one under the left-side holding-bolt of the aerial coil, one on the right side of the IR5 socket, on the left side of the IT4 socket, under both holding-down bolts of the I.F. transformers, on the right side of the IS5 socket, on the left side of the 3V4 socket, under

each of the two bolts holding the octal socket and one under the right-hand bolt of the speaker socket.
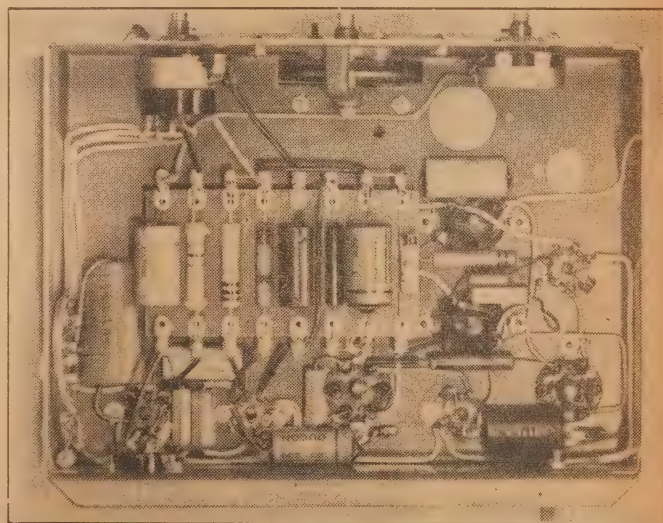
## EARTH POINTS

The "earth" signs in the wiring diagram are shown at points close

to where they are actually earthed in the original set. Make sure that the bolts used for holding solder lugs make good and firm contact with the chassis, even if you have to scrape a little paint away. Be careful when tightening up the hold-




Compare this photograph with the above diagram.


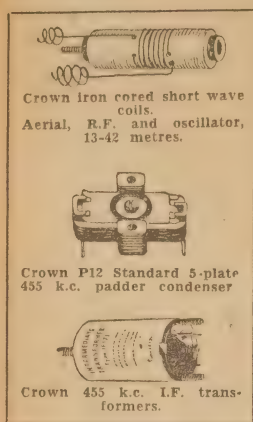
# NOW! FACTORY KITS at FACTORY PRICES!

CROWN MAKES SPECIAL OFFER TO GENUINE AMATEURS



Fully aware of the important contribution that amateur experimentation has made to the development of radio in Australia, Crown Radio Products Pty. Ltd. have decided to assist genuine amateur builders throughout the Commonwealth by offering the latest in quality radio components direct from the factory. This will mean a big saving in component costs to genuine experimenters. The directors of Crown Radio Products Pty. Ltd. feel that some concrete acknowledgement should be made of the value that amateurs have added to the standing of Australian radio. Crown components are already well known for their quality. They cover coils, transformers, padders, short wave kits, in fact, practically every component required by the ham. Genuine amateurs should avail themselves immediately of this great Crown offer and write direct to Crown today for full particulars.


Write today for full particulars of Crown's offer to genuine amateurs.

**Crown**  
**RADIO PRODUCTS PTY. LTD.**  
51-53 MURRAY STREET PYRMONT — SYDNEY  
Telephone MW2628 (2 Lines)

**PRESENTING**

★ **TWO SPEED!**

**THE NEW  
CONNOISSEUR  
GRAMO-MOTOR**

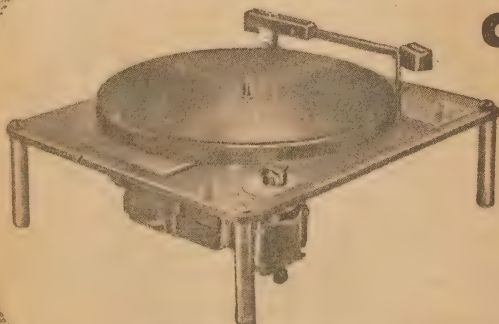

Available with or without Pickup as illustrated.

Sensational news for the Radio Enthusiast a brilliant new **TWO SPEED** connoisseur Gramo-motor, precision engineered throughout to the usual connoisseur standard. 78 or 33 1/3 r.p.m. at the turn of a switch. Low noise level and hum induction. Heavy lathe-turned turntable of non-ferrous material. Phosphor bronze bearings—all spindles hardened, ground and lapped. Input Voltages 200-250V A.C., 50 cycles.

From Selected Distributors Throughout Australia or

**J.H. MAGRATH & Co.**

PTY.  
LTD.

**208 LT. LONSDALE ST., MELBOURNE** *Phones. CENT. 3688 4414*

ing-down bolts of the coils and I.F. transformers, as too much pressure will pull the eyelets out of the side of the aluminium can.

Speaking about the I.F. transformers, there are differences in the electrical characteristics of the one feeding the 1T4 I.F. amplifier valve and the one feeding the diode of the 1S5 second detector valve.

For means of identification, the transformers are marked "No. 1" and "No. 2" respectively. No. 1 is mounted between the 1R5 and the 1T4 and the No. 2 between the 1T4 and the 1S5. The No. 1 transformer will have a lead coming out of the top of the can. This lead is for use with valves which have the control grid connection brought out through the top of the envelope. It is not required with these miniature valves and should be clipped off close to the top of the can, leaving about 1-8th of an inch to spare to avoid shorting to the can.

Before commencing the wiring,

## PARTS LIST

- 1 Chassis 8½" x 6½" x 2½".
- 1 Small 2-section gang tuning capacitor (AWA).
- 1 Dial to suit (USL44 or similar).
- 1 Broadcast aerial coil, 1 broadcast oscillator coil (for 1R5 or 6J8-G).
- 2 Standard high-gain 455 kc I.F. transformers, No. 1 and 2.
- 2 Gang trimming capacitors.
- 4 Miniature valve sockets, 1 octal wafer socket, 1 4-pin miniature plug and socket.
- 1 1.5-volt dry battery and two 45-volt dry batteries (capacity to suit requirements).

### VALVES

- 1 1R5, 1 1T4, 1 1S5, 1 3V4.

### CONDENSERS

- 1 8 mfd. electrolytic, 2 0.1 mfd. 200VW tubular, 2 0.05 mfd. 200VW tubular, 1 0.01 mfd. tubular, 2 0.005 mfd. tubular, 1 0.001 mfd. tubular, 1 0.0004 mfd. mica (low tolerance), 2 100 pf. mica, 1 50 pf. mica.

### RESISTORS

- 1 10 meg., 2 3 meg., 1 2 meg., 1 1 meg., 1 1 meg. potentiometer with DPDT switch, 1 0.1 meg., 1 0.1 meg. potentiometer, 1 400 ohm, 1 500 ohm.

### SUNDRIES

- 2 Terminals (1 red, 1 black), 3 knobs, 4in of terminal strip, approx. 7in of solder, solder lugs, nuts and bolts, 2 ½" bolts 1" long, etc.

mount the remainder of the components, such as the speaker socket, the aerial and earth terminals, the volume and tone controls, the 2-section tuning gang and the dial. In fitting the tuning gang, use an 1-8th nut as a spacing washer under each of the four mounting bolts.

Don't forget to use the insulating washer supplied with the terminals when mounting the one for the aerial. Place a solder lug between the nut and insulating washer. Naturally the earth terminal should make contact with the chassis, so use an ordinary 1-8th metal washer under the nut.

When it comes to the act of solder-

ing, we will presume that you know the story, in that the bit should be cleaned and then well tinned. Watch the heat of the bit to avoid burning the tinning off. Apply just sufficient heat to a connection to allow the solder to run freely, particularly in the case of the terminal wires to the coils and IF transformers.

Now to the actual wiring. Commence with the earthing of the centre spigot of each valve socket to the negative filament pin of the socket, and thence to the solder lug nearest to each socket. It is a good idea, actually, to connect all earth points together with a length of busbar.

Earth pin 1 of the battery socket to the solder lug near to it, and run a wire from pin 2 of this socket to one side of one pole of the switch on the volume control. The other side of this pole of the switch connects to pins 1 and 7 of the 3V4 socket and thence in turn to pin 7 of each of the other valve sockets. The filament circuit is now complete.

You can find out which of the four lugs on the DPDT switch on the volume control are associated with the aid of a multimeter, or a battery and torch globe.

The next step is to put in all those leads which run from valve sockets to coils or I.F. transformers, from coils to the tuning gang sections, aerial terminal to aerial coil and from the speaker socket to the 3V4 socket.

## "B PLUS" WIRING

This section of the wiring will include also the wiring of B-plus from the battery socket to the 3V4 socket or the speaker socket and the runs from pins 5 and 6 of the battery socket over to the switch on the volume control. Wire the 500 ohm resistor from pin 5 of the battery socket to the earthed solder lug just near it.

Now is the time for the installation of those components which are not mounted on the terminal board. Start with the 0.05 mfd. A.V.C. bypass capacitor between terminal "F" of the aerial coil and the solder lug under the left holding-down bolt. Then follow with the 0.1 megohm oscillator grid resistor from pin 4 of the 1R5 to the same solder lug. The "E" terminal of the aerial coil also is earthed at this solder lug.

Carry on around the chassis with the components as they appear in

**EVERY FAMILY  
NEEDS A  
SECOND RADIO**

**And you can use a portable radio  
anywhere!**

The most powerful batteries are



**EVEREADY**  
TRADE-MARKS  
**MINI-MAX**  
**PORTABLE RADIO BATTERIES**

— they last longer, too!

EM50-4



## RANGE FINDERS

Horizon and Bubble Type. A beautiful precision-made instrument with valuable lenses and revolving calibrated disc. Can be used for measuring depression as well as elevation in feet. Original cost to R.A.A.F. £35.  
Our Price, **£10/10/-**  
Each .....

Post Free.

## Military Overcoats

For warmth and hard wear these Coats are unexcelled.

OUR PRICE

**30/-**

Sizes: S.M. and M.

Post 2/-; Interstate, 3/6.

## CALICO

Super quality calico by the ROLL! This is the best quality we have handled for some time. In 30yd. Rolls, 36in. wide.

PER ROLL .....

Post Free.

**11/3**

Or In Eyd. lengths .....

Post 1/3 extra.

## P.M.G. ADJUSTABLE MORSE KEYS



Genuine P.M.G. Morse Keys, with adjustable buzzer, brand spanking new. Cost the Army £4/10/-.

OUR PRICE .....

**10/- ea.**

Without batteries, which are easily obtained at any electrical store.

Postage: N.S.W., 1/6; Interstate, 2/6.

**Only 10/- ea.**

## ARMY WORSTED SHIRTS

Jungle Green Work Shirts, made from soft Wool De Chene material. Will stand tough wear. Sizes 17 to 18 inches neck. Unsurpassed value. Shirt with separate collar .....

**14/6**

Shirts with attached collar .....

**17/6**

Post 9d; Interstate, 1/3.

## Blue Drill Work Shirts

All sizes, a good, strong wearing shirt.

Each .....

**14/11**

Post: N.S.W., 9d; Interstate, 1/3.

## Bearing & Distance Plotter

For measurement of bearings and distances. It is provided with a protractor and scales. Made of celluloid.

Price, each .....

**3/-**

Post, 6d.

## COURSE & WIND CALCULATOR

A super precision made instrument. All aluminium. Original cost to R.A.A.F. £24. Our Price, Complete with well-made wooden case, 12" x 12" x 4".

Only, each .....

**£3/10/-**

Post: N.S.W., 1/-; Interstate, 1/6.

LUMINOUS DIALS.

## AIRCRAFT FUEL GAUGES

190 Gal. Capacity. Cost R.A.A.F. £25.

Our Price, each .....

**10/-**

Post, 1/6 extra.

## Imported Prismatic Binoculars

We have a grand assortment of Binoculars, including some of the best German, English and French Makes.

## LARGE RANGE AVAILABLE

6 x 24 .. £10 10 0 Wide Angle £12 10 0  
6 x 30 .. £12 10 0 Wide Angle £14 10 0  
8 x 24 .. £13 10 0 Wide Angle £15 10 0  
8 x 30 .. £15 10 0 Wide Angle £17 10 0  
Wide Angle 7 x 50 .. £25 0 0

Well packed. Post, Ins. Free.

## GROUND SHEETS

Brand New Ground Sheets, 74 x 38.

E1 value,

Special Price, each .....

**13/6**

Post: N.S.W., 1/-; Interstate, 1/6.

## FEATHER SLEEPING BAGS

Warm and cosy lightweight bags, weight only 3lb., roll up into small carrying bag.

Each .....

**77/6**

Post: N.S.W., 1/9; Interstate, 2/6.

## Khaki Drill Jackets

Coat Style, ex-R.A.A.F. In sizes S.M. and M.

Only, each .....

**9/6**

Post: N.S.W., 1/-; Interstate, 1/6.

## Gas Bottles

As used to inflate rubber dinghies. Will hold many pounds of pressure. Approx. 12 inches long, 3 inches in diam., weight 3/8lb. Sturdily constructed with screw top release valve.

Only .....

**10/- ea.**

Post: N.S.W., 1/6; Interstate, 2/6.

## OIL PAINT

A genuine Oil Base Paint, extra good quality. Gray, Red, Cream, White, Chocolate, Light Stone, Dark Stone, Mild Stone, Green.

1 Gallon Tin .....

**£17/6**

4 Gallon Drum .....

**£5/-/-**

Please add 1/6 per drum cartage to rail.

Freight payable at your nearest attended railway station.

## SPEED INDICATORS

Perfect Condition, made by Elliott Bros., of London. In three ranges: 100 to 500 Revs. 400 to 2000 Revs, and 800 to

4000 Revs. Each .....

**£5/15/0 ea.**

Post 2/6 extra.

## GREY BLANKETS

Pure Wool Army type, 3 1/2lb in weight. 78in. x 56in. Brand NEW

each .....

**37/9**

Post: N.S.W., 1/3; Interstate, 2/-.

## TRAVELLING RUGS

Pure Wool, soft and woolly, in pleasingly colored overchecked designs 3 1/2lb in weight. Brand NEW.

**46/6**

Post: N.S.W., 1/3; Interstate, 2/-.

OUR LATEST DISPOSALS PURCHASES

## ALL EX-R.A.A.F.

SUPER QUALITY ELASTIC CORD

in 40ft. Lengths.

3/16in. in diameter.

This cord is comprised of 14 strands of best quality elastic and covered with cotton.

Price, per 40ft. length

**6/6**

## COURSE and SPEED CALCULATORS

A beautiful precision made calculator with Port Drift and Starboard Drift Indicator, may be used for many types of calculating. Complete with neat dovetailed wooden case, 11" x 6" x 2 1/4", fitted with brass hinges and catches and leather handle. Cost Air Force £12/10/- each.

Our Price, each .....

**15/-**

Post: N.S.W., 1/3; Interstate, 2/-.

## COMPUTORS

Height and Airspeed Computers, aluminium calibrated disc types. Original cost £7/15/-.

PRICE, .....

**7/6**

Post: N.S.W., 1/-; Interstate, 1/6.

## American Directional Gyro Indicators

Brand New. Contain a specially precision made Gyro.

ONLY, each .....

**15/-**

Post: N.S.W., 1/3; Interstate, 2/-.

## Aircraft

## Luminous Compasses

Brand New. Liquid filled, 3 1/2" diameter x 3" deep. Ideal for ships, small-craft, etc. Original cost £19.

Our Price, each .....

**£3/15/-**

AND SLIGHTLY USED .....

**£2/10/0**

Post: N.S.W., 2/-; Interstate, 3/-.



## HEAD PHONES

Brand new S.T.C., complete with cord and plug.

2000 ohms Impedance .....

**£1**

Suitable for crystal sets. Postage 1/6 extra.

## REFLECTOR GUNSIGHTS

Ex-Air Force. Containing best quality condenser lenses and adjustable reflector. Parts can be used for many purposes.

**£2/5/- ea.**

Postage 2/6 extra.

COMPONENTS

INCLUDE THESE

VALUABLE LENSES.



No. 1 Diam. 3% Foc. Len. 10in. No. 2 Diam. 3% Hollow Ground. No. 3 Diam. 3 1/4 Foc. Len. 4 1/2in. plus No. 4 Diam. 2% Foc. Len. 6 1/2in. plus No. 5 Diam. 1 1/2 No. 6 Diam. 1-18 Amber Coloured ordinary.

Sorry, No. C.O.D. SPECIAL ATTENTION PAID TO MAIL ORDERS AND WE GUARANTEE PROMPT DELIVERY.

# DEITCH BROS.

DEPT. R, 70 OXFORD STREET, SYDNEY.

the underchassis wiring diagram and photograph. You will note that on the tubular capacitors the outside foil is marked on the label either with the words or a black ring at one end. Where there is no label, you will find a small "blob" moulded near one end. With those capacitors shown in the circuit as connecting to "earth" or chassis, connect the end marked "outside foil" to the chassis. With the 8 mfd. electrolytic, the red end is positive.

By this time you will begin to appreciate how simple the wiring of the set really is. Nothing is crowded, and it is possible to see almost every wire at a glance.

Very little else now remains to be done. It's simply a matter of installing the terminal board, mounting the eight components thereon and wiring them into circuit together with the volume and tone controls. The underchassis wiring diagram renders unnecessary any further comment in this direction.

The only wiring necessary on the top of the chassis is the mounting of the aerial and oscillator gang sections trimming capacitors. We mounted them on their side on the top of the frame of the gang with one side of each soldered to a gang section lug and the other side soldered to a solder lug held under a bolt passed through a hole in the top bar of the frame. The top plate of each trimmer should be the one which connects to the solder lug,

### Resistor Color Code

VALUE	BODY	END	DOT
10 megohm	Brown	Black	Blue
3 megohm	Orange	Black	Green
2 megohm	Red	Black	Green
1 megohm	Brown	Black	Green
0.1 megohm	Brown	Black	Yellow
4000 ohms	Orange	Black	Red
500 ohms	Green	Black	Brown

thus earthing the adjustment screw. We have not shown the dial lights as being connected into circuit mainly from the point of view of keeping the A-battery drain to a minimum. You can please yourself about this point.

You are now ready for the initial trial and setting-up. However, before applying power to the set give your finished job a thorough visual inspection to ensure that there are no wiring errors and that all soldered joints meet with your approval.

Wire the batteries to the battery plug, making sure that you count the pins in the correct way, that is, when looking on to the pins. Leave the valves out of their sockets for the moment and plug the batteries in. Wire a couple of short leads to a torch globe and test each valve socket filament wiring by touching the leads between pin one and earth. If the globe glows nicely at each socket you can consider that, so far, your wiring is OK and that it is safe to plug the valve in. Torch globes are much cheaper than valves, if you see the point.

Don't be too hard on these minia-

(Continued on Page 99)

# HOMECRAFTS

## CARRY COMPLETE STOCKS OF ALL RADIO COMPONENTS


### SET BUILDERS —

### EFCO DIALS

Type MSL48	26/11	Type MK17A	13/7
" USL 37	25/9	" SLV 21	28/6
" USL 44	31/2	" SLV 45	30/1
" USL 46	41/5	" USL 50	41/5

WRITE FOR FREE ILLUSTRATED LIST

R  
O  
L  
A

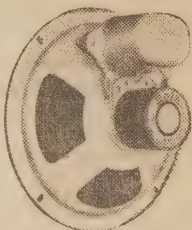

N.S.W. distributor for  
Rola speakers, chokes  
and Transformers —

FREE ROLA CATALOGUE  
MAILED ON REQUEST.

SUPER PICK-UP  
BARGAINS.

TRU-TRACK MAGNETIC PICK-UP. The famous Tru-Track Magnetic Pick-up with curved counter-balanced tone arm and off-set head. As illustrated, reduced from 70/- to 14/11.

## NEW STOCKS

P.A. amplifier chassis and covers. Grey crackle finish, up to 14 valves — £4/19/6

Polystyrene lining up tools  
Test leads complete with banana plugs and prods.  
Red and black. Pr. — 8/3

D104 Crystal Microphones chrome casing. Complete with lead. — £4/19/6

Floor Microphone Stands

Complete range of Uni-versity test equipment.

## SPECIALS

### ERSIN MULTICORE SOLDER KITS.

Contains four different coils of famous multicore solder—ideal for handymen 3/- ea.

We carry full stocks of Rola Speakers; Eveready Batteries; Radiotron and Philips Valves; Aegis and "Q" Plus Coils and L.F.T.'s; Ducon Chanex and Simplex Condensers; I.R.C. Resistors and Vol. Controls; Ferguson and Henderson Chokes and Transformers; Ferrocart and Oak Vibrators; Palec Meters and Test Equipment; Astor Car Radio Sets; etc., etc.

CADMIUM PLATED  
1/8" NUTS AND BOLTS  
Available in gross pkts.  
Only — 4/6 gross.

### KITSETS

We will quote you for any  
Radio and Hobbies Kitset—

CAR RADIO KITS  
AMPLIFIER KITS

Try Our Mail Order Dept.

# HOMECRAFTS PTY. LTD.

98-100 CLARENCE STREET, SYDNEY.

Mail Orders, Box 5000, Sydney.

Phone: BX4451


Also at 26 Hunter Street, Newcastle.



# Quality Components

At Clearance Prices

## SWITCH POTENTIOMETERS

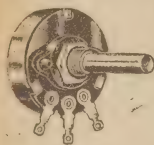

Standard 1 meg. potentiometer with SP switch 1 3/8" dia. with 1" spindle 2" long. Usually 9/3. Bargain Price.

**4'9**

Postage 3d. extra.

## KEY SWITCHES




Standard telephone type key switch with single action lever motion. Four pole double throw.

**5'6**

Postage 6d. extra.

## POLAR Miniature Gang CONDENSERS

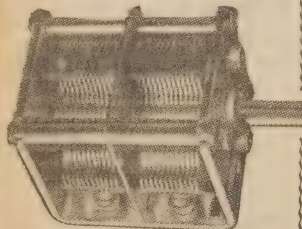

A precision English miniature tuning condenser suitable for all small receivers. Capacity is 385 mmF. Height 1 1/2". Width 1 1/2". Length 2" and 3" respectively.

A GENUINE REDUCTION.


Two Gang **15'-**

Three Gang **18'6**

Postage 9d. extra.
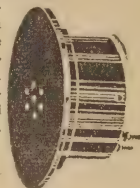
## DYNAMIC PHONE UNITS

Genuine dynamic phone units, in bakelite case with ear pad. Impedance 45 ohms. Ideal for microphones or small loud speakers. Brand new.



**5'-**

Postage 6d. extra.

## VIBRATORS

Brand new Type V5211 6volt, 7-pin split reed—

Buy a spare now at 1/3rd of the original price.

**10'-**

Postage 6d. extra.

## METERS



Best quality English meters. 2" dia. flush mounting. Available in two ranges only:— 0-1 mA. and 0-500 microamps. These meters are half their normal price.

0-1 milliamps. **32'6**

0-500 microamps. **50'-**

Postage 1/- extra.

## TOYS

Xmas is approaching and the wise buyer will order now—large stocks are available:—

- HORNBY TRAINS.
- MECCANO SETS.
- DINKY TOYS.
- DUBLO TRAINS
- ETC., ETC.

## ACOS GP10 CRYSTAL PICK-UPS



Incorporating the unbreakable crystal, housed in a smart, moulded bakelite arm with plated finger-lift bracket.

Resonance-free response from 50 8000 cps. Output 1.5 volts at 1000 cps. Nominal needle pressure 1 1/2oz. (Adjustable).

Usually £2/8/6

A few still available.

**32'6**

Postage 1/- extra.

## 5" PERMAG SPEAKERS




Well-known 5" speaker at less than half price, fitted with 12,000 ohm transformer which is suitable for most battery valves and 6V6 with 100V on screen. Brand new in original cartons.

**19'9**

Postage 1/3 extra.

## VERNIER DRIVES

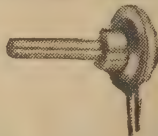

An English ball-driven unit with a ratio of 6:1 to 4" spindles. Ideal for construction of small vernier dials.

To Clear at **5'-**

Postage 3d. extra.



# Price's RADIO

5 & 6 Angel Place  
SYDNEY

# FITTING AN EXTENSION SPEAKER

VERY often in a home the need arises to hear a programme at a point remote from the radio. If, for instance, the radio is installed in the living room, the pleasure of quiet background music to accompany meals in the breakfast-room is denied.

Certainly, it is possible to turn the set on full blast to do the job by brute force, but this is not likely to help the neighbors' nerves, nor is the quality of the programme heard under these conditions likely to be good.

Apart from the instance quoted, there are dozens of other situations in which the utility of the family radio can be extended by a remote speaker.


## DOMESTIC SETS

This is probably a good argument in favor of a second set or a portable. However, a complete radio costs a good many pounds, as can be verified by a visit to your local radio dealer or parts supplier.

Most domestic receivers nowadays follow the same general pattern. Five valve, either dual-wave or broadcast, with a single-ended output stage. In eight cases out of ten the output valve will be a 6V6-G. Other common types are 6F6-G and EL33N. All have standard octal bases and exactly the same pin connections.

By fitting an octal socket into the top of an old octal valve base, it is possible to tap into both the plate and screen wiring of the output valve without interfering with the set's internal wiring. Simply add a switch and the primary winding of the extension speaker can be switched in or out as required.

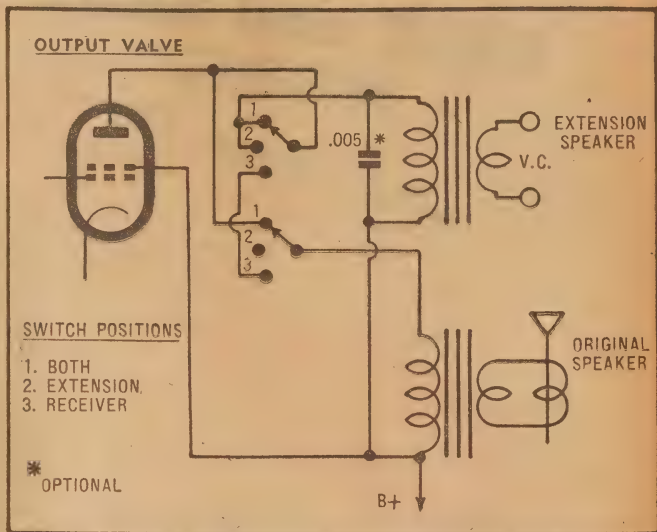Admittedly, the load conditions for the output valve are upset somewhat when the two speakers are operating, but listening tests show that the effect on quality is not even noticeable to the average ear. Quite an im-



Electrically, the circuit operates the speakers singly or in parallel.

With the aid of this little unit, you can fit an extension speaker to your radio simply and easily. Either or both speakers can be operated at the flick of a switch. No special knowledge of radio is required. It is not even necessary to take the set out of its cabinet.

provement on the technique of turning up the volume control!

The unit can be made up in any physical form which happens to be convenient. Most constructors will probably install the switch and output transformer together on a small panel or in a case which can be mounted in a convenient position near the radio. The adaptor plug is connected to it by a length of three-core flex or twisted hook-up wire.

The extension speaker voice coil


leads may be run with ordinary plastic power flex.

We have specified the .005 mfd. condenser across the primary of the extension speaker as an optional component. If the speaker is small and mounted on a small baffle it will probably sound a little high-pitched and the condenser helps to restore the balance.

The exact load reflected by the extension speaker transformer is not particularly critical. Anything between about 5000 and 10,000 ohms would be suitable.

Although the diagram we have drawn is for an octal-based valve, there is no reason why the idea could not be extended to any other pentode or tetrode, operating with equal plate and screen supply. With a little care, an adaptor could be made up to accommodate either the noval or button-based valves.

Almost any serviceman would be willing to oblige with an old valve from which you can obtain the base for the adaptor, and the socket can be bought as a stock line. Solder the insulated wires into the base first, allowing the interconnecting leads to extend about an inch over the top for easy soldering. After the wires have been attached to the socket, they can be pushed down into the body of the base and the two can be firmly cemented together. Drill a hole in the side of the base to take the leads to the control box before doing any soldering.

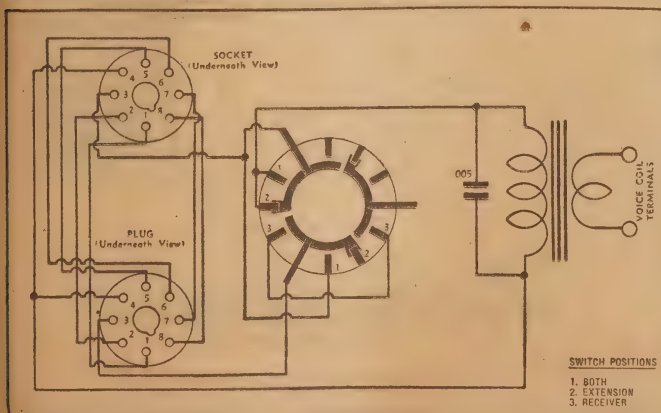

Pictorial diagram of the wiring. Components inside the dotted border normally mount in the switch box.



**FAST and EASY  
WORK**  
with these three.

*University*

**Universal  
Speaker  
and Output  
Meter — USO.**



This is a much needed and widely popular Radio Service Instrument combining the functions of an accurate calibrated output Meter with a Universal Speaker designed to suit all types of Radio Receivers and Apparatus whether A.C. or D.C. The Meter is calibrated in decimals and watts, and three ranges of 0-500 Milliwatts, 0-5 Watts and 0-50 Watts are provided. The "University" Square Rectifier type Meter is used and it comes complete with book of Instructions and all necessary Leads.



**STB — SIGNAL TRACER.**

Self-contained and Battery operated, the STB traces a signal right through the Radio Receiver from start to finish. Fault finding is quick and easy. When the probe strikes a faulty section indications are given on both Meter and Speaker. This Portable, light and sturdily constructed Instrument, is a definite necessity for fast, speedy and accurate servicing.

**DCM —  
MULTIMETER.**

This small and easily Portable Multimeter is well built and accurate. It provides the following ranges:—

- D.C. Volts:—10, 50, 250 and 500.
- D.C. Current:—1, 10, 50 and 250 Milliampères.
- D.C. Resistance:—0-1000 and 0-100,000 ohms.

It is entirely self-contained and comes complete with Test Leads and Instruction Card.



*University*

**RADIO KIT SETS • RADIO & ELECTRICAL TEST EQUIPMENT**

MADE BY UNIVERSITY GRAHAM INSTRUMENT CO., 5 North York Street, Sydney. Phone BU3169—2 lines.

## LET'S BUY AN ARGUMENT

(Continued from Page 31)

After careful analysis, he produced a special wide-band tuner terminating in a low-distortion push-pull amplifier.

This would leave me in a spot and anyone else who has discovered the usefulness of tone compensating stages in the domestic amplifier set-up. Control and pre-amplifier stages in push-pull are liable to get very messy and by the time audio is coaxed from the output stage, there would be more bits and pieces than a radar station.

I'm not trying to belittle the efforts of our worthy contributor, who has concentrated a lot of thought and ingenuity into his tuner design. It is possible that the principles can be applied to produce a more simple hi-fi circuit which will be a worthy partner for our best amplifier efforts. In the meantime, anything that's too complicated isn't good enough.

### TOO COMPLICATED

That last remark goes, amongst other things, for the whole present conception of television, with or without the added headache of FM sound.

We may carry on with the present techniques for many years, but sooner or later someone will come up with a principle that will outdate our best efforts at one stroke. The whole business of 25-tube sets and 19-tube color adaptors is plainly fantastic, and more than one engineer agrees with me on this point.

With all this off my chest, I'm beginning to feel better about things. But, just as a final gesture, let me disburden myself of two more "technicalities" which seem particularly to get under my skin.

Number one is the idea of regarding a crystal set as the ultimate reference for fidelity or clarity — the distinction between the two seems vague.

Someone builds a set, says that it goes well, gets all the stations, &c., but "it lacks the sweetness" of a crystal set. Pardon me while I tear our another handful of hair!

The whole point about a crystal set is that it offers only the bare minimum of sensitivity necessary to receive the strongest local stations. They are the only ones ever listened to and there is never any question of competing with the noise level. What's more, the earphones are normally clamped to the ears, blocking out all the distracting external sounds. With this enforced selection and concentration, is it any wonder that signals have a distinctive clarity.

But as for fidelity, have you ever examined the response curve of ordinary earphones? There's a big hump in the middle, sundry peaks on either side and beyond that—nothing!

Nor am I convinced about the fidelity of crystal detectors. Some spots on some detectors are very good but other spots are worse than any valve detector I've ever heard. To demonstrate the fact, simply feed

## TWENTY YEARS FROM NOW

(Continued from Page 13).

to begin work and that we can expect practical results in five years.

Plentiful and cheap power is not the only benefit from atomic energy we shall be getting in 20 years. Medicine will benefit very greatly as atomic fissure makes it possible to obtain great quantities of radioactive substances for tracers and medical purposes, so that we can think of "radium treatment" in a new way. Is less than 20 years time the cost and shortage of radium which handicapped surgeons will have disappeared.

### RADIOACTIVE ELEMENTS

In addition, atomic fission enables us to create radioactive elements and compounds, like "heavy water," in which the ordinary hydrogen of plain water is replaced by a special form. A whole new field opens up for chemistry.

The number of possible substances is immensely multiplied. We have not yet had time even to contemplate what some of these new "materials" may be like, or what magic we can perform with them.

These radioactive elements could, in many cases, be made before atomic fission, but only in minute quantities at immense expense. Now they are mere by-products of atomic piles and should become plentiful.

In 20 years the results of research based on these new substances should be apparent. They may be very far-reaching. Consider one piece of research alone that may be made possible with the aid of atomic-pile by-products. Scientists have never been able to unravel the process by which plants, with the aid of sun-

shine, turn water, carbon-dioxide, and mineral substances into living tissue.

Before 20 years are passed, with "activated" materials the mystery may be solved. In 20 years we may be setting up food factories in which starches and sugars are really synthesised on the same principles as plants work. The effect would be revolutionary. It would mean the end of the danger of famine anywhere in the world.

Atomic energy will bring new responsibilities which are not limited to its use as an explosive. If we obtain energy to change climate and weather, we shall be forced to work in co-operation with other nations to avoid disaster. Warming the Polar regions, for instance, might have far-reaching effects on the weather in the rest of the world.

### A HAPPIER PLACE

Many people say it would have been better if the scientist had failed in his effort to "split the atom," and that the world would have been a happier place. Myself, I like to think that this great achievement is the beginning of an adventure, perhaps the greatest adventure on which the human race has ever embarked.

Whether the adventure ends in disaster or in triumph may well be decided in the next 20 years. Disaster will come through failure to realise our responsibilities. But triumph cannot come simply by negative action. Research for the exploitation of the atoms as necessary as avoiding its use for destructive purposes.

the output into a good amplifier and listen!

Last, but not least, I have a particular aversion to the stock phrase which runs this way . . . "Theoretically such and such is the case, but in practice, it does not hold good."

The phrase is plainly incongruous and self-contradictory, because theory and practice are completely complementary. One is the expression of the other. To suggest any difference between the two is tacitly to admit that our theory is incomplete (or incorrect) or that our practical observations are at fault.

### EXAMPLE

Let's just take a simple example and, for the purpose of illustration, I invent a typical statement.

"Theoretically, a 6V6 should have -12.5 volts of bias but, in practice the bias can be increased to 14 or 15 volts without affecting the power output."

This statement, like so many others of its kind, appears to create a divergence between theory and practice but the fault is really in the statement itself. It is incomplete and misleading.

According to tables and graphs (which are the "theory" in this case) a 6V6 does need -12.5 volts of bias under ordinary operating conditions. Increasing the bias by the suggested amount will, in fact, decrease the power output by an amount which can be calculated theoretically and demonstrated practically with quite simple gear.

### THEORY


I agree that you may not be able to notice much indifference by listening tests but this does not disprove the matter of optimum bias.

Theory also explains, if we look for it, that our ears cannot detect a change in level or power smaller than 2 or 3 decibels. Our ears are the guilty party in this instance, not the implied discrepancy between theory and practice.

And it's just like that for every other case you like to think up. There never is and there never can be any discrepancy between the two. It's just that we don't know enough, or we interpret wrongly, or we fail to observe accurately the things that happen "in practice."

Thanks readers, I feel better now.



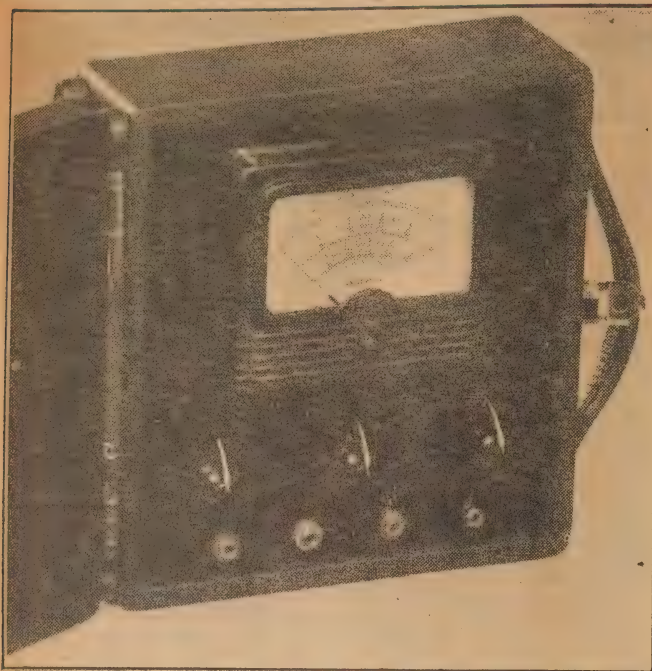

The instrument installed in its leatherette covered case. Rubber feet are fitted and the meter can be used in either a vertical or a horizontal position.

always at a disadvantage. There is no need to elaborate on the value of a-c scales for checking power transformer voltages, making power output measurements, &c.

If a built-in blocking condenser is included to facilitate making relative output measurements for receiver alignment, so much the better.

#### COMPONENTS AVAILABLE

Having established the general trend of our proposed multimeter we made a systematic check with the principal meter manufacturers in order to determine the type of meter that you are most likely to be able to buy over the counter from your usual radio supply house.

The differences between the usual run of test meters are connected with the a-c and the ohms scales.

Meter rectifiers tend to read the average value of a sinusoidal alternating voltage. The average value is approximately .9 of the R.M.S. value which is the quantity usually quoted. For this reason, manufacturers make some meters with

# THE STANDARD MULTIMETER

A multimeter is an indispensable item for anyone who is taking up radio as a serious hobby or for those who plan to graduate to full-time radio service work. The instrument described here is perfectly standard in design and uses parts which are readily available.  
Radio & Hobbies Kit No. 3.

**B**ASICALLY, most multimeters for radio work are much the same nowadays. Variations are mainly in the physical shape and layout and the method of selecting ranges.

Moving coil meters have proved their accuracy and reliability for this type of work over many years. The usual sensitivity is in the vicinity of 1.0 mA, which is a good compromise. Meters of higher sensitivity are in existence but the benefits of the lighter circuit loading are offset by the greater cost and the likelihood of accidental damage to the delicate movement.

Apart from this, meters of higher sensitivity give readings which differ from the standard 0-1 mA meter in certain cases, due to the altered loading, and since readings quoted on some commercial circuit diagrams are for the standard meter, the position becomes confused with a non-standard type.

In designing a multimeter it is necessary to consider carefully what

ranges will be required. Without going into this aspect of the subject too deeply, we have found by experience that it is desirable to measure direct current within a range of from about .1 mA to 250 mA, d-c voltages from about 1.5 to 1000, while a selection of ohms ranges is also desirable.

#### A.C. SCALES

Even country experimenters will find the a-c voltage ranges very desirable. Vibrator power supplies and rotary converters are coming into more general use and an instrument which lacks this facility is

sensitivity of .9 mA. The full sensitivity of the meter is used on the a-c ranges and a shunt is connected in parallel with the movement so that the same set of scales can be used for the d-c ranges.

The ohms scale on some meters is designed for use with a 1.5 volt battery while others are calibrated for a 4.5 volt battery.

Our investigation showed that 0-1 mA. meters with separate a-c scales and an ohms scale designed for 1.5 volt battery are the easiest to obtain and, accordingly, our instrument was designed to use this type.

If you have a 0-.9 mA meter on hand, it should be possible to contact the manufacturer and obtain from him a shunt to reduce the sensitivity to the required amount. It will also be necessary to obtain a replacement scale with provision for the shorter a-c ranges. A replacement scale will also be necessary if the ohms scale is calibrated for a 4.5 volt battery.

by Maurice  
Findlay

An ohms scale calibrated for a 1.5 volt battery and series adjustment is easily recognised, since the centre scale calibration will be 1.5, 15 or 150.

Of course, if you have a fair understanding of the principles involved, it would be possible to modify the circuit constants to suit out, if you are in doubt, you would be well advised to follow the course we have outlined.

As this article is intended to be largely of a practical nature, we will not attempt to discuss the theory of operation of the instrument at length but a few remarks on the general principles involved will be appreciated by the uninitiated.

## READING CURRENT

The meter movement itself is a current operated device. If, for example, we wished to construct an instrument to read 2 mA full scale deflection with our 1 mA meter, it would be necessary to connect a resistor in shunt (or parallel) with the coil. This resistor must have exactly the same resistance as the coil, in which case half the current will flow through the coil and half through the resistor. You can easily see that, although the meter has only 1 mA actually flowing through it, the scale can be calibrated for 2 mA.

We quoted the above simply because it is an easy example but useful current ranges on a multi-meter for radio work are 1 mA, 10 mA, 50 mA and 250 mA. In the latter case, when the instrument is reading 250 mA there is still only 1 mA passing through the meter, but 249 mA is passing through the shunt resistance.

You will have gathered from this that the value of the shunt resistance is related to the meter resistance. For this reason it is always desirable to obtain correctly-matched shunts from the meter manufacturer or, at least, shunts which are designed to work with a meter of the same resistance as the meter you have on hand.


## VOLTAGE RANGES

The voltage ranges are obtained by placing a resistance in series with the meter movement. The value of the resistor is such that it will allow 1 mA to pass through the meter coil when the instrument is connected across the full-scale deflection (FSD) voltage required. (The value of the resistor is calculated from Ohms law.)

For instance, if FSD is required with 1 volt applied, it can be calculated that the series resistance required is 1000 ohms. Similarly, for a FSD of 1000 volts with a 1 mA meter, the series resistance is 1 meg-ohm.

You will probably be about to point out that we have neglected to allow for the resistance of the meter, which is usually in the vicinity of 100 ohms. However, even on the 10-volt scale this works out at only 1 per cent of FSD, with correspond-

# STANDARD MULTIMETER CIRCUIT

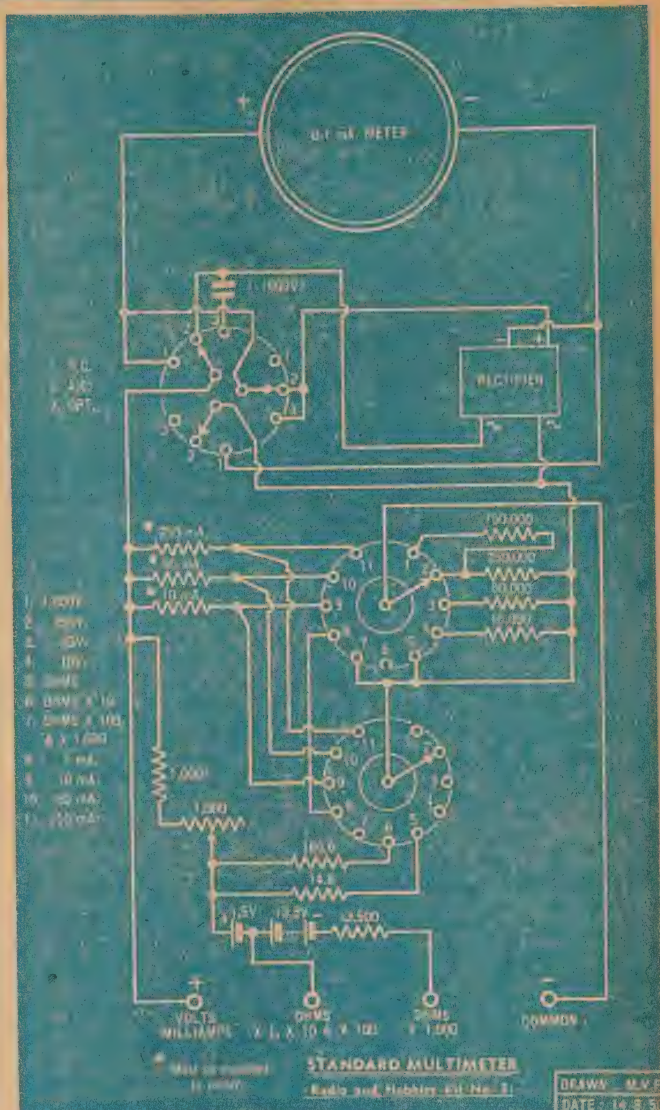

The circuit. Note that the 1000 volt multiplier is actually 4.25 meg. resistors in series. Higher value resistors tend to be unstable.

## PARTS LIST

- |                               |  |
|-------------------------------|--|
| 1 Case (see text).            | 1 .05 meg.   |
| 1 Panel 8" x 7 1/2" x 1/4".   | 1 .01 meg.   |
| 1 1 mA. Meter (100 ohms).     | 1 166.6 ohm.   |
| 1 5 mA. Rectifier.            | 1 14.8 ohm.  |
| 1 2 Bank, 11 position Switch. | 10% RESISTORS  |
| 1 3 Pole, 3 Position Switch.  | 1 1000 ohm   |
| 1 1000 ohm Potentiometer.     | 1 13,500 ohm.  |
| 4 Tip-Jacks.                  | SHUNTS (from meter manufacturer)   |
| 2 Pointer Knobs.              | 1 10 mA. 1 50 mA. 1 250 mA.  |
| 1% RESISTORS                  | SUNDRIES   |
| 4 .25 meg.                    | 1 .1 mfd. 600 volt condenser, 6" length of resistor panel, 3 4.5 volt cells, 1 1.5 volt cell, hook-up wire, spaghetti etc. |



# JOHN MARTIN

announce


their appointment as distributors of—
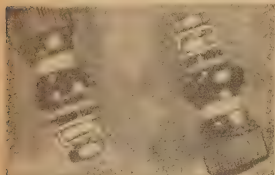
## BELLING-LEE

components



L.623/S Flex Socket Peak working voltage 7000.  
L.623/P Panel Plug.



"L" TYPE.  
L.1004/11.  
12 Standard.  
14 Head only.  
L.1004/21.  
22 High Voltage.



MOTOR BLOCKS  
No. 561. 12-way. 15-amp.



Right-angle Plug, Single Entry. L.614.



MULTI-CONNECTORS  
L.530 7-pin Flex Plug without cord grip.  
L.531 7-way Chassis Socket, single panel.



L.610 4-way non-reversible.  
L.611 8-way non-reversible.  
L.612 12-way non-reversible.  
L.613 18-way non-reversible.

Belling-Lee products are designed and manufactured in accordance with the standards issued by the British Standards Institution and the Radio Component Manufacturers' Federation and, where applicable, to the specifications of the Inter Services Radio Component Standardisation Committee. This means that Belling-Lee components are built to the highest possible current standards. Amateurs are invited to write to us for full data on all Belling-Lee electronic components and accessories that are now available through John Martin Pty. Ltd.

Multi-Connectors  
2 & 3-way Clock Connector.  
L.1091/S Flex Socket.  
L.1091/P Panel Plug.

Loud Speaker Plug with Extension Switch.  
L.1286A Plug.  
L.348 Switch Socket.

Mains Input Connector  
L.1116/P 2-Pin 5 amp. Chassis Plug.  
L.1116/S 2-way 5 amp Flex Socket.

Three-Pin Plug and Socket  
L.1107 Plug only.  
L.1113 Socket Panel.

Three-Pin Plug (Heavy Duty)  
L.525 Plug.  
L.1113 Socket Panel.

Multi-Connectors  
Sealed Unscreened Plugs and Sockets.  
L.563/EP End entry flex plug.  
L.563/ES End entry flex socket.  
L.563/R Right-angle entry flex socket.  
L.563/P 3-way Panel Plug.

Fuseholders  
Single Safety Fuseholder.  
L.1045/C3 with lid retaining clip.  
L.1045/C5, as above, with back connection and brushes.

Twin Safety Fuseholder.  
L.1033/C4 with lid retaining clip.  
L.1033/C3, as above, with back connection and brushes.

Terminals  
("B" TYPE)  
L.1001/1W, L.1001/2W. Standard.

L.1001/21W, L.1001/22W High voltage.

"B" TYPE.  
L.1001/1SW.  
25W.  
L.1001/21SW.  
225W, High voltage.

"H" TYPE.  
L.1005.

"F" TYPE.  
L.309.

"R" TYPE.  
L.1003.  
L.1003/4 Head only.  
P.P. 264 Insulation bush.  
P.P. 366 Insulation washer.

"W" TYPE.  
L.505/10 Fixed head.

"Q" TYPE.  
L.1006.  
L.1006/H 4 B.A. (Head only).  
L.1006/H 6 B.A. (in black or red).

Insulators  
Stand-off Low Loss.  
L.1292, 10,000V. Peak Working.  
L.1277, 5000V. Peak working.

High Voltage Bushing for Chassis or Screens.  
L.1296. 5000V.

Sealed Terminals  
Sealed Insulated.  
L.583.

Glass Seal.  
L.576. 750V., DC. Working at 40,000 feet.  
L.1296. 1500V., DC. Working at sea level.

Glass Seal.  
L.577. 1500V., DC. Working at 40,000 feet.  
L.581. 3000V., DC. Working at sea level.

War Office (No. 4, insulated slotted 4 B.A.).  
L.541 (small).  
L.542 (large).

Turret Lug  
L.592. L.666.

Coaxial Plugs and Sockets  
L.1249 Screened Flex Plug.  
L.1250 Screened Flex Socket.  
L.1264 Screened Chassis Plug.  
L.1267 Screened Chassis Socket.

Line Coupling  
L.616.

Through Chassis Connector  
L.617.

Right-angle Plug Double Entry.  
L.615.

"OZ" Plug Pins.  
L.513 3mm, 10 amps.  
L.514 4mm, 15 amps.  
L.515 5mm, 15 amps.  
L.517 7mm, 40 amps.

Plugs  
Midget Wander-plug.  
L.1019.

"Bowspring" Wander-plug  
L.341

Banana Type  
L.378/3 3mm Plug.  
L.315 0.125in. Socket.  
L.378/4 4mm Plug.  
L.316 0156in Socket.

# JOHN MARTIN PTY. LTD.

116-118 CLARENCE STREET, SYDNEY.

Phone BX5061 (5 lines). Telegrams "Jonmar"







# PICKUP RANGE SEPTEMBER 1950

THE WORLD'S MOST COMPREHENSIVE RANGE OF PICKUPS

EVERY MODEL THE BEST IN ITS FIELD

## HEADMASTER PICKUPS



Type	Output	Frequency Range	Stylus	Particulars	Price
Supplied with: 1 Cartridge Arm 12" 1 each Cartridge Green Red Orange Tonaliser C Multi-Ratio Transformer	45 millivolt 250 millivolt with transformer.	30-18000	Sapphire	Highest quality reproduction of all records. Interchangeable cartridges with sapphire points of correct dimensions. Easy & quick operation of plug-in cartridge. Recognised by experts as the best & cheapest Pickup on the market. COMPLETE	£ s d 10/14/6
				Available separately. Cartridge Arm (12")	1/8/6
				Cartridge Arm (16")	1/13/6
				Cartridge—Green (Standard)	1/8/6
				Cartridge—Red (Wide range)	1/8/6
				Cartridge—Orange (Old recordings)	1/8/6
				Cartridge—Yellow (Microgroove)	1/15/0
				Transformer	2/6/9
				Tonaliser	2/16/0

## THREE-WAY PICKUPS




Type	Output	Frequency Range	Stylus	Particulars	Price
150	150 millivolt	30-16000	Sapphire Stylus	Especially designed to give high-fidelity reproduction of all types of records. Plays standard 78 revs. as well as long-playing (Microgroove) Records (33 1/3 & 45 revs.). Incorporating the Magnetic Cartridge. No. 150. Weight adjustment. Supplied with two styli: BLUE for standard and YELLOW for long-playing records. Beautiful Polystyrene Mouldings.	£ s d 6/7/6

## LIGHTWEIGHT PICKUPS




Type	Output	Frequency Range	Stylus	Particulars	Price
122	.25 Volt	30-8000	Replaceable Sapphire	High Output. Medium frequency range. Ideal for use with standard receivers. Low needle pressure minimising record wear. Finished in florentine bronze.	£ s d 3/13/10
123 (MAGNA)	.25 Volt	30-8000	Replaceable Sapphire	As above, but with one interchangeable Cartridge. Ideal for Commercial or P.A. equipment with quick needle changing or replacement essential.	3/13/10
125	.25 Volt	30-7000	Standard Needles	The Lightweight P.U. using standard size Sapphire, steel or thorn needles.	2/17/-


## AUTO-STOP PICKUPS

	Type	Output	Frequency Range	Stylus	Particulars	Price
	137A	.7 Volt	40-6000	Standard Needles	An amazing new feature: The automatic start-stop device incorporated in the base. This makes it the ideal replacement pickup for any old or heavy pickup (magnetic or crystal). Maximum output in minimum of space. Needle pressure only 40 grams. Beautiful Polystyrene Mouldings.	£ s d 4/0/0


## BANTAM PICKUPS

	Type	Output	Frequency Range	Stylus	Particulars	Price
	130	.3 Volt	40-7000	Standard Needles	Inexpensive, sturdy, reliable. Really good value.	£ s d 2/1/2


## MAGNETIC CARTRIDGE To replace CRYSTAL CARTRIDGES

	Type	Output	Frequency Range	Stylus	Particulars	Price
	150/CART-RIDGE	150 Millivolt.	30-16000	Sapphire Stylus	High fidelity cartridge, fitting most crystal pickups of American, Australian and U.K. manufacture. Supplied with Blue stylus for standard and Yellow stylus for long-playing records. Easy to fit. As incorporated in three-way pickup.	£ s d 3/3/0

## REPLACEMENT HEADS FOR GARRARD CHANGER

	Type	Output	Frequency Range	Stylus	Particulars	Price
	G.1	.25 Volt	30-8000	Replaceable Sapphire	Owners of Garrard Changers from R.C.4 to R.C.70, can easily and without skill IMPROVE their reproduction and preserve their records by using this Lightweight Head. Low needle pressure and all other advantages of Lightweight Pickups. Not suitable for RC 65A or RC 70A.	£ s d 2/15/9
	G.2	.25 Volt	30-7000	Standard Needles	As above, but using standard size Sapphire, steel or thorn Needles. Low needle pressure and most advantages of Lightweight Pickups.	£ s d 2/5/3

## PICKUP HEADS

	Type	Output	Frequency Range	Stylus	Particulars	Price
	112	.3 Volt	45-5000	Standard Needles	Convert your Portable Gramophone into a Record Player simply by connecting the Pickup Head to the Wireless Set.	£ s d 1/13/4
	112/IVORY	.3 Volt	45-5000	Standard Needles	As above, Ivory finish.	£ s d 1/15/1

Leaflets giving full TECHNICAL INFORMATION, Frequency Response, Curves of every Pickup, etc., are available on request from your supplier, and from:

**GOLDRING ENGINEERING (A/SIA) PTY. LTD, 57 H.E. AREA, ST. MARY'S, N.S.W.**

**Phone: St. Mary's 447. After Business Hours, UW6907.**



# BUILDING A STANDARD MULTIMETER

(Continued from Page 67)

banks of the eleven-position switch respectively. As you can easily work out for yourself, the same connections could be achieved by wiring the upper and lower banks of the switch directly together and then running a single lead to each of the shunts. However, if this were done, each of the leads would be effectively in series with its respective shunt.

The same principle is employed in wiring the unswitched side of the shunts. A lead is run from the tip-jack to the shunts and a second lead from the shunts back to the three-position switch.

We admit that the error introduced by not following these wiring precautions would be very small indeed with hook-up wire of normally low resistance, but nobody is likely to object to installing the extra four wires involved.

By the way, the switching system in the meter is so arranged that the effects of contact resistance in the switch are minimised.

## BATTERY LEADS

The batteries for the ohms ranges are mounted in the back of the case, and it will be necessary to install three leads to make the necessary connections to them. We suggest that the leads be firmly anchored to the panel to prevent the wiring being disturbed when the instrument is removed from the case. A small clip for this purpose can be made from a piece of scrap metal and mounted under one of the tip-jacks. Wrap the battery leads with insulating tape before bending the clip to grip the leads, so that there is no possibility of a short-circuit.

Naturally, before you consider the instrument complete you will wish to compare all the ranges with an instrument known to be accurate. However, before doing this, it is a good plan to roughly check all the ranges to make sure that the wiring is correct. An ordinary a-c operated receiver will be of assistance in this matter.

## TESTING

Switch the set on and allow it to warm up. Select the 1000-volt d-c range and place the test prods across the cathode bias resistor of the output valve or the back bias resistor, as the case may be. The meter should give a very slight deflection. Switch to the 250 and 50 volt ranges in turn, and the meter should give increasingly higher readings. The 10-volt range may be roughly checked across a cathode bias resistor for one of the RF or IF stages, or alternatively a torch battery.

Similarly, the a-c ranges can be checked using a convenient filament winding.

Switch to each of the ohms ranges in turn and make sure that, with the test leads shorted, the zero adjuster

will bring the meter to exactly FSD. A few checks with resistors of known value will serve to determine if each range is reading correctly.

In making all these tests, be prepared to disconnect the meter quickly should the needle go hard over past full scale or bang against the stop in the reverse direction, indicating an error in the wiring or a faulty multiplier or shunt.

## PANEL MARKING

Having carefully assembled and wired the instrument, you will prob-

ably not be satisfied to have the positions of the controls indicated by sundry scratches or pencil marks on the panel.

If circumstances permit nothing better, the scale can be marked on a piece of good quality card with Indian ink and mounted under the control locking nuts. However, for a few shillings a jeweller will engrave the panel and the engraving can be filled with white enamel making a very attractive and easy-to-read panel.

Even if you decide later on to invest in more advanced test instruments, your multimeter will always be one of the most useful and versatile on your test bench, and extra care in carefully constructing and finishing it will be well repaid.

# WHO REALLY DISCOVERED ATOMIC ENERGY?

**A**LTHOUGH atomic energy has been very much in the limelight since the bombing of Hiroshima and Nagasaki, it is by no means a new scientific subject, for experiments have been going on in various parts of the world for more than 100 years.

For many centuries scientists have endeavored to discover methods of transmuting the elements. The alchemists endeavored to find methods of changing the atomic structure of base metals, and to turn them into gold, in other words, methods of making one element into another. Mendeleeff discovered the periodic law of atomic structures and graded the elements in the order of valency.

His table showed that there was a common order and gaps in this order indicated that there were missing links, most of which have since been discovered, plutonium being the latest.

## THE ELEMENTS

The elements arranged according to their atomic numbers start off with hydrogen, which is No. 1, and in numerical order there follow: helium, lithium, beryllium, boron, carbon, nitrogen, oxygen, fluorine, neon, sodium, magnesium, aluminium, silicon, phosphorous, sulphur, chlorine, argon, potassium, calcium, scandium, titanium, vanadium, chromium, manganese, iron, cobalt, nickel, copper, zinc, gallium, germanium, arsenic, selenium, bromine, krypton, rubidium, strontium, yttrium, zirconium, niobium, molybdenum, ruthenium, rhodium, palladium, silver, cadmium, indium, tin, antimony, tellurium, iodine, xenon, caesium, barium, lanthanum, cerium, praseodymium, neodymium, samarium, europium, gadolinium, terbium, dysprosium, holmium, erbium, thulium, ytterbium, lutecium, hafnium, tantalum, tungsten, osmium, iridium, platinum, gold, mercury, thallium, lead, bismuth, polonium, niton, radium, thorium, protoactinium and uranium.

These elements may be arranged

in order of valence or valency, which is a property possessed by elements or radicals of combining with or replacing other elements or radicals in definite and constant proportions. Thus valency is the degree of this property, commonly indicated by the number of monad elements, represented by hydrogen, with which the atom or radical can combine or which it can replace. It, of course, varies with different elements.

## COMBINATION

Thus hydrogen has a valence of 1 and is called a monad; oxygen has a valence of 2 and is called a dyad; bismuth has a valence of 3 and is called a triad; carbon has a valence of 4 and is called a tetrad. Certain elements have more than one valence; tin, iron and sulphur, for example. Rearranging the elements we find that they group themselves into monovalents, divalents, trivalents, tetravalents, pentavalents, hexavalents, &c.

It is not surprising that various countries are claiming the credit for atomic energy, but investigation will show that beyond all doubt it is due to Great Britain alone. It was John Doulton, an Englishman, who first expounded the idea of atomic structure of matter, but it was the work of Clerk Maxwell, who toward the end of the last century propounded the mathematical basis for the theory of high-speed particles emitted by atoms, which really set the scientific world to work.

J. J. Thompson, in 1898, carried the work of Maxwell further by propounding the idea that the atom was made up of electrons. Later Professor Einstein produced the equation relating mass to energy, and it is upon this equation, first published in 1905, that the principle of atomic energy rests. It was not until the end of the first world war that Lord Rutherford, at the Cavendish Laboratory, Cambridge, conducted his famous experiments in splitting the atom.

—F. J. Camm, in *Practical Mechanics*.

# TRADE REVIEWS AND RELEASES

## MAGNAVOX SPEAKER—MODEL 525


Latest addition to the Magnavox "Centre Pole" series is the model 525 illustrated below. Intended for mantel and portable receivers, it has a 5½-inch cone and a housing that is comparable in overall dimensions to standard 5-inch types.

**S**PECIAL feature of "Centre Pole" series is that the complete permanent magnet structure is removable, thereby simplifying and cheapening cone repairs, &c.

The speaker has a 1½ in diameter voice coil with a nominal impedance of 2.7 ohms—a standard figure for all Magnavox speakers. The main cone resonance is quoted as 120 c/s but it is well damped and cone movement is smooth down to at least 50 c/s. At the top end, and with the standard midget transformer in circuit, the response is well sustained to 4000 c/s, sensitivity is excellent.

Retail price for the model 525 is quoted as 33/8.

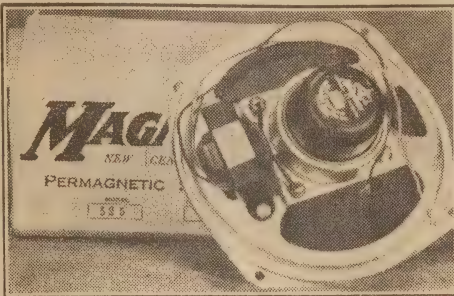Interstate distributors for Magnavox products are as follow: Bris-



bane Irvines Ltd. and Edgar V. Hudson Ltd., Sydney. George Brown & Co., Pty. Ltd., John Martin Pty. Ltd. and Bloch & Gerber Ltd., Melbourne, Warburton Franki, Melbourne, Ltd. Adelaide, Gladiola Co., Perth, Ronfred & Co.

(Magnavox Pty. Ltd., 61 Dowling St., East Sydney, NSW.)

## Book Review

"SCREW THREADING AND SCREW CUTTING" by "DUPLEX." Paper cover, 88 pages, Australian price 5/6 approx. plus postage.

Plenty of clear, easily understood diagrams are used to assist the presentation of this little book, which contains a great deal of practical workshop information.

Chapter 1, deals with the various types of screw threads giving their specifications and particular uses. It goes on to discuss the use of the thread tables.

The remaining five chapters emphasise the practical aspect of screw threading methods and screw threading equipment, plenty of illustrations from actual projects being given. Tables of standard threads with clearance and tapping drill sizes are included in the appendix. They cover most of the British, American and Metric threads likely to be met.

"IN THE WORKSHOP" Volume 2, also by "DUPLEX," hard cloth cover, 151 pages Australian price 13/3 approx. plus postage.

This volume is also a practical workshop guide being a selection of articles from "The Model Engineer." Detailed descriptions of the construction of a number of useful workshop devices are given, together with information on the use of a number of hand and machine tools. Two of the nine chapters deal with Lathe Filing-rests and an Auxiliary Bench Vice respectively while one chapter is devoted to Hacksaws and Hacksawing.

(Our copies of both books from the publishers, Percival Marshall and Co., Ltd., 23 Great Queen St., London WC2.)

## CHANGE OF NAME

**T**O be more in keeping with the nature of current activities, Radio Equipment Pty. Ltd. is now operating under a new name—"University Graham Instrument Co." Located at 5 North York Street, Sydney, the firm specialises in the manufacture of radio and electrical test equipment.

## MANLEY ROTO-TRIMMER

Latest release by Amplion (A'sia) Pty. Ltd. is the Manley Roto-Trimmer—a labor saving device for the professional or home gardener.

**T**HE ROTO-TRIMMER is designed to make light work of the tedious task of cutting lawn edges

Retail price of the Roto-Trimmer is £22/10/- exclusive of the transformer or battery. It is available on immediate delivery. (Amplion (A'sia) Pty. Ltd., 36-40 Parramatta Road, Camperdown, NSW).



and other inaccessible spots where it is impossible to use the normal type of mower.

An enclosed electric motor spins a high speed cutting blade past a coarse "comb," as seen in the accompanying close-up photograph.

The motor operates at 32 volts for complete safety. For a-c operation it is powered from a step-down transformer, while a mobile battery can be used as an alternative where power is not available. Power consumption is approximately 130 watts.

## OTHER ITEMS OF INTEREST:

● A new catalogue is available from the Aegis Manufacturing Company, listing in attractive fashion, their current lines. The catalogue illustrates and lists the various coils, coil kits, I.F. transformers, foundation kits and sundry other small items. Of special interest is mention of a projected push-button tuner. The catalogues are available for the cost of the postage, amounting to 9d. (Postal address: 208 Lit. Lonsdale St., Melbourne, C1.)

● Messrs. J. H. Magrath and Co., advise that a new Super Light-

weight Connoisseur pickup is available which features three interchangeable heads for standard and microgroove, recordings. Needle point pressure is quoted as 10/12 grams for standard records and 5/7 grams for microgroove discs. The frequency range is stated to be 25-15000 c/s within plus or minus 2db. A 25 ohm model gives 10 mV. output direct or 300 mV. from a step-up transformer. A 400 ohm model is also available. (J. H. Magrath, 208 Little Lonsdale St., Melbourne, C1.)



# 

## 

AN EFFICIENT ELECTRIC MIXER AT A REASONABLE PRICE.



12 Months Guarantee

Exclusive Patent Beaters


Complete with 2 Mixing Bowls and Recipe Book.

PRICE  
£15-19-6
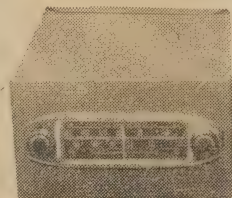
## 

COMPLETE WITH ALL PARTS. VALVES, SPEAKER, DIAL, COILS, ETC.

Fit this 5-Valve Receiver to any model car  
Chrome aerial extra depending on type of car.  
£18/18/-



Price £120

## 

Complete with microphone, amplifier, and two speakers, enclosed in an attractive carrying case, this unit is capable of performing the following functions.

- (1) RECORDING FROM MICROPHONE
- (2) RECORDING FROM RADIO OR PICKUP
- (3) PLAYBACK FROM RADIO
- (4) PLAYBACK FROM COMMERCIAL RECORDINGS
- (5) A SMALL PUBLIC ADDRESS SYSTEM

ON DEMONSTRATION AT  
100 CLARENCE ST.

£120



Easily operated by non-technical users

## 

## 

## 

Acclaimed overseas as the greatest postwar development in pick-up design.

10 inch, 12 inch and 16 inch discs.

Interchangeable head for microgroove.

### 

Extremely high output — permanent sapphire automatic bass boost — unbreakable crystal. Needle pressure less than 1/2 ounce.

LIST PRICE — £4-17-6



Battery Charger Kit. Homecrafts 6 volt 4 amp. Battery Charger Kit. Kit includes 6 volt 4 amp. English Selenium Rectifier, transformer, black crackle finish metal case, 2 terminals and hook-up wire. Complete kit, as illustrated, only £4/10/-. 12 volt 2 amp. Kit, 5/- extra.

## 



"Collaro" Rim Drive Electric (A.C.) Gramo motor, complete with Crystal Pick-up, £6/-/-. Above Motor, complete with Magnetic Pick-up, £5/8/6.

## 

We can supply everything in radio . . . Our staff is trained to attend to your special requirements.

All Orders are  
Promptly Despatched

# 

DIVISION OF ELECTRONIC INDUSTRIES LTD.

98-100 CLARENCE STREET, SYDNEY. Also at 26 Hunter Street, Newcastle.

MAIL ORDERS: Box 5000, G.P.O. SYDNEY. PHONE: BX4451.

## M.S.P. JENSEN LOUDSPEAKERS

A special agreement between Manufacturers Special Products Pty. Ltd. and the Jensen Company of America has resulted in the release on the Australian market of speakers carrying the well known "Jensen" label.

The speaker illustrated below is referred to as M.S.P. Jensen type 12P36. It is nominally a 12" unit and requires a baffle hole of 11" diameter. Overall depth is 6".

These speakers incorporate for the first time a special "Hawley" cone and an improved dust-proof "breathing" type suspension. Properly baffled, they are credited with a power handling capacity of 15 watts, making them suitable for use in large console receivers or multiple-speaker amplifier systems.



An Alcomax 11 magnet is employed in a special magnetic circuit giving a flux density in the air gap of 10,000 gauss. All steel parts are cadmium plated and the transformer is a wax-immersed insulated core type.

For purposes of identification, the speakers are sold under a composite type number which indicates both the speaker type and the transformer impedance. Thus type AU50-12P36 is a 12P36 speaker fitted with a 5,000 ohm transformer.

Voice coil impedance is 6.5 ohms and a variety of transformers are available to meet differing load requirements. The speaker retails for £7/6 complete with a "single-ended" transformer, or for 70/- with a push-pull or line transformer fitted.

Main cone resonance is quoted as 17 c/s but samples submitted for test averaged nearer 100 c/s. At the top end, the response appeared to hold up well to about 5 kc., with a gradual taper thereafter.

Jensen speakers are handled by Trade Houses throughout the Commonwealth. Trade enquiries to Manufacturers Special Products Pty. Ltd., 47, York St., Sydney.

## MAKE YOUR OWN RECORDS

Of Radio, Music, Speech, Orchestral and Vocal Items

Make your own records with the American "Green Flyer" Recording Unit—uses standard 10" discs. Suitable for recording radio programmes, speech, vocal and orchestral music. For full particulars write for technical data sheet.

Recording and play back unit as illustrated £25/-

4 valve amplifier with matching transformer £20/10/-

Carrying Case (leatherette covered) £5/-

Microphone £5/2/6

These units can be supplied mounted with speaker, recorder and amplifier as a self-contained unit at £59/10/-.

Recording-sets may be made and played back independent of any other equipment.



## £31/- FOR THIS 8-VALVE DUAL-WAVE RADIO

Here's Value only to be found at Radio House. This ready-wired and tested chassis is complete with valves and 12" Rola Speaker.

Complete in every detail, it's easily fitted into your radio cabinet and is supplied with a polished wood front panel. Ideal for overseas short-wave reception, fitted with Phono pick-up terminals and has tone controls for treble and bass boost. DIMENSIONS: 16" w. x 10 1/2" d. x 9" h. Panel 16" w. x 10" h. Weight, packed in crate, 63lbs.

Front view with panel attached.

With "Plessey" Record Changer .. £39/10/-



MAIL ORDER DEPT. GOODS SENT  
C.O.D. RAIL OR POST.

## The New 1951 High Gain 4 Valve Midget Amplifier

### Specifications

240 volts A.C. Valves: 6AU6, 6AU6, 6AQ5, 6X4, 4 watts output, overall size 7" x 4" x 5 1/2" high, suitable for both microphone and phono pick-up amplification, equipped with volume control, tone control and change-over switch for microphone to pick-up. Weight 5lbs. without speaker, with 8" speaker 7lbs. price, £11/17/6, with 12" speaker 9lbs. price, £13/4/6.

## 240 VOLT A.C. AUTOMATIC RECORD CHANGER

Reduced from £18/10/-

to £10/17/6

It's a Special Purchase — but hurry before they go!

The Plessey British-made record changer is second to none. Special features are: repeat and reject buttons, automatic cut-off after playing last record—will take eight records, either 10" or 12" grouped or intermixed. This unit is also available as a portable phonograph complete with 4 valve amplifier and 8" speaker mounted in a leatherette covered carrying case, being self-contained, it can be plugged into any 240 volt A.C. power socket and used independent of radio; suitable for use with a microphone, size 17" x 17 1/2" x 9" high, £28/17/6, plus freight.



### THIS MONTH'S SPECIALS

- "Marmac centre drive variable speed 240 volt electric phonomotor, 78 R.P.M. 12" turntable, £4/- plus freight.
- "General Industries" American synchronous type phonomotor, 240 volts A.C. £4/10/- 78 R.P.M.
- Dual speed model 33 and 78 R.P.M.—£16/12/6.
- Triple speed 33, 45 and 78 R.P.M.—£13/10/-.
- "Philips" neon pocket tester, screwdriver type, tests A.C. voltage, 110 to 750 —7/6 each, plus postage.

# RADIO HOUSE LTD.

2 STORES

296-298 PITT ST.  
Opp. Neon Board

6 ROYAL ARCADE SYDNEY.  
Opp. Queen Victoria Bldgs.





# A READER BUILT IT!

Gadgets and circuits which we have not actually tried out, but published for the general interest of beginners and experimenters.

## BETTER BASS FROM RADIOGRAM CABINET

Many readers, desiring better bass response, find they have not the room to accommodate a vented enclosure, either inside or outside the normal cabinet. Mr. I. W. Emmerson, of 17 Frederick St., Concord, NSW, describes a system of partitions which, when added to his cabinet, gave a worthwhile improvement in results.

**MR. EMMERSON** purchased the cabinet, which was found to be quite well built, but not very successful as a baffle. This was due in part to a light baffle board and also to the natural limitations of any open-backed cabinet. Results fell far short of those obtained from a vented enclosure, which however, could not conveniently be located in the room, in addition to the cabinet.


Accordingly the first step was to install in the cabinet a large baffle board made up from solid stock and over an inch thick. Excellent timber for this purpose can be obtained from large packing cases, particularly those coming from European ports.

### NEW Baffle

Addition of the heavier baffle improved matters somewhat but the results were still not acceptable, or at least not to be compared with those obtained using an enclosure.

Measurement of the cabinet showed that nearly eight cubic feet of space was available but a good deal of this would be required to house the amplifier, the tuner, the record players, record compartment and so on. Allowing also for the bulk of any damping material which might be included, there was just not enough room for an adequate built-in vented enclosure.

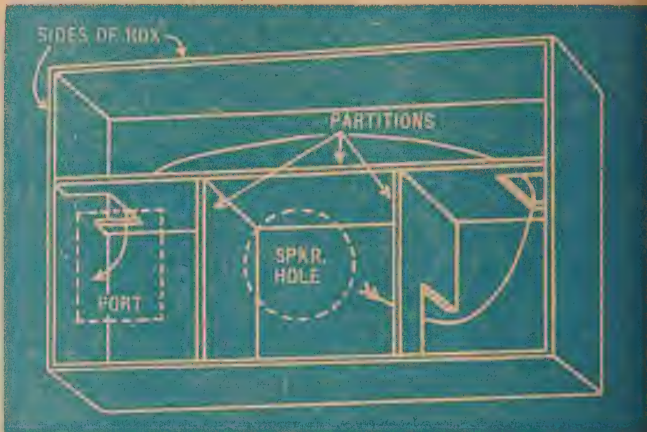Accordingly, a different approach altogether was adopted, aimed at leading the back wave from the speaker through a longer and more heavily damped return path, thereby lessening its interference with direct radiation from the front of the cone. The nature and position of the baffle plates was simply intended to satisfy this basic idea, rather than to satisfy any particular design data.



Whether by good luck or good management, the net result is much more acceptable than that originally obtained from the untreated cabinet.

The exact procedure for the construction will vary with the materials and facilities available but Mr. Emmerson built the complete speaker housing as a unit which was then fitted into the cabinet.

The timber used throughout was 1 1/8-in pine which was solidly braced and all permanent joints sealed with gasket cement and made firm with long nails. The removable bottom panel was sealed with felt and attached by means of long screws. The assembly as a whole is thus substantially airtight, except for the designed return path, and it is a tight fit inside the cabinet. Screws and steel brackets hold it firmly in place.

### VENT AREA

All vents were made equal to 0.8 of the speaker cone opening—a figure suggested by specifications for vented enclosures.

On test, with a signal supplied from a frequency disc, Mr. Emmerson reports the response as being smooth down to 70 c/s. which is the approximate cone resonance of the 12in speaker used. It tapered gradually to 50 c/s, then fell away sharply to 35 c/s. While this is not as good as can be expected from a heavy speaker in an ade-

quate baffle, it showed up as a marked improvement on the open-backed cabinet arrangement.

Incidentally, it was found desirable to remove a "tone control" condenser from the plate of the output valve in the set to improve the high frequencies and give a better overall balance to the reproduction. Extended bass, with severely limited high notes tends to give a rather muffled result.


The outside dimensions of the original box measured 28in x 14in x 20in but these figures have no special significance apart from the fact that they worked in with the original cabinet.

### EXPERIMENTS

For readers who may care to experiment along these lines, the idea behind the suggestion is basically to lengthen the return path for the sound waves from the rear to the front of the cone. While it helps to keep the path as long as possible, the cross sectional area of the path at any point should not be less than the cone area, otherwise it will tend to resonate the sound waves inside the inner compartments only.

Some acoustic damping may be an advantage, particularly in the inner compartments.

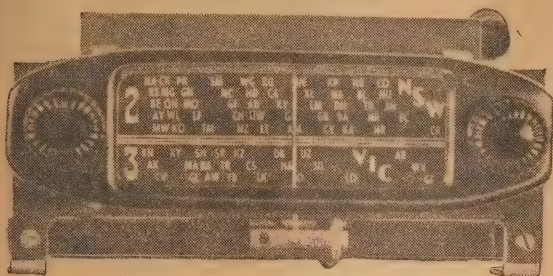If the sides of the cabinet are of at least 3/4 in timber, they could serve as the sides of the box.



Ask your Radio Dealer to  
show you this new unit

## MSL-48

Available with calibrated scale as shown, or marked in kilocycles for car radios.

With calibrated scale this dial is very suitable for use with new miniature valves, for use in very small mantel receivers. It has an attractive two colour scale.

The escutcheon is cast brass, and is available in florentine bronze, or satin chrome finish.

Overall Dimensions: 5½ in. x 2½ in.

Escutcheon: Vision 3-3-8 in. x 1-1-8.

## THE EFCO MANUFACTURING


CO. PTY. LTD.

ARNCLIFFE, N.S.W.
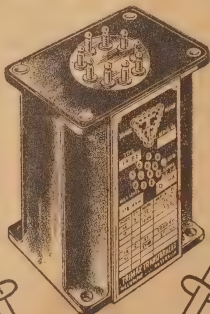
## TRIMAX

★ Selected by Govt. Depts. &  
leading Radio Stations.

"TRIMAX" high fidelity, low level transformers feature excellent frequency characteristics, low distortion, minimum transfer of longitudinal currents, low hum pick up. Also available in high permeability multi shielded case for extra low level operation.



With improved production facilities most types are now available from stock. A standard range sufficient for most applications is listed in leaflet 47-1. If you do not have a copy please write.

## Transformers

### TRIMAX TRANSFORMERS

CLIFF & BUNTING PTY. LTD.

CHARLES ST. NTH. COBURG

Telegraphic Address 'TRIMAX,' MELB.

Q'LAND  
Chandlers Pty. Ltd.

N.S.W.  
Radio Equipment  
Pty. Ltd., John  
Morlin Pty. Ltd.

TAS.  
W. & G. Genders Pty. Ltd.

STH. AUST.  
A. G. Healing  
Ltd., Gerard and  
Goodman Pty. Ltd.,  
Radio Electric  
Wholesalers Ltd.


W.A.  
Nicholsons Ltd.,  
Atkins (W.A.) Ltd.,  
Carlyle & Co. Ltd.



RED  LINE
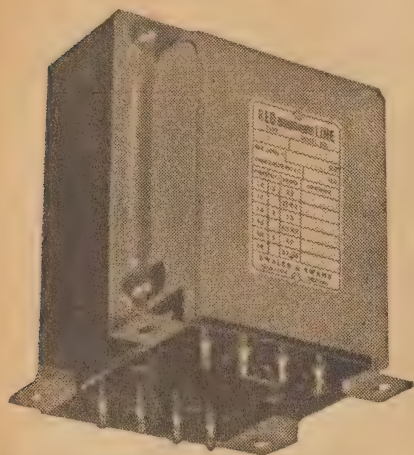
# Matched Transformer Kits

for the Williamson Negative Feed back Amplifier



As originally designed by  
Mr. D. T. N. Williamson in "Wireless World,"  
April and May, 1947.

## ● OUTPUT TRANSFORMER

Primary Impedance 10,000 Ohms 807 (T) P.P.  
Secondary Impedance as required—see panel.\*

FREQUENCY RESPONSE: Linear within 0.2 db.  
20 cps. to 30,000 cps.

PRIMARY INDUCTANCE: (at 5V A.C.\*) not less than  
100 Henries.

LEAKAGE INDUCTANCE: (at 5V A.C. 1000 cps) 17  
Millihenries.

INSERTION LOSS: 0.4 Decibels.

## AF Series

### Output Transformers\*

10,000 ohms p.p. plus 34 db	
500 & 125 ohms	AF 10
8 & 2 ohms	AF 8
12 & 3 ohms	AF 3
15 & 3 ohms	AF 15

## CONDENSER INPUT POWER SUPPLY

	Type No.	Price
Output Trans	AF*	127/9
1 P/Trans	20453	93/2
1 Choke	201515	36/2
1 Choke	50825	30/3

# RED LINE EQUIPMENT PTY. LTD.

TRANSFORMER ENGINEERS

City Office:

157 Elizabeth St., Melbourne. MU6895

Workshop:

2 Coates Lane, Melb. Central 4773




Distributors:

S.A.—Gerard & Goodman Ltd.  
N.S.W.—United Radio Distributors Pty Ltd.  
Q'ld.—A. E. Harold, B. Martin Pty. Ltd.  
Vic.—All Leading Wholesalers.

## A GUARANTEE OF DEPENDABILITY

# SUPER-FAST, VERSATILE BOMBER

MARTIN XB-51 BOMBER

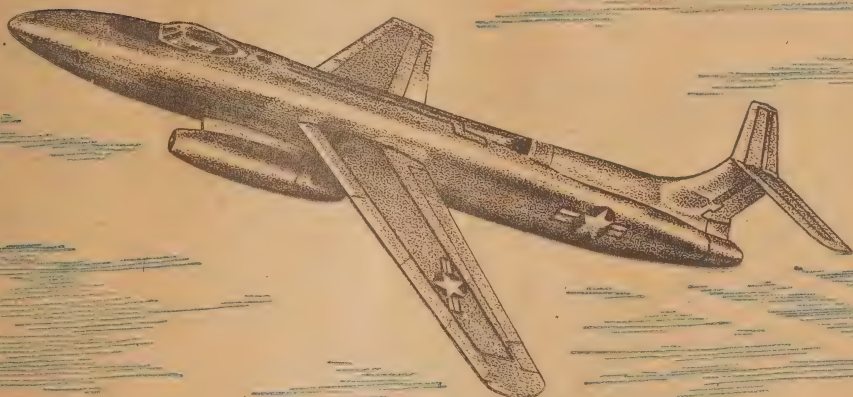

Described by its builders as "the US Air Force's first postwar plane specifically designed for supporting ground forces," the Martin XB-51 is a three-jet bomber of sleek outline. Following the design style that has been set for high-speed jet combat aircraft, the XB-51 features wings which are drastically backswept. Of thin section, the wings spring from the fuselage about half-way along its length and in slightly higher than mid-wing position.

ONE of the main roles visualised for the aircraft is that of hampering enemy supply lines and installations. It is a versatile machine, however, and is capable of very high speeds as well as having high manoeuvrability, so that it should not find itself at a disadvantage in air combat.

Power comes from three jets, one mounted on a pylon on each side just out from the base of the fuselage, and the third in the tail. The intake for the fuselage jet is on the top of the fuselage forward of the tail root. The outlet is in the extreme tail.

## T-SHAPED TAIL

This arrangement has made necessary a specially-designed T-shaped tail unit, with tailplanes mounted on the top of the fin and showing slight dihedral.

Another feature that has been revealed is tandem landing-gear. Many other installations on the XB-51 are still secret, however.

The designers, the Glenn L. Martin Company, of Baltimore, have stated that the XB-51 represents the product of co-ordinated studies by the firm's engineering team covering electronic, aerodynamic, metallurgical research, and servo-mechanism experts.

The great surge of power available from the three jet motors cuts the takeoff runs, and faster starts would make it possible for the XB-51 to be operated from small combat-area fields.

To cut down landing run, the aircraft has a great parachute stowed which may be released at the pilot's discretion. This form of parachute brake had already been tried successfully on Boeing's Stratojet B-47.

Little has yet been heard of the XB-51, but it is clearly an aircraft destined to play a specialised and important role in the US Air Force's programme of preparedness.

It is one of the new pacemakers of military aircraft.

## Turbo-prop Convair

CONSOLIDATED VULTEE are almost ready with their new turbo-prop Convair. Almost identical with the 40-passenger Convairs now long in service except for the power plant, it will be equipped with two of the new Allison T-38 twin turbo-prop engines. Old Convairs can be easily fitted with the new engines.

The engine is said to be the most powerful propeller-type engine ever cleared for flight. It develops two horsepower per pound of weight.

Turbo-prop planes have a permanent place in the future, LaMotte T. Cohn, president of Convair, recently declared. They are the logical step in airline progress because the vast public investment in airports, airways and traffic control systems is geared to propeller-driven planes. The new planes will fit neatly into today's traffic pattern because fuel economy is such that planes can carry ample reserves to meet government requirements.



# EXCEL ————— KIT SETS


KIT No.

2

COMBINES EFFICIENCY  
WITH  
ECONOMY & SIMPLICITY

The complete Set to the last Nut and Bolt  
and 12" Permag Speaker.


(NOT INCLUDING BATTERIES)

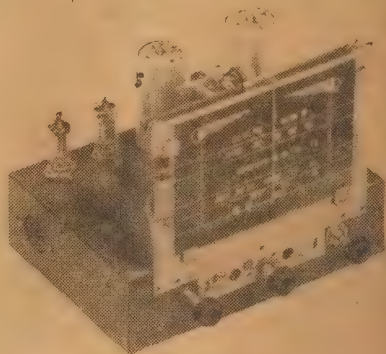

£11/17/6

WIRED & TESTED £14/2/6

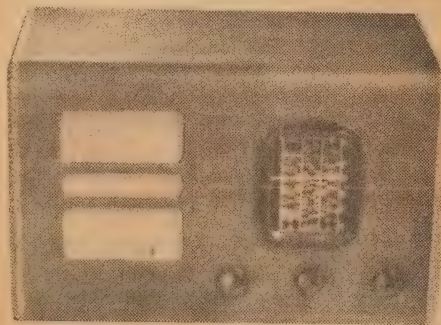We will be pleased to supply batteries if required, but distant patrons should remember that they would add considerably to freight charges.



MANTEL VERSION

INCLUDING CABINET AND 6" SPEAKER

£13/2/6

WIRED & TESTED

£15/7/6

R. & H. KIT No. 1

5 VALVE A-C

KIT COMPLETE TO LAST NUT &  
BOLT, INCLUDING 12" SPEAKER

£13/17/6

Mantel version, including cabinet as  
above and 6" speaker --- £15/2/6

Dual Wave Version --- £14/12/6

Dual Wave --- £15/17/6

Wired and Tested, £2/10/- extra.

GET OUR QUOTE FOR ALL R & H CIRCUITS

PHONE  
LA1604

**EXCLAIR RADIO**

PHONE  
LA1604

136 VICTORIA ROAD, MARRICKVILLE, N.S.W.

# RADIO CONTROL OF MODEL AIRCRAFT

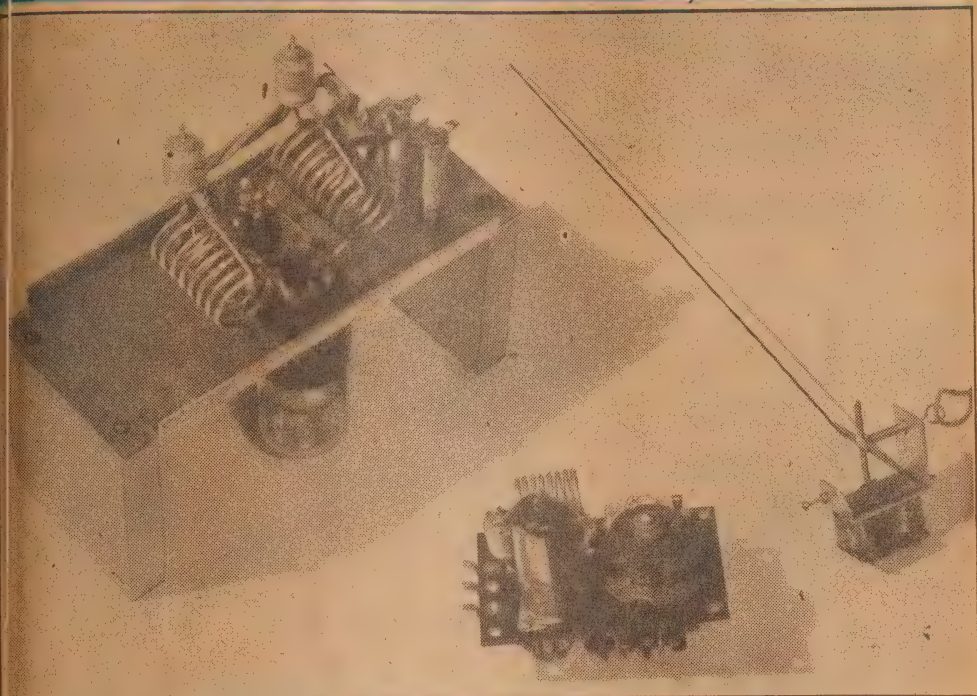


Fig. 4.—Transmitter, Receiver and Actuator of the simplest sequence system.

The author of this most comprehensive series of articles has been engaged for some time in radio control investigation for the CSIRO's Radiophysics Division and is well qualified to discuss all its aspects. The articles have particular value in that the same general principles are applicable to many types of models.

RADIO control of model aircraft is an absorbing subject, and apart from the fact that remotely-controlled models are used as targets for military practice and for aerodynamic and meteorological research, the experienced aeromodeller can with comparatively simple equipment, enjoy this fascinating extension to his hobby.

## EARLY HISTORY

Claims over the years have been made, but it is generally agreed by competent observers that 1934 saw the first successful application of radio control by the Americans during their National Model Airplane Competition that year. Strangely enough, it was an Australian radio amateur, the late Ross Hull, then resident in America, who introduced the rubber drivers' escapement, an ultra lightweight control device which contributed much to the success of that time, and today his device is still considered highly satisfactory for preliminary work.

In latter years, of course, the availability of miniature valves, motors and components, plus new control techniques developed during and since the war, have emphasised further the possibilities of very small and reliable equipment. From inquiries already received, it is evident that the radio amateur and the aeromodeller are both very interested, in what is to us, in this country, something new.

## RADIO KNOWLEDGE

It would be true to say that it takes radio people to build radio gear and aeromodellers to build successful flying models. As each will need the other for technical assistance, members of both hobbies should get

together for their mutual benefit, for successful radio control will require our very best efforts.

Although almost every other country is using different transmitter frequencies and input powers, the conditions for Australia have been very definitely laid down by the Wireless Branch of the Postmaster-General's Department, and it is strongly advised that intending experimenters obtain the necessary permit to operate.

## THE MODELS


As this is a discussion of the radio requirements of controlled flight, the model will be dismissed by saying that it must of course be capable of lifting the radio equipment, and should have already proved itself a ~~safe~~ flyer. Most models have sufficient stability built in, and are trimmed to climb under power and glide with the engine off, therefore rubber movement alone will provide directional control, which, after all, is the

by GIL  
MILES



# Maxwell's Radio

## ENGLISH CRYSTAL PICK-UPS

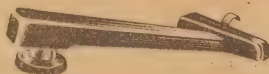

- \* Needle pressure 1½oz.
- \* Wide frequency range.

\* New type needle fitting which obviates damage to crystal if pick-up receives a direct blow. **29/6**  
ACOS G.P.10



5 VALVE A/C D/C  
10½" x 6½"

## CHASSIS

Complete with ROLA SPEAKER.  
Ideal for that built-in job. **£13/10/-**

## REPEAT BARGAINS — AFTER STOCKTAKING CLEARANCE


### MARMAC MOTORS



Automatic stop and start—12-inch turntable—220-240 volt input—speed regulator—for all types of pick-ups—brand new—boxed and guaranteed—induction motor:—

**79/6** Special Quote for lots of six or more  
TRADE ENQUIRIES INVITED

### GRAMO MOTORS

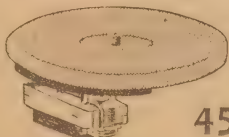


Well-known English make, 220/250 Volts. Complete with turntable

**45/-**

### POWER TRANSFORMERS

40MA 275/275

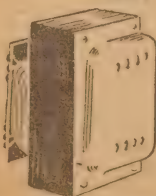

**17/6**


### Meter Rectifiers

(0-5 Mill)

Ideal for Multi-meters. Every rectifier pre-tested and guaranteed to specification.

**15/11 ea.**


While they last.

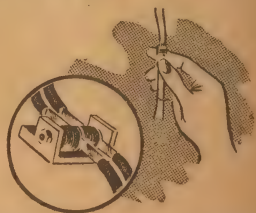

### Veneer CABINETS

Attractive finish  
7½" H. x 7" W. x 11"

**19/11**

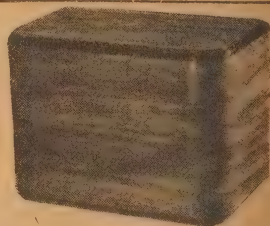

### English Dulcic Microphones


With inbuilt transformer. Fits any type radio. Easy to connect.

**5/11**

Battery 2/5 extra.
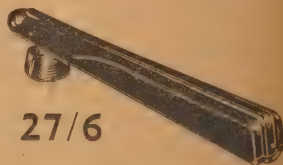
### YOUNG ATOM

Magnetic Pick-ups, Needle Pressure 1½ozs. Output at 1000 C.P.S. of .5 Volts R.M.S.



**27/6**

## MAXWELL'S RADIO

48 ELIZABETH ST., MELBOURNE. CENT. 4913

Same Day Despatch

Add Postage to All Amounts

primary purpose of adding radio control models from 5ft to 10ft wing span indicated, as wing spans under tend to produce a flit rather than a flat.

Rudder control easily tops the list what to control, with engine speed cut off next. Ailerons can also be used to produce a turn, but they are as easy aerodynamically or mechanically to set up as a rudder, will be placed third on this list.

Fourth and last are the elevators. Less very precise and instantaneous control is available, elevator control is a danger, particularly when the model is near the ground.

The fact that radio can be made lower wheels, flaps, and work any other gadgets is of secondary importance to the newcomer, and usually leads to complicated arrangements which do not necessarily contribute anything worthwhile.

This article, then, is intended as a very brief review, rather than a comprehensive survey of equipment used over the years, with a look at most of the known control systems, as well as a description of some experimental gear made by the author over the last 20 years.

## ESSENTIAL PARTS

Any radio control system can be reduced to three essential parts, the transmitter, usually on the ground, which radiates the control signals, and in the model, the receiver, which picks up the signal and passes it on to the actuator, which does the required work, such as moving a control surface, changing the engine speed, and so on.

The equipment used by the early experimenters certainly showed a variety of ideas. Transmitter powers ranged from 5 watts to 50 watts, and frequencies anywhere between 3 mc/s and 60 mc/s.

Some very elaborate set-ups have appeared using telephone dial type control boxes on the ground, and complicated selector switches in the model.

In one case up to four transmitters and receivers were used, one for each control function. They all had the same idea, however, and that was to operate a sensitive relay in the model's receiver, whenever the control signal was transmitted. The relay contacts usually connected into a circuit some form of escapement, either rubber or motor driven, to move the control surface.

## RECEIVER

The receiver operating on 3 mc/s used the well-known oscillating detector. With the transmitter "on," the resultant audio beat note from the detector was passed through an amplifier valve to an over-biased relay valve, the increase in anode current with signal, closing the control relay.

This method of detection proved unstable, so the super-regenerative detector, known for its extreme sensitivity and having other advantages for this work, made its appearance, and has formed the basis for most receiving systems since.

The super regenerative method of

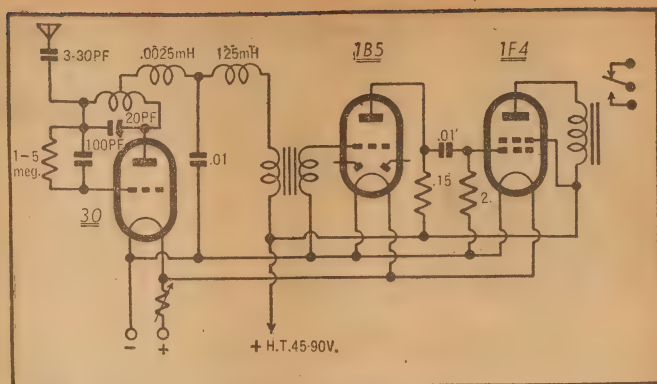


Fig. 1. — Carrier operated super-regenerator for 60 mc.

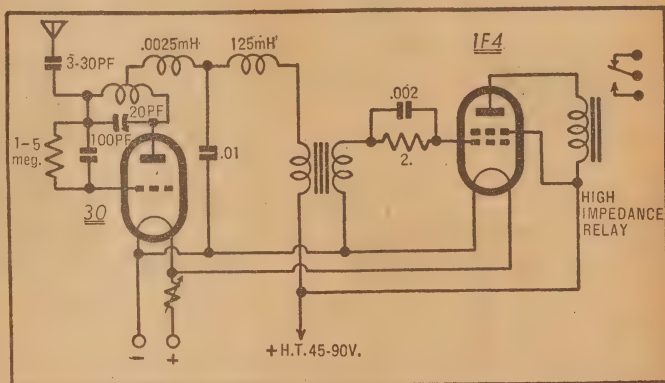


Fig. 2. — Tone operated super-regenerator for 60 mc.

detection produces a large quench current, as it is commonly called, "hiss" voltage, which can be heard if a pair of headphones are connected into circuit.

In the early receiver circuit shown in fig. 1, the hiss voltage is used for control purposes. Amplified, it is used to bias the following relay valve to minimum anode current. With an incoming signal (transmitter on), the hiss stops and the relay valve anode current seeks its static value, the resultant current change operating the relay.

Another early system made use of an audio tone, as modulation of the carrier for control purposes. The

receiver used with this type of transmission is shown in fig. 2. It consists of a super regenerative detector followed by a relay valve, the rectification of the modulation by the relay valve, providing the required anode current change.

The simplest radio control system used today still makes use of the super regenerative detector, but the relay is connected directly in its anode circuit. Adjustments are such that, with the detector valve idling (carrier off), the anode current is sufficient to hold the relay closed. With the transmitter "on," however, the detector anode current can be made to drop as much as 2.0 mA, allowing a held-up relay to drop out.

## SPECIAL VALVES

The Raytheon Valve Co. of America developed many years ago the RK62 especially for radio control; a miniature version, the RK61, is a later edition. A circuit diagram using either of these valves is shown in fig. 3.

An English sub-miniature valve, the Hivac XF91, with similar characteristics to the two Raytheon valves, has just made its appearance.

Known as gas triodes or thyratons, sufficient anode load must be used to limit the anode current to not more than 2.0 mA.

In the absence of an incoming

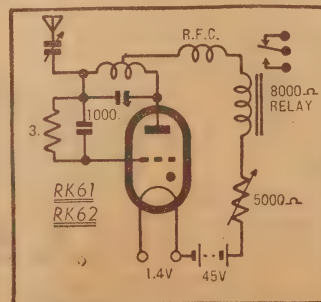



Fig. 3. — Thyatron self quenching detector.




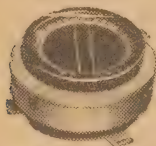
### COMPASS

Liquid Damped, Card Type. 6 1/2" dia. x 3 1/2" deep, fitted with large viewing prism, ideal for small craft, etc., for normal navigation and also taking bearings. £6/10/-



### COMPASS, TYPE P.8

5 1/2" dia. x 2 1/2" deep accurate Aircraft type navigation compass. Reconditioned 27/6

Vic., 2/-; N.S.W., S.A., Tas., 3/6, Qld., W.A., N.T., 5/-.



### HYDRO-METER

For Temperature and Humidity readings, as supplied to the Air Force. No Home, Farm, Factory or Dairy should be without one of these. 19/6

Postage and Packing: Vic., 1/6; N.S.W., S.A., Tas., 2/-; W.A., Qld., N.T., 2/6.



### BLOWER MOTORS

Complete with fan and approx. 1-10th h.p. motor, 12 and 24 volt tappings, laminated field, will operate on £2/5/-

Postage and Packing: Vic., 2/-; N.S.W., Tas., S.A., 3/6; Qld., W.A., N.T., 5/-.

### Aircraft Bomb Aiming Sights Barr & Stroud Mk. IX A.

Containing liquid damped compass. 5" dia. x 2" deep, with corrector box, many useful gears and also a rack and pinion. Two spirit levels, etc., in strong wooden carrying box 12" x 2 1/2" x 8", which has two mortise type catches and metal handle. £2/10/-

# Waltham

## TRADING CO.

393 Flinders St., Melbourne, C.1.

Mail Order Dept.: 319 Swanston St., Melbourne.



BEDSIDE ..



OFFICE ..



### PORTABLE ARMY TELEPHONES

English "H" Type. Incorporating a Voice Powered Handset and Bell-generator. NO BATTERIES REQUIRED. Simple to install by connecting two wires to each Unit.

Two telephones and 100 yd. reel twin wire ... £8/12/6

Extra 100 yd. reels twin wire. Per reel ... 17/6

Addition telephone units. Each ... £3/17/6



### ASTOGRAPHS

R.A.A.F. Navigators Projector Unit. Complete with three films, in wooden carrying case, 17 ins. x 10 ins. x 6 ins. 17/6



### BELL-RINGING HAND GENERATORS

Suitable for installing in the Don V Telephone to convert to Bell Call System ... 37/6

Postage and Packing: Vic., 1/6; N.S.W., S.A., Tas., 2/3; Qld., W.A., N.T., 3/-.

### AIRCRAFT GILL MOTORS

These contain a 24 volt motor, approx. 1-10th H.P., that can be revolved in either direction, A/C or D/C. A magnificent brake, and a 5000 to 1 reduction gearbox. £2/17/6

### TANK WHIP AERIALS

Two four foot sections, ideal for car aerials, or fishing Rods. Each 15/-



### CHART TABLE PLOT-TING ARM

Suitable for draughtsmen, etc. Length of arm extended 24" Length of runner 3 feet 35/-

Postage and Packing: Vic., 2/-; N.S.W., Tas., S.A., 3/6; Qld., N.T., W.A., 5/-.



### BATTERY CHARGING GENERATORS

All generators checked and tested before despatch.

24 Volt 1500 Watt	£ 8 0
12 Volt 300 Watt	12 10 0
12 Volt 750 Watt	10 10 0
	12 10 0



### WESTERN ELECTRIC U.H.F. FOUR VALVE MIDGET RECEIVER

Frequency 238 to 258 Mc. cycles Valves 3-945, 1- Super Regenerative Receiver Brand New £2/19/-

Postage and Packing: Vic., 2 N.S.W., S.A., Tas., 3/6; Qld., W.A., N.T., 5/-.



### SELSYN MOTORS

50 volt 50 cycle, ideal for use with Rotating beam 30/-

Postage and Packing: Vic., 2 N.S.W., S.A., Tas., 3/6; Qld., W.A., N.T., 5/-.



### TELEPHONE HAND-SETS

Standard P.M.G. Type, complete with cord and 4-pin plug. Brand new 37/6

Postage and Packing, 2/6; States.



### ENGLISH THROAT MICROPHONES

Magnetic type, high output may also be used as contact microphones on musical instruments or adapted for use as a pick-up for electric guitar. Comprises two microphone units which may be used separately. 12/6

Brand new 12/6

Postage and Packing: Vic., 9d N.S.W., S.A., Tas., 1/-; Qld., W.A., N.T., 1/3.



### R.A.A.F. ASTRONOMICAL INSTRUMENT

can be utilised to measure horizontal and vertical angles such as those encountered in road making and irrigation work. It is fitted with scales calibrated in degrees, two levels and adjustable turntable. £2/15/-

Postage and Packing: Vic., 2/-; N.S.W., S.A., Tas., 3/6; Qld., W.A., N.T., 5/-.

signal, the circuit is oscillating at both radio and audio frequency. When the RF control signal is received, the AF oscillation stops, with a sudden decrease in anode current from 2.0 mA to approx. 0.5 mA. The photograph of fig. 4 shows the three units that go to make up the simplest control system, the transmitter, receiver and actuator.

This particular transmitter, with its circuit of fig. 5, uses a pair of 1Q5-GT valves arranged in a push-pull, tuned-plate, tuned-grid circuit, with component values for operating in the 40.66 to 40.7 mc/s band. The filaments are supplied from a single No. 6 dry cell and high tension from 135 volts of heavy duty "B" batteries.

Connected to a suitable antenna, it will provide a workable signal over half a mile at ground level; this distance increases, of course, with the model in the air.

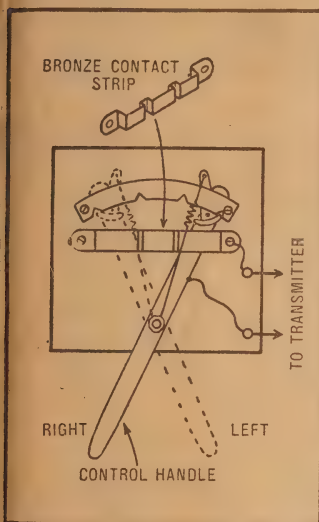


Fig. 6. — Bourne type control stick.

This system is known as "on-off" sequence control and its operation is based on the transmission of a series of pulses. With the actuator connected to the model's rudder, the first pulse or dash turns the rudder from neutral to, say, right, the next pulse back to neutral, the next left, and the next back to neutral, and so on, in a definite sequence.

It might seem, at first glance, that the continuous cycle complicates and delays the control function, but in practice this is not so. The operations can be performed so rapidly, if necessary, that the rudder can go "through" a position without the model responding. Any sort of switch can be used to switch the transmitter on and off as control signals are required.

A telephone type switch that has been rebuilt so that contact is made and broken (sending a dash) as the switch is moved from centre or neutral to either extreme position is quite satisfactory. Experience has shown that it is not always possible to remember just what the next posi-

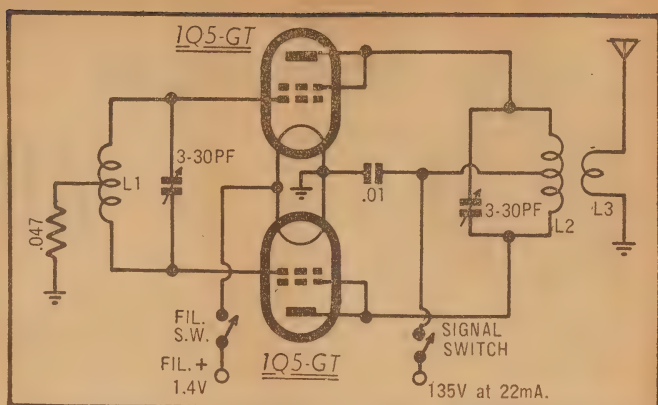


Fig. 5. — Battery operated transmitter for 40 mc. L1 and L2 have 8 turns of 16 gauge,  $\frac{1}{2}$  inch diameter, centre tapped. L3 has one or two turns.

tion of the rudder is going to be, so, to avoid confusion, the "Bourne" type control was developed.

Shown in fig. 6, this control stick has three positions, neutral, right and left. The centre arm makes momentary contact as it is moved from one position to the next; it always moves in the "right" direction and at the same time it points in the direction of the turn.

### OLD TIMER

The single-valve receiver using the circuit shown in fig. 7 is another old-timer, but still good. Miniature valve types 3S4 or 3V4, triode connected, will work satisfactorily. It has been found that the use of separate quench oscillator coils give superior results to the usual method of juggling the grid capacitor, grid resistor combination to make the detector valve super regenerate. A separate valve or the second half of a twin triode used as the quench

oscillator allows the detecting and quenching condition to be individually adjusted with an overall gain in operation. A suitable design of quench coil is shown in detail in fig. 8.

An antenna of doublet dimensions if the model is large enough, or a single wire a few feet long can be directly, capacitively, or inductively coupled to the coil. In order to achieve the large anode current charge with transmitter on or off that is required to operate the relay, the antenna length and coupling, and the grid resistor valve are the important adjustments with these receivers.

An idling current of 5.0mA, with a drop to 3.5 or 3.0mA is possible when everything is working properly.

Although the relay cannot be seen in fig. 4, it is the same type as shown in fig. 32. These relays are ex-disposals stock, and are found in the receiver section of the SCR-522-A communication set. The coil has a DC

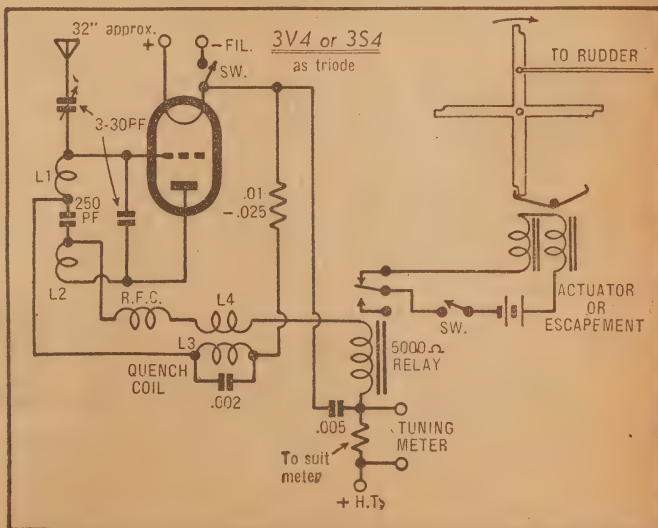


Fig. 7. — Receiver and actuator for 40 mc. L1 and L2 have 5 turns of 16 gauge wire,  $\frac{1}{2}$  inch diameter. L3 and L4 comprise a 30 Kc. quench coil.



# SIGNAL GENERATORS



BY **"ADVANCE"**

Designed for the discerning radio service engineer, the Type "E" Signal Generator is a robust, portable instrument of exceptional dependability. This high performance is due to the design being based on standard signal generator technique. Its range is sufficiently wide to cover all present needs and likely developments in the servicing and design of radio and television receivers.

The frequency coverage is 100 Kc/s-60 Mc/s in 6 ranges plus 60-120 Mc/s using the second harmonic of range "A." Accuracy is guaranteed to be within plus or minus 1%. Internal modulation is 30% at 400 c/s. A.F. output is variable from 0.5 volts. The accurate attenuator system embodies a non-inductive slide wire followed by a 5 decade 75 ohm ladder network. Use of a 75 ohm cable correctly terminated ensures that there are no reflections due to mis-match. This arrangement means that the output voltage at the dummy aerial is accurate and also helps to overcome the problem of poor attenuation at frequencies above 10 mc/s. Stray leakage is less than 3 microvolts at 60 Mc/s.


An illuminated directly calibrated dial with a scale length of over 30" is provided and this is easily and accurately set by means of a slow motion control with a reduction ratio of 10-1.

## WRITE

## FOR

## DETAILED

## SPECIFICATIONS

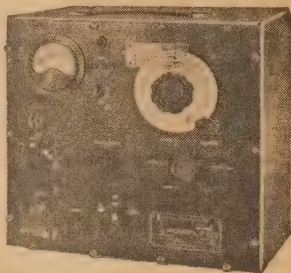

A SUB-STANDARD SIGNAL GENERATOR, TYPE "B4," is available in two models with a frequency coverage of 100 Kc/s to 70 Mc/s and 30 Kc/s to 30 Mc/s respectively. The standard Advance decade step attenuator, accurate at frequencies up to 300 Mc/s, is used, and output from this is matched through a 75 ohm transmission line to the termination pad and standard dummy aerial network. Stray radiation is less than 1 microvolt.

Internal modulation, variable up to 50%, and also R.F. output, may be monitored by a crystal voltmeter. A 400 cycle A.F. output is available up to 15 volts and provision is made for external modulation.

Calibration is accurate to within plus or minus 1% and output to within plus or minus 1db. The direct reading dial is clearly engraved and setting is facilitated by a high quality slow motion drive, making this the ideal instrument for laboratory and production applications.

Specially developed for both radio service and factory production engineers, the Type "F" Audio Generator has a frequency range of 0-10,000 c/s and is of particular interest. The range 100c/s-10,000 c/s is substantially level due to the use of a well designed negative feedback network and accurately calibrated to within plus or minus 2%.

Power output is approximately 1 watt into a matched load of 600 ohms, 5 ohms or 10 ohms attenuator and is monitored by a 2 range rectifier type meter. Total undesired signal is less than 3% at full output.

The dial is directly calibrated and is provided with a high quality drive, making this a particularly flexible instrument for audio frequency measurements.

## IMMEDIATE DELIVERY



*Sole Distributors:*

# JACOBY, MITCHELL & CO. PTY. LTD.

477 KENT ST., SYDNEY. MA5058-MA9569-0

Manufactured by: ADVANCE COMPONENTS LTD., Great Britain

distance of 5000 ohms and with the original base removed, its weight is reduced to 2oz. This relay is rugged enough to withstand vibration, easy to adjust, and is reliable on 0.5mA current charge and positive on 1mA.

A 950 1.5v cell will supply the filament, and 467, 67.5 volt minimax high tension is recommended. Although batteries can account for the weight of receiving equipment, the very miniature battery types are not recommended. The saving in weight does not compensate for too frequent renewals, and it should be remembered that the smaller batteries' higher internal resistance can change the receiver's operation completely over a small period of time. Always check the receiver tuning after fresh batteries have been installed.

## WINDING

Tuning adjustments being fairly critical, a metering resistor has been included in the receiver's high tension positive lead. Its value is chosen so that the particular 0-1mA meter used will read 5.0mA full scale. This resistor enables the meter to be connected in and out of circuit without disturbing any adjustments. Keep the meter leads very short, better still, fit banana type plugs in the meter and equivalent sockets in the receiver.

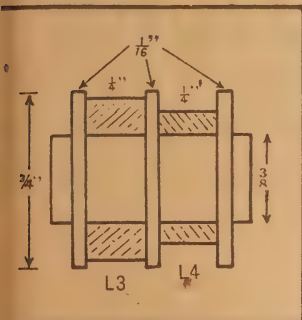


Fig. 8.—Details of the 30Kc quench coil. L3 has 1050, and L4, 700 turns of 38 B & S S.S.C. wire.

A tightly wound-up rubber band is about the lightest and most practical reservoir of energy in small quantities known, and it powers the new types of escapement to be described. The standard escapement shown in fig. 9, connected to a rudder, operates in the following manner.

With the rubber motor exerting a turning force in the direction of the arrow, (a) indicates the control arm in neutral. The transmitter "ON" will energise the coil, and allow the control arm to go half right to (b). Transmitter "OFF" will let the escapement complete the first cycle and the rudder go full right (c). There it stays until the transmitter is operated again, when the escapement goes half neutral, and with transmitter off, back to neutral.

Any further transmission repeats this cycle, only giving left this time. The advantage claimed for this escapement is that current is only required to take the rudder from

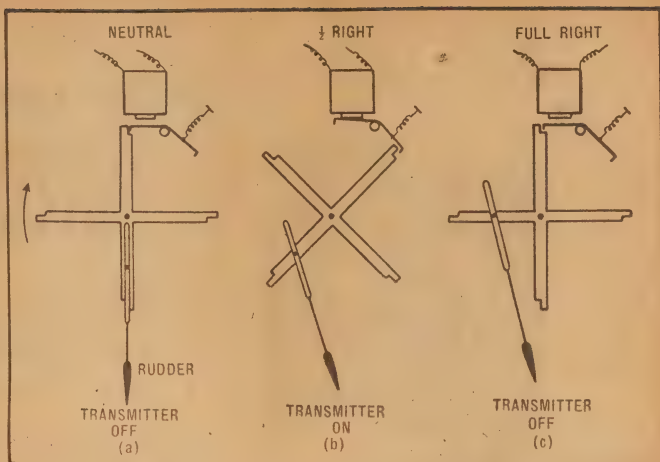



Fig. 9. — Standard escapement - operating cycle.

one position to another, not to hold it there.

The self-neutralising escapement of fig. 10, requires only one transmitter pulse to take the rudder, say, right.

It will stay there as long as the transmitter is "on"; returning automatically to neutral, when the control signal ceases; the next pulse taking the rudder left, and so on.

## AT LAST — THE MOUTH ORGAN Made Easy

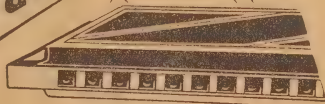

JUST ARRIVED—

a limited supply of de luxe "Silver-tone" Mouth Organs, COMPLETE WITH SIMPLE NEW HOME-STUDY LESSONS to teach you to play.

**500 Mouth Organs with simple Lessons For Playing—available for immediate delivery—WHILE THEY LAST**

Here's your chance to win friends, fun, and outings—to be playing the Mouth Organ in 30 minutes, and all popular tunes with the latest tricks and effects in almost no time.

### Join the SAMPSON MOUTH ORGAN CLUB

All who join the Club before it is booked out will receive one of these de luxe 20-reed "Silver-tone" Mouth Organs, together with the world's simplest course of Mouth Organ lessons, RIGHT AWAY—and all for a few shillings. Even this small Membership Fee can be paid at a few pence weekly if desired.

**HOW TO LEARN** to play AT HOME. Step by step they show you how to hold the Mouth Organ—vamp—tremolo—add professional tricks and effects, and play at parties—even to a simple way of playing from music—they're fool-proof. You will receive your Mouth Organ and simple lessons by post as soon as you join.

**SEND NO MONEY** Post the coupon at once for free details of the wonderful Mouth Organ and simple lessons available. But don't delay—there are only 500; bound to go quickly! Act now to be in time.

To Get Your Mouth Organ with Lessons — ACT NOW

**POST COUPON TODAY DONT DELAY**

**THE SAMPSON MOUTH ORGAN CLUB**

Dept. 3T, 481 Kent St. Box 4184, G.P.O., Sydney.

Without obligation, tell me how to join the Club and get my Mouth Organ with Lessons for playing. I enclose 2d. postage stamp.

Name .....  
Address .....



**Have You Heard?**

## AUSTRALIA'S FINEST RADIO CONSOLE

- Dual Speakers (12" and 5").
- Provision for Record Player.
- Exclusive Streamlined Chassis.
- Large, flood-lit, easy-to-read dial.
- Available in five, six and seven valve superbly-engineered chassis.

N.S.W. Country Distributors: Streamlined Electric  
Co., 41a York Street, Sydney.  
Queensland Distributors: Irvin's Ltd., Albert  
Street, Brisbane.

**Zenith**  
RADIO COMPANY PTY. LTD.

THE **CALSTAN** '529'

131 PALMER STREET, SYDNEY . . . FA2157


AMATEURS THROUGHOUT AUSTRALIA ACCLAIM
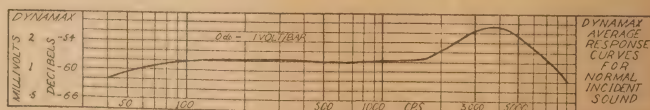
## "DYNAMAX"

MOVING COIL TYPE MICROPHONE



- EXCELLENT FREQUENCY CHARACTERISTICS. Due to a rising frequency characteristic (see curve below), this microphone gives a high degree of intelligibility to speech and will make it penetrate through extraneous noises with perfect clarity.
- EXTREME ROBUSTNESS. The heavy diecast cage of the "DYNAMAX" will stand up to rough treatment such as would ruin an ordinary microphone.
- WEATHERPROOF. You can use this microphone with confidence in the heaviest of rain or in the thickest of dust because it is completely waterproof and dustproof.



Curve shows the excellent high frequency response of the Dynamax.

Special Application for Speech Reproduction in Sound Trucks, Sports Grounds, Paging Systems, Airports, etc.

**Manufactured by**  
**STEANE'S SOUND SYSTEMS PTY. LTD.**

Head office: 60-80 MILLER ST., MEL BOURNE. FJ 4543, FJ 9140, FJ 9149  
And at 367 Kent St., Sydney. MA 2588, M 3136



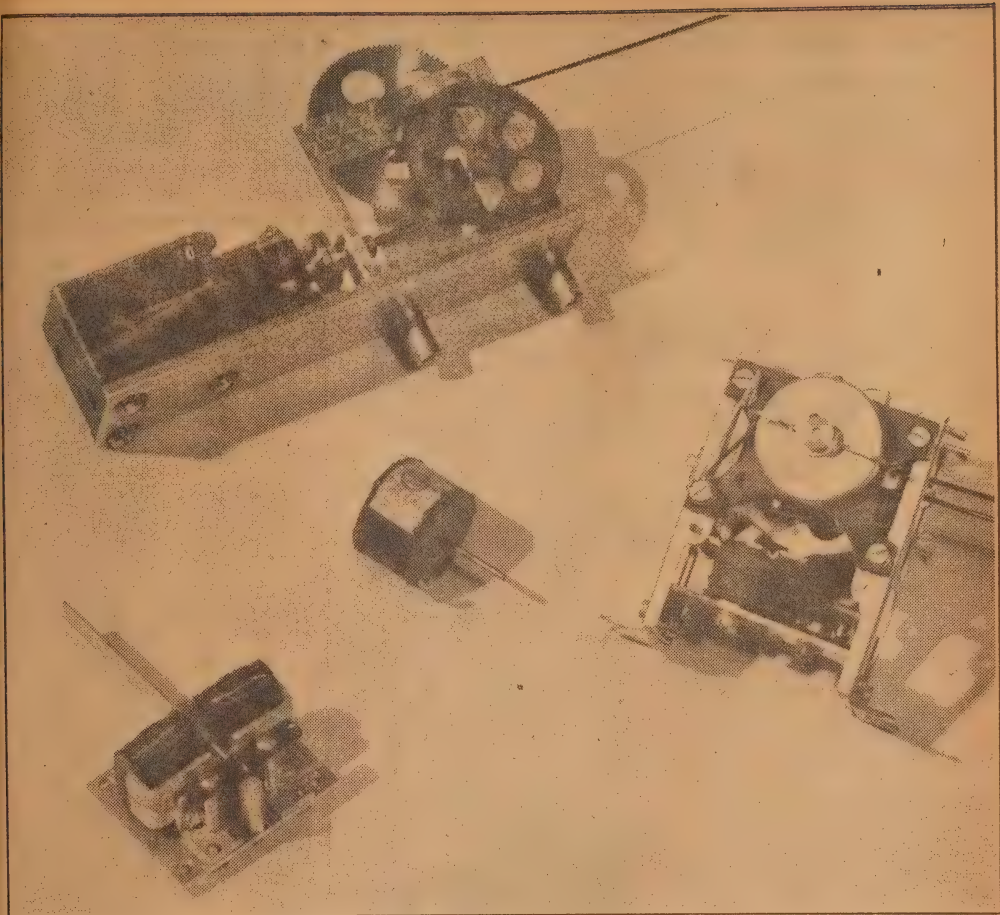


Fig. 12. — Details of motors discussed in the text.

The circuit diagram of fig. 11 depicts a motor-driven control unit which is operated by the same sequence type of transmission as the escapement just described. A small motor drives through a train of gears to the control wheel "A," fixed to this wheel are the cam and control pins.

The closing of the receiver relay contacts, by the transmitter pulse, starts the motor. The cam moves and switch S1 closes the motor circuit,

and the motor will continue to run until the cam has made a quarter revolution, so opening S1. The control pins on wheel "A" are coupled to the rudder by small cables. As the control wheel moves in the direction of the arrow, a quarter of a revolution for every transmitter-pulse, the rudder will move in sequence from right to left, with a neutral between each position.

Shown in the photograph of fig. 12,

are three types of control units, as well as a small motor. The motor in the centre of the picture, known as the "electrotor," about 1 1/2 in in diameter, is made in the models 1.5v, 3v and 6v. Due to the peculiar construction of the armature, they all have a dead spot from which they will not self-start. They are still small and light enough, however, to consider coupling two of them to the

(Continued on Page 103)

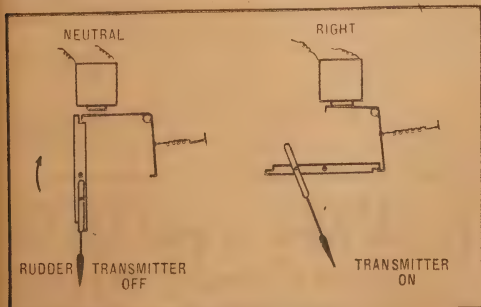


Fig. 10. — Self neutralizing equipment.

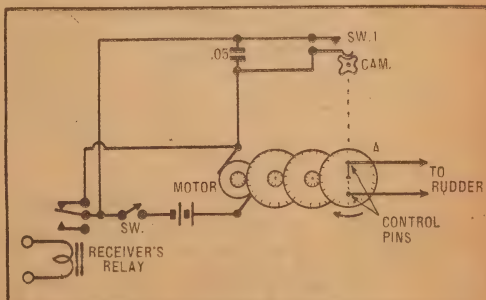


Fig. 11. — Sequence motor control unit.



## THIS MONTH'S BARGAIN LIST

- English Diagonal Cutting Pliers, 6/6  
 RAAF Sleeping Bags £3/15/-  
 Brand New Army Blankets,  $\frac{3}{4}$   
 bed size 35/- each  
 American Feeler Gauges 8/6  
 Dental Inspection Mirrors 5/6  
 Vacuum Gauges 0.30ins. 27/6  
 Pressure Gauges 0.150lbs. 25/-  
 Campers Ground Sheets 12/6  
 Brand New American Micro  
 Switches 6/-  
 Hobbyists Drills 6/- doz.  
 Upholsterers' Needles 1/-  
 Morse Keys and Buzzer, Ideal  
 for Boy Scouts. Cost £5, for 10/6  
 Genuine British 4-draw 22  
 magnification Rifle Range  
 Telescope £6/19/6  
 Pocket Compasses, English 5/9  
 Pocket Telescopes 12/9  
 Extra Strong Double Lens  
 Watchmakers' Eye Glasses 15/-  
 Car Type Grease Guns 19/6  
 12 volt Heavy Duty Accumula-  
 tors. Brand New, 75 amp. £4/10/-  
 12 volt, 17 amp. 39/6  
 Car Type Fire Extinguishers 25/-  
 Brand New American Pyrene Car  
 Type Fire Extinguishers £3/5/-  
 Extra Long Nose Radio Pliers,  
 8" long 9/6 pair  
 Brand New English Vernier  
 Calipers. Ideal for all engin-  
 eering work. Can be carried  
 in the pocket 22/6  
 Workman's Tool Bags, made  
 from solid leather and canvas.  
 Ideal for plumbers or brick-  
 layer; 18" x 8". Limited  
 quantity at, 12/6  
 Pocket Folding Telescopes,  
 optic glass lenses. Wonderful  
 range 37/6  
 Finest Quality Waterproof and Rot-  
 proof Tarpaulins. Ideal for cover-  
 ing cars, Hay Stacks, etc.  
 9 x 9 £4/10/-  
 8 x 10, £4/15/-, 9 x 15, £7/15/-  
 9 x 12, £5/19/6, 12 x 12, £7/15/-  
 12 x 15, £9/5/-, 18 x 14, £13/10/-  
 18 x 16, £14/15/-, 20 x 18, £19/19/-  
 30 x 20, £33/10/-  
 6 x 7 Genuine Japara Covers. Ideal  
 motor cycle covers 37/6  
 Army Paint, Brown or Buff, 29/6  
 gallon.  
 Brand New Army Boots. Size 9.  
 Only, pair 26/6  
 English Spiral Screwdrivers 16/6  
 Rear Vision Mirrors. Chrome  
 plated 19/6  
 Car Tow Ropes, 13ft. long 9/6  
 Gasket or Workshop Snips. Brand  
 new. Pair 4/9



A Lucky Re-pur-  
 chase.  
 £3/19/6  
 Brand New.  
 Army Phones.  
 Ideal for Farms.

Install one in your workshop or  
 house. Equal to P.M.G.



Ball and  
 Socket  
 Jointed  
 Inspection  
 Mirror

Genuine Douglas  
 AIRPLANE SEAT CUSHIONS  
 CARS, TRUCKS, CARAVANS,  
 CAMPERS'  
 WEEKEND HOMES.  
 Exceptionally well  
 sprung. Many uses.


£3/10/-  
 COMPLETE  
 As illustrated



AT LAST:  
 DALTON  
 COMPUTERS  
 IDEAL FOR  
 AERO CLUBS  
 A.T.C., ETC.



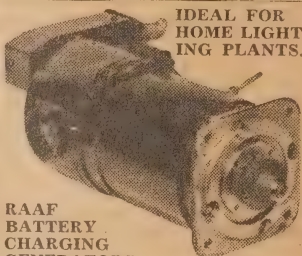Only  
 Limited  
 Stocks  
 Available.  
 Be  
 Early  
 35/-



IDEAL FOR  
 HOME LIGHT-  
 ING PLANTS.

RAAF  
 BATTERY  
 CHARGING  
 GENERATORS  
 24 volt 1500 watt £13/15/-  
 Brand New English Lucas, 12  
 volt 500 watt £10/15/-

BRAND NEW CARPENTER'S  
 BRACES  
 COMPLETE WITH RATCHET.  
 BALL NICKEL PLATED.  
 BEARING MADE IN  
 HANDLE ENGLAND  
 10" SWEEP



Wonderful Value. Worth 50/-.  
 OUR PRICE, 32/6. BE EARLY.

1 Mill Full Wave  
 Meter Rectifiers, 17/6  
 each.  
 Rectifiers for Meters  
 using 5 to 50 mill full  
 wave 5/- each  
 Cake Mixers, water  
 driven, works off any  
 water tap, as good as  
 electric. Cost £7/1/-  
 Our Price 39/6

# SURPLUS

512 ELIZABETH ST., MELBOURNE, C.1.  
 PHONE: FJ5904. Just 4 doors from

RAAF AIRPLANE  
 COMPRESSOR  
 Two Stage  
 Limited Numbers  
 Highest Quality  
 £5/5/-



PHOTOGRAPHIC BROMIDE  
 PAPER—KODAK

Fraction of New Price

5 1/2 x 5 1/2	5/- per pkt. 144
8 1/2 x 6 1/2	12/6 " " "
9 1/2 x 7 1/2	17/6 " " "
10 x 10	22/6 " " "




SURGEONS'  
 SCALPELS  
 SMALL 4/6  
 LARGE 5/6

Many other uses — Hobbyists,  
 Chirophy, Photography, etc.

AT LAST. British Army Issue  
 DOUBLE SCALE VOLTMETER  
 0-15 0-250 VOLTS

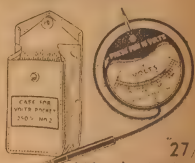
IDEAL  
 FOR  
 BATTERY  
 SET  
 USERS  
 AND  
 DEAF  
 AID  
 USERS  
 OR HOBBYISTS.



27/6  
 Worth £3/15/-

Brand New Complete Spraying  
 Outfit, Complete with Gun.

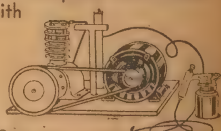Fitted with  
 $\frac{1}{4}$  h.p.  
 Motor



£32/10/-  
 Complete  
 Operates off any 230v. A.C. supply.  
 Further Limited Supply Available.

BRAND NEW  
 WESTON DOUBLE  
 READING  
 MILLIAMMETERS  
 0-40 0-120, 25/- each.



## SURPLUS STORES


PLEASE ADD FREIGHT OR POSTAGE

Mail Orders Carefully Packed

# STORES

12 ELIZABETH ST., MELBOURNE, C.1.  
Victoria Street. Phone FJ5904

## REDUCED PRICE

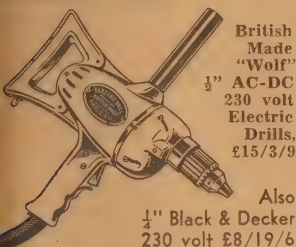

British Made "Wolf"  
1/2" AC-DC  
230 volt  
Electric Drills.  
£15/3/9


Also  
1/4" Black & Decker  
230 volt £8/19/6

ever again at these prices. Brand new. Limited Stocks available. Grinding and Buffing Sets to suit Black and Decker Drills 25/-

Brand New American Vacuum Air Pump.



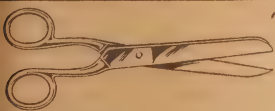Builds up air pressure to 100 lbs. at 1000 R.M. Develops up to 20 lbs per sq. in. of hydraulic pressure will pump 7 1/2 gals. S.A.E. oil or other liquids per minute. Useful for spraying, milking, presses, oil burners, hydraulic systems, £3/15/-.



urses' Scissors, 6/6  
urses' Scissors, sm. 4/9; large, 6/6.  
ressmakers' Scissors, 12/6, 17/6.  
in. Tailors' shears 27/6.

## WATCHMAKERS AND INSTRUMENT MAKERS



English Tweezers 5/6  
English Pin Vices 6/6  
Angle Drivers, 5 sizes, 2/6 to 3/6 ea.  
eyeglasses 6/6 & 8/6

# Telephone FJ5904

INCLUDE STATE IN ADDRESS  
and Efficiently Despatched

Flexible Silver Cine Screens. 6ft x 42 inches 12/6  
Altimeter or Height Meter. Lots of interest. Fit one to your car 30/-  
English Make 150 amp. AC-DC Meters, 3 1/2" dial. Ideal for Generators 57/6

## Brand New First Quality English Hand Saws, 26" long.



25/-

4 1/2, 5, 6, 7, 8 and 10 point. Never before at this price. A real Tradesman's Job.  
22" Panel Saws, 8 and 10 point. Just arrived from England 19/6  
English 6-Point Kensa Saws, 17/6



Motorist Trouble Lights  
Work off any Car Battery  
6 volt 4/6  
12 volt 3/6

Every motorist should have one.

## DRILLING OR ENGRAVING




### HANDPIECE

Brand New . . . 20/- each  
Burs 2/6 packet of 5.

## 24-volt AC-DC Geared Electric Motor

100  
Revs.  
per  
minute

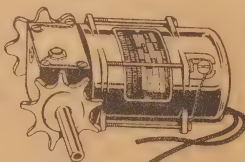

55/- . Cost £8/10/-.

## BRAND NEW BRITISH

### METRO-VICKERS

0-1 Milliampmeters  
2 1/2" diameter, 32/6



## Brand New American Weston Voltmeters 0-50V, £2/2/-.

0-50 volts, 0-100  
amps c o m b i n e d.  
£3/10/-

0-10 Weston Amp-  
meters 50/-  
0-5 Weston Amp-  
meters 50/-

Also Metro-Vickers 0-15 volts,  
0-600 volts, full scale, 0-500 Micro-  
amps. Brand New 25/-



Perspex Sheet takes the place of glass. Ideal for car windows, etc.

18 x 16 3/32" £ 1/1/-  
24 x 18 3/32" £1/12/6  
22 x 14 3/16" £1/1/-  
18 x 12 3/16" 17/6

## THIS MONTH'S BARGAIN LIST

Army Ground Sheet with cape, ideal for campers, cyclists 16/6  
Stainless Steel Pocket Knives, with 2 blades 8/6  
American-style Expanding Wristlet Watch Bands, chrome plated 9/6;  
Gold plated 16/6.

Genuine English Barbers' Scissors, 12/6 pr.

English Hair Clippers 10/6

Waterproof Trousers, Elastic Tops, ideal bike riders, golf, etc., pr, 24/9

American 66ft. Steel Flexible Tapes £3/15/-.

3ft. Flexible Pocket Tapes 2/6

Army Kit or Sausage Bags 8/6

A.C.-D.C. 0-20 Milliampmeters, 2 1/2 in. dial 23/6

First Aid Kits, complete in metal box 3/6

## AT LAST AT LAST RAAF RUBBER DINGHIES



Ideal Rivers, Lakes, Beach, etc.  
£5/5/- complete with hand pump.

Invaluable for flooded areas.

## LUCKY PURCHASE

### Complete Battery Charger

Fitted with brand new English Selenium Rectifier



Works off 230V. A.C. Household Supply.

Charges and battery from 2 to 6 volts at 5 amps. £5/15/- complete. BE EARLY—LIMITED QUANTITY AVAILABLE.



Engineers' Special Outside Screw Calipers, 4" Dividers and inside Screw Calipers, each . . . . 4/6

## Brand New ENGLISH RECTIFIERS

Make yourself a battery charger.



6v. 2 amp. 24/6  
6v. 5 amp. 32/6  
6v. 10 amp. 57/6  
12v. 5 amp. 57/6

Transformers to suit above Rectifiers 2 and 5 amp . . . . 37/6  
10 amp . . . . . 57/6



# SHORT WAVE LETTERS BY RAY SIMPSON

## NEW SCHEDULES FOR N.Z. STATIONS

In last month's issue we wrote a paragraph on Radio New Zealand, but before it was on sale, alterations were made in frequencies and call letters. On 29th July two new stations came into use, ZL8 on 9.62 mc and ZL10 on 15.22 mc.

THEIR new schedule is as follows: 4.00 am to 6.45 am on ZL3, 11.78 mc, and ZL8, 9.62 mc; 7.00 am to 4.45 pm on ZL4, 15.22 mc, and ZL10, 15.22 mc; 5.00 pm to 9.30 pm on ZL3, 11.78 mc, and ZL8, 9.62 mc. It is understood that this new schedule will continue till the end of October and possibly longer.

### Radio Australia alterations

Our own Radio Australia has also announced changes in their schedule which affects the programmes directed to the British Isles, North America, Africa and French possessions in the Pacific. Their new schedule is as follows:

VLB3, 11.76 mc, 4.55 pm to 6.15 pm, to British Isles.  
VLA8, 11.76 mc, 6.00 am to 9.00 am, to British Isles.  
VLB6, 15.20 mc, midnight to 1.00 am, to North America.  
VLB9, 9.58 mc, 1.15 am to 2.15 am, to Africa.  
VLG11, 15.21 mc, 5.45 pm to 6.45 pm, French possessions.

## STATION ADDRESSES

- OZE — The Danish State Radio, Radiohuset, Rosenorssalle 22, Copenhagen, Denmark.  
OXI — OY Yleisradio Ab., Fabianinkatu 15, Helsinki, Finland.  
FRANKFURT — Hessischer Rundfunk, Eschersheimer Landstrasse 10, Frankfurt, Germany.  
ATHENS — National Broadcasting Institute, 4 Righillis Street, Athens, TI, Greece.  
VPARD — Trinidad Broadcasting Co. Ltd., Broadcasting House, Port of Spain, Trinidad.  
HPSJ — La Voz de Panama, Servicio Publico de Radio, Box 34, Panama City, Panama.  
WRUL — World Wide Broadcasting Foundation, Box 320, Hatherly Beach, Scituate, Mass., USA.  
CHNX — The Voice of Halifax, Broadcasting House, PO Box 400, Halifax, NS, Canada.  
VEBAI — Edmonton Broadcasting Co. Ltd., Birks Building, Edmonton, Alta., Canada.  
YNEQ — La Voz de la Victoria, Apartado No. 3-3-8, Managua, Nicaragua.  
ZYB8 — Emissoras Associadas, Caixa Postal 252, Sao Paulo, Brazil.

## Korean Stations Still Heard On 7.96 Megacycles

KOREA — This country is in everyone's mind at the present time and unfortunately it is something much more serious than the identity of a short wave station. Despite the unfortunate hostilities which are now in progress their short wave stations are still on the air. The South Korean station at Seoul, HYKA, can still be heard nightly on 7.96 mc, though of course it is now in the hands of the North Koreans.

The North Korean station at Pyongyang is also still on the air over JWM, on 4.5 mc, and is also sometimes audible on their other outlet of 7.785 mc.

## LATEST CALL SIGNS FROM U.S.A.

THROUGH the courtesy of the Universal we are able to publish a complete list of the new call letters assigned to USA stations.

6.06 mc Tangier II, 6.08 mc Munich III, 6.08 mc WLW01.  
7.215 mc WGL1, 7.25 mc Munich IV, 9.515 mc KRCA1, 9.53 mc WGE01, 9.53 mc Manila III, 9.54 mc Munich II, 9.57 mc, KWID1, 9.57 mc WRUL4, 9.57 mc KWID2, 9.65 mc KRCA2, 9.65 mc WABC1, 9.67 mc KGEE1, 9.67 mc WRCA6, 9.7 mc KRCA2, 9.7 mc KCBR2, 9.7 mc WLW08.  
11.71 mc WLW07, 11.847 mc WGE02, 11.71 mc WLW05, 11.73 mc KGEE2, 11.77 mc WRCA5, 11.79 mc Honolulu I, 11.79 mc Tangier 2, 11.79 mc WRUL4, 11.79 mc WRUL1, 11.86 mc KWID2, 11.87 mc Munich I, 11.89 mc Manila I, 11.9 mc KWID1.  
15.105 mc KGEE1, 15.13 mc KRCA1, 15.21 mc KCBR2, 15.21 mc Tangier 1, 15.13 mc WRCA1, 15.24 mc WLW05, 15.25 mc Tangier 2, 15.25 mc KRCA3, 15.25 mc Honolulu 2, 15.25 mc WLW05, 15.25 mc Manila 2, 15.27 mc WABC2, 15.28 mc Munich 1, 15.285 mc WBOS1, 15.29 mc WRUL1, 15.31 mc WRUL3, 15.31 mc KCBR1, 15.33 mc Manila 1, 15.33 mc Manila 2, 15.33 mc WGE02, 15.33 mc WLW06, 15.35 mc WLW05, 15.35 mc WRUL1, 15.35 mc WRUL2.

17.75 mc WRUL4, 17.75 mc WRUL5, 17.76 mc KWID1, 17.765 mc WGE03, 17.77 mc KCBR3, 17.77 mc KCBR2, 17.28 mc WRCA2, 17.78 mc Manila 3, 17.8 mc Honolulu 1, 17.8 mc WRUL3, 17.8 mc WLW02, 17.83 mc KRCA3, 17.83 mc WABC3.  
21.46 mc KRCA1, 21.5 mc WABC6, 21.52 mc WLW03, 21.57 mc Manila 2, 21.57 mc WABC1, 21.59 mc WGE02, 21.61 mc WRCA3, 21.65 mc WLW07, 21.73 mc WRCA6, 21.74 mc KCBR2.

## Latest Verifications

PEKING, CHINA. — With conditions they are in China it is surprising that verifications at all come out of this country. Arthur Cushen was therefore very pleased to receive one from Peking confirming his reception on 15.06 mc. The state that they are on the air from 6.30 pm to 1.30 am on both 15.06 mc and 10.26 mc.

Their address is Peking Broadcasting Station, 3 St. Si-chang-A, Peking, China. A few weeks ago this station was heard quite well on 15.06 mc, though was inclined to wander around quite a bit between 15.03 mc and 15.07 mc. Malaya are apparently still being delivered to that part of China.

OMDURMAN, SUDAN. — Quite an interesting letter was received from Mr. M. Eld, the broadcasting officer at Omdurman, confirming our reception of the station on 9.746 mc. In his letter he said that they were now using 9.746 mc and 5.975 mc from 2.15 pm to 2.45 pm every day except Saturday from 2.30 am to 4.0 am and 5.0 am to 5.30 am; Saturday from 2.30 am to 3.30 am and 5.0 am to 5.3 am; Fridays from 6.0 pm to 7.30 pm, and Saturdays from 12 midnight to 1.0 am. English can be heard on Saturday from 3.30 am to 4.0 am. This station also sent a very interesting book, Sudan Almanac which gives much interesting information concerning the country.

OSU, DENMARK. — The Danish State Radio are very interested in listener reports, and as a help in identifying the stations they also announce in English. Their latest verification card received was for OSU, on 7.26 mc, confirming report of last April.

ZYS8, BRAZIL. — After a rather long wait Art Cushen has received a very welcome verification from ZYS8, Radio Difusora de Amazonas. With the verification was a very nice letter in English from the managing director, Jose Eduardo, who stated that they were anxious for further reports. The actual verification was a photograph of the Civic Theatre, Manaus.

The letter was sent by registered airmail, the address being Radio Difusora de Amazonas, ZYS8, Rua Joaquim Sarmento 100, Manaus, Brazil. This station is now transmitting on 4.805 mc with a power of 5 kw and on a favorable night it can be heard exceptionally well around 8.30.

## NEWS ITEMS ABOUT SAUDI ARABIA

Some months ago we gave details of test transmissions being carried out from Saudi Arabia on many different frequencies. Once again it is our well-known New Zealand listener Art Cushen who is the first to give full details of the station taken from its verification which he has just received.

THE verification took the form of a long letter sent by air mail and written by John E. Morrow, giving an insight into this interesting station. The station commenced operations on September 26, 1949, is located in Jeddah, which is on the Red Sea. In addition to the transmitters at Jeddah there are small studio facilities.

Each year 300,000 pilgrims pass through Jeddah on their way to Mecca. Due to Mecca being a non-Moslem forbidden area the studios which are being built in that city will be handled by Moslems only and linked with the transmitters at Jeddah by VHF-FM.

The transmitters are six 3 kw and the present frequencies are 3.95 mc, 5.975 mc, 9.65 mc, 11.85 mc, 11.95 mc, and 725 kc on the broadcast band. Due to slow progress the VHF-FM has not yet been completed, and consequently all programmes are at present originated in Jeddah. The schedules at present are subject to change, as

the station is primarily intended for religious purposes, programmes being all in Arabic and under Government control.

The engineering staff at Jeddah are all Americans, while the Mecca staff are all Egyptians. Various antenna are used such as 9.65 mc rhombic on Bahrein Island, 11.85 deg, 11.96 mc on Baghdad, 21 deg, 11.85 mc on Damascus, 10 deg, 5.975 mc on Cairo, 330 deg, 3.95 mc on an axis of 67 degrees, 6.1 and 6.17 mc were also rhombic.

Their present schedule is 5.30 pm to 6.15 pm, 1.40 am to 2.16 am, and 3.30 am to 4.45 am. Both the 5.30 pm and 1.40 am sessions may soon be changed, though the 3.30 am transmission is permanent.

Mr. Morrow said in his letter that QSL cards were now being printed, congratulations, Art, on this your latest country verified, and many thanks for the above information.

# NEW STATIONS OF THE MONTH

**COLOMBIA.**—Our mystery Colombian which we listed last month as being heard 5.55 mc has been identified by Art as HJCP and slogan appears to be de Bogota. They are still being heard to well opening at 9.40 pm, followed a few minutes later with a few bars of Inebeth Walk and then the BBC English Radio session, which continues till about 10.0 pm, when the call letters are on again.

There is a strong Morse station a few hours away from HJCP which sometimes makes reception rather difficult. Art has heard this station in the afternoon, so far we have logged them only at night.

**EL SALVADOR.**—Another of our stations last month whose call sign we could not distinguish has turned out to be YSC. This station has improved since last month and is now very good when they come on the air at 9.55 pm, when they give opening announcement, call letters and slogan. They are known as Radio Mil Vienticinco and use a three-note chime at times.

The announcement is very rapid, but the letters YSC can be followed if you listen carefully. Art Cushen put us right on this as well and states that he can hear the station in the afternoon till closing at 3.0 pm, though once again it is only at night that they seem to be audible in this part of the world. The frequency of YSC is 6.015 mc.

**HONDURAS.**—Just after we went to press last month we managed to identify a station on 6.025 mc which we thought was from Guatemala. It turned out to be ROW, Radio Montserrat in Tegucigalpa, Honduras. This identification was also confirmed by Art Cushen and an English respondent.

This station also comes on the air at 5 pm and after announcement by a lady they go into their usual marimba type music, which continues till after 10.0 pm. Their closing tune is Concerto For Two, which can be heard when they leave the air at 3.0 pm, and as this is a well-known number listeners should have no difficulty identifying this station. Actually, this has been testing for some considerable time now.

**ITALY.**—We are beginning to wonder how many more frequencies the Italian people are going to use for their various transmissions, as we have now heard them still another two, namely 17.765 mc and 18 mc. The best time to listen for these stations is around 11.0 am, as they are in English at that time, which makes identification easier.

The 17.8 mc outlet can also be heard on 10.0 am till 10.53 am with a programme directed to North America, while at the same time it is carrying a different signal directed to Mexico. At our location the 6.01 mc outlet is still the loudest around 7.0 am.

**PHILIPPINES.**—Still another new station from the Philippines, this new one being DYH4, operating on 6.055 mc. The best time to hear it is from around 8.30 pm, when HJEX in Cali, Colombia comes on the air it completely blots out DYH4. HJEX is much the louder of the two. They give their call letters as DYSR 830 your dial, and DYH4 short wave located in Ilo Ilo City, Philippines. They have apparently been on the air when they frequently look for reports from listeners.

We thought we may have had a reply on them in time to include in this month's notes, but at time of writing it had not arrived. This is the first station that we have heard from Ilo Ilo City, as the majority of the Philippines are in Manila.

**GERMANY.**—For some weeks now we have been hearing a station on 6.13 mc every morning broadcasting in both French and German, mostly the latter. They can be heard as early as 6.0 am and continue still there when the band folds up just after 8.0 am. They give identification quite often, which always sounded like Radio Europa Lederer.

According to Sweden Calling DX-ers the title of the station is Radio Free Europe and is located in the US zone of Germany

## NEW STATION LOGGINGS

Call	Kc	Metres	Location	Time heard
HJCP	5965	50.28	Bogota, Colombia.	9.45 pm
YSC	6015	49.88	San Salvador, El Salvador	10.00 pm
ZEAF	6020	49.83	Salisbury, Sth. Rhodesia.	5.30 am
HROW	6025	49.79	Tegucigalpa, Honduras	10.00 pm
DYH4	6055	49.55	Iloilo City, Philippines.	8.30 pm
Free Europe	6130	48.94	U.S. Zone, Germany.	6.30 am
ZL8	9620	31.19	Wellington, New Zealand.	6.30 am
CE970	9780	30.67	Valparaiso, Chile.	10.00 pm
ZL10	15220	19.71	Wellington, New Zealand.	4.00 pm
Rome	17765	16.88	Rome, Italy.	11.00 am
Rome	17800	16.85	Rome, Italy.	11.00 am

## Shortwave Flashes From Everywhere

**LIBERIA.**—This is a country which few listeners have heard or verified, and it was therefore very interesting to hear from a recent session from Radio Australia that there was now a short wave station in operation. This station is supposed to be on the air under the call sign ELEC from 6.0 pm using 6.025 mc.

The power is between 500 and 1000 watts and it is stated that they will later use other channels under the calls ELB2-3-4-5-6. Their address is given as Liberian Broadcasting Co., National Drug Building, Monrovia, Liberia. There is also word of another station, ELM, the Voice of Liberia, but we have no further word of this one at present. Keep a lookout for these new ones.

**BRAZIL.**—From the latest issue of Radio News and Television we learn of a new station in Brazil. This newcomer is known as Radio Record and is located in Sao Paulo and is said to be on the air from 9.0 pm to noon on either 9.59 mc or 9.585 mc, though Art Cushen reports having heard them on 6.06 mc in the early afternoon. When testing they used the medium wave call PRB9, but no call has yet been heard for the short wave outlet.

Their address is said to be Radio Record, Rua Quintino Bocaiuva 22, Sao Paulo, Brazil. The writer has heard a new station around 7.30 am operating on 9.655 mc which quite likely may be Radio Record, as it certainly sounds like a Brazilian and is quite apart from ZYC8, on 9.61 mc.

**PHILIPPINES.**—The Philippine stations do not seem to be verifying listeners' reports as readily as formerly, and it therefore is rather difficult to keep track of the new ones. A new one reported a few months ago, DYB2, on 4.985 mc, is now believed to be operated by the Bacolod Broadcasting Corporation.

Their broadcast call is DYBR, which uses 1120 kc, and station is known as Voice of Bacolod. No verifications have been reported from this one or from DZ13, on 6.11 mc, which we reported in the May issue. We hope that this month's new

one, DYH4, on 6.055 mc, will decide to acknowledge reports from listeners. There is also supposed to be a station operating in Davao, but no reports of a short wave outlet as yet.

**BELGIAN CONGO.**—In addition to the Leopoldville stations OTC, OTH, OTM, &c., there are also one or two other stations in this country which have been heard from time to time. The best heard of these is OQ2AB, in Elizabethville, which transmits on 7.15 mc and 11.9 mc. The address for this station is Radio Elizabeth, OQ2AB, A. F. M. Schovens, Box 1039, Elizabethville, Belgian Congo.

Another Elizabethville station is OQ2AC, which uses 3.39 mc, 4.98 mc and 7.2 mc, their address being College des Francais, De Sales, Elizabethville.

Schedule for OQ2AB is 11.0 pm Sunday to 1.0 am Monday only, and OQ2AC is on the air daily 2.30 am to 3.15 am and on Sunday only from 5.0 pm to 8.0 pm.

**CAMEROONS.** We receive very few reports of reception of Radio Douala, in the French Cameroons, and in fact have heard it ourselves only on two or three occasions. Reports have been sent off each time, but still there is no sign of a verification coming along.

It is gratifying, therefore, to know that this station really does verify on some occasions, as in the latest issue of the Universale a US reader reports having received one signed by a Mr. F. Fournier. The station's call letters are FIA6 and it operates on 9.15 mc with a power of 600 watts, using a delta aerial direction NW by SE. Their schedule is from 5.30 am to 6.15 am, including Sundays. Programmes are in French and they identify themselves as Radio Douala.

**SPAIN.**—Radio SEU, or to give their actual call letters EDV10, have just sent along a very attractive illustrated brochure giving details of their station. Although all in Spanish we have ascertained that the station is operated by the Sindicato Espanol Universitario and was inaugurated on 5th June, 1941, with a power of 200 watts.

At 5.30 am they change to a musical programme, and this continues till the station closes at 6.0 am with announcement by lady "Goodnight, wherever you may be." It all sounds very English and reminds you of the BBC type of programme, and the day we heard them they were coming in at quite good strength.

**CHILE.**—This is not a new station but rather a change in frequency of a very old one. While listening on the 31 metre band one night we were surprised to notice CE970 operating on 9.78 mc instead of their usual channel of 9.73 mc. The time was just after 10.0 pm, so we presume they came on the air at that time. They can easily be identified by their announcement, La Voz de Chile Para Toda America.

Another easy way to identify this station is by their opening number, Land Of Hope And Glory, and their location, Valparaiso. A few years ago they used to give opening announcements in English from their sister station CE1190, but this now seems to have been abandoned.


**SHORT WAVE NOTES for the October issue** are due on September 9. For the November issue they are due on October 7. Please send them direct to Mr. Ray Simpson, 80 Wilga Street, Concord West, N.S.W.

and is on the air from 3.0 am till 9.0 am. Strength is usually quite good and we hope by next issue to have something more to tell you regarding this station. It is also being heard quite well in New Zealand.

**SOUTHERN RHODESIA.**—Moving now to the Dark Continent we have noticed ZEAF, in Salisbury, Southern Rhodesia, using the new frequency of 6.02 mc till leaving the air at 6.0 am. At 5.0 am on a Saturday they give a programme entitled Spotlight, which surveys the colony's sport and included interviews with the Australian Soccer team and other interesting items.



# AMATEURS—DISPOSALS—EXPERIMENTERS

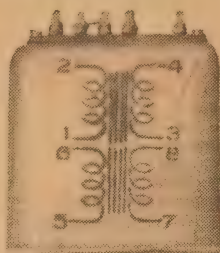

## LINE TRANSFORMERS

Four 600 ohm windings, excellent for use with Public Address and other types of Amplifiers.

12/6

Postage and Packing, 2/-.



## MIDGET GENEMOTORS

Input—28 Volts at 1.1 Amps.  
Output—250 Volts at .06 Amps.  
Size—4½ x 2½. Weighs only 3 1-8lbs.  
Perfect for use with 32 Volt domestic Receivers.

32/6


Postage and Packing, 3/-.



## VIBRATOR POWER UNIT

Volts input, tapped Voltages to 220 volts, including Bias Voltages. Used with 101 type Transceivers. Leads available 7/6 per set. Fully tested before despatch.

£3/0/0 F.O.R.

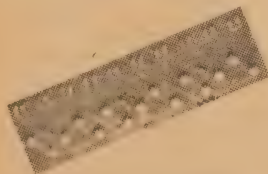

## TERMINAL BOARDS

With 15 plated terminals, also 23 pair of plated bridge type terminals with plug-in shorting bars.

7/6

POSTAGE 2/6 EXTRA



## H.F. OSCILLATORS

Complete with 7193 valve, ready to use. Tuned by a split stator condenser worth this amount alone. An excellent driver for your 144 m/c. Transmitter. Alternatively, modulate the unit as it stands.

15/-

POST FREE



## MICROPHONES

Double Button type. Quality of these compare with higher-priced Carbon Microphones.

6/-, Post Free.



## CONDENSERS

Oil Filled .01-5000 V.W. . . . . 5/-

.02-10,000 V.W. . . . . 6/6

Mica "Porcelain case" .001-5000

V.W. . . . . 7/6

Mica (Porcelain case) .0028-900

V.W. . . . . 3/6

POSTAGE 1/6 EACH

## VALVES

AV11 High Voltage H.W. Rectifiers interchangeable with the 879 Rectifier.

15/- Post Free.

EF50 Valve and Ceramic Socket.


15/- Post Free.

EA50 Miniature H.F. Diode. Complete with Socket.

8/- Post Free.

7193 V.H.F. Triode for Frequencies up to 300 m/c.

8/- Post Free.

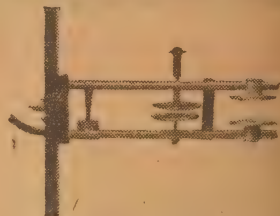


## LECHER BARS

Silver plated, complete with sliding aerial taps and tuning discs, suitable for 144 m/c.

7/6

POSTAGE 2/- EXTRA

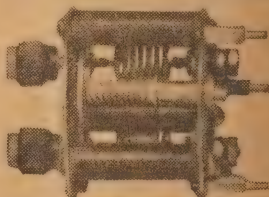

## H.F. TUNING UNIT

Cathode Tuning Unit with disc-type tuning, another necessity for your 144 Transmitter.

5/-


POSTAGE 1/6 EXTRA



## RELAYS

Rotary type using a standard oak switch bank. Can be connected to extra banks for band switching, etc.

10/6. Postage 2/-.

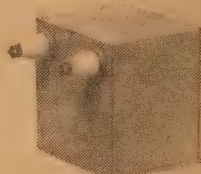

## H.V. TRANSFORMERS

80 to 3200 volts, 500 cycle type. Excellent as a spark coil for electric fences.

10/- F.O.R.

Available also at—  
Box 14, P.O., Haberfield,  
N.S.W.

# PARAGON RADIO

Address all mail to—  
No. 5 Royal Arcade,  
Sydney.

# BANDS WITH MORE

The major contest of the year, the VK-ZL International DX Contest will be run during September and October. The two national societies, the New Zealand Association of Radio Transmitters and the Wireless Institute of Australia invite amateurs throughout the world to participate.

It is not anticipated that the conditions on the 28 and 14 mc bands will improve much by then, so the lower frequency bands 3.5 and 7 mc will receive more attention. Anyone who does enter is ensured of some interesting contacts. The following are the objects and rules—

Objects—For the world to contact Australian and New Zealand amateurs.

The contest is divided into two sections, W and Telephony, and the periods of operation for each are as follows—

CW—1201 GMT, 22nd Sept, to 1159 GMT, 1st Sept, and again from 1201 GMT, 6th Sept, to 1159 GMT, 8th Sept.  
Telephony—1201 GMT, 29th Sept, to 1159 GMT, 1st Oct, and again from 1201 GMT, 13th Oct, to 1159 GMT, 15th Oct.

Duration.—(a) VK and ZL stations for contest purposes will limit their period of operation to any consecutive 24-hour period on each weekend within the times given above. Once an operator commences he must not exceed 24 hours of consecutive operation reckoned from the commencing time.

(b) In other countries stations may contact VK and ZL stations at any time within the periods shown above.

Rules.—1. There shall be three main sections in the contest—

(a) Transmitting CW.  
(b) Transmitting Telephony.  
(c) Receiving (telephony and CW).

2. The contest is open to all licensed transmitting stations in any part of the world. No prior entry need be made. Mobile marine or other non-land based stations are not permitted to enter the contest.

3. All amateur frequency bands may be used.

4. CW will be used for the first and third weekends, telephony for the second and fourth weekends. Stations entering on both Telephony and CW sections must submit separate logs for each.

5. Only one contact per band per weekend with any one station (for contest purposes) will be permitted.

6. Only one licensed amateur is permitted to operate any one station under the owner's call sign. Should two or more operators operate any particular station, only one will be considered a competitor and only one submit a separate log under his own call sign.

7. Before points may be scored for a contact, several numbers must be exchanged and acknowledged. The serial number of five or six figures will be made up of the RS (Telephony) or RST (CW) figures. The first three figures, which may begin with any number between 001 and 100 for the first contact, and which will increase in value by one for each successive contact. Eg. if the first contact for the first contact is 001, then for the second contact the number must be 054, for the third 055, and so on. If any contestant reaches 999 he will then start from 001 and continue.

8. Scoring—Fifteen points will be scored for the first contact on a specific band, and five points for each subsequent contact with any overseas country (VK-ZL districts for overseas stations), fourteen points will be scored for the second contact on the same band with the same country (VK-ZL district), thirteen for the third and so on, to the fifteenth contact, which will score one point. All contacts with that particular country (VK-ZL district) on that band will thereafter count one point each. This scoring procedure will be repeated on each band, to encourage multiband operation. There will be no VK-ZL contacts between each other. ARRL official countries lists will be used. VK-ZL districts are VK's 1, 2, 3, 4, 5, 6, 7, 8, 9, ZL's 1, 2, 3, 4.

9. Logs—Logs must be shown in this order: Date, time in GMT, band of

operation, call sign of station contacted, serial number sent, serial number received, points claimed.

b. A separate log must be submitted for each band. For each band an analysis sheet must be given showing: List of countries (VK-ZL districts) contacted, with the number of contacts and points claimed for each country (VK-ZL districts) contacted.

c. A summary sheet to show:—

1. Station call sign; 2. name and address of operator; 3. whether phone or CW; 4. points claimed for each band; 5. grand total of points; 6. brief description of transmitter, tubes, power, antenna, &c.

d. A declaration that all contest rules and regulations for Amateur Radio in your country have been observed, and that the log is correct and true to the best of your belief.

10. The judges reserve the right to disqualify stations for: a. Consistent tone reports under T8, b. continuing key clicks; c. phone splatter and/or over-modulation; d. off-frequency operation.

11. The ruling of the Executive Council of the NZART will be final, in the event of any dispute.

12. Overseas stations should call CQ VK-ZL and VK-ZL stations CQ Test.

13. Awards: Attractive certificates will be awarded to the station returning the highest score from any particular country and each call area in the USA. Additional certificates may be issued at the discretion of the contest committee. VK and ZL awards will be announced by the WIA and NZART, respectively.

14. Entries from overseas stations should be plainly marked on the wrapper, "VK-ZL Test," and forwarded to reach the NZART, Box 489, Wellington, NZ, by January 14, 1951. Logs from NZ stations should reach the same address not later than November 24, 1950, while VK logs should be sent to their respective divisions by November 24, 1950.

## RECEIVING STATIONS

1. The rules for the Receiving Section are the same as for the Transmitting Contest, but is open to all members of any short-wave listeners' society in the world. No transmitting station is permitted to enter for the receiving contest, too.

2. The contest times and the logging of stations once on each band per weekend are the same as for the transmitting contest, except that VK and ZL listeners may listen and log stations over the whole period of the contest. Logs will be in the same form as for the transmitting contest.

3. To count for points, the call sign of the station being called, the strength and tone of the calling station, together with the serial numbers sent by the calling station must be logged. Points will be claimed on the same scale as for transmitting stations.

4. It is not sufficient to log a station calling CQ Test.

5. VK receiving stations cannot log VK stations and ZL receiving stations cannot log ZL stations, but VK's may log ZL's, and vice-versa. Overseas stations will log only VK and ZL stations heard operating in the contest.

6. Certificates will be awarded, as in the transmitting contest.

Conditions at the time of writing are extremely poor on both the 14 and 28 MC bands, and it is hoped that some improvement will be shown before the end of September. Stations entering are assured of some interesting and enjoyable times and all are wished the best of luck in the VK/ZL test.

## OVERSEAS

THE Amateur Radio broadcasts sponsored by the ARRL and presented over the voice of America by Bill Leonard, W2SKF, are now transmitted on a different frequency schedule. Broadcasts to the Far East and Latin America are made at 1345 GMT, Sundays, on 9515, 9570, 9650, 11,730, 15,130 and 17,830 kc/s. This broadcast is relayed in the Far East by transmitter on 920, 11,730, 11,890, 15,250, 15,330 kc/s. The Broadcast to Europe is at 1915 GMT, on Sundays, on 15,270, 17,780, 21,500 kc/s, and relayed in Europe on 7200, 9700 and 15,230 kc/s. Both sessions are received reasonably well here on a suitable frequency.

Another interesting broadcast on amateur affairs is given from OFC in Belgium Congo on 9767 kc/s, using their new 50 kw. transmitter. The programme of 20 minutes covers general amateur news, interviews with Belgian and foreign amateurs and reviews of amateur radio periodicals. The broadcast is made in three languages—English, Dutch and French. The English session is given at 2040 GMT each Wednesday. Roger Allard, ON4RA, prepares the programme, and they are received here in excellent strength.

The 25th September sees the commencement of the Extraordinary Administrative Radio Conference, to be held at The Hague. The main business concerns the re-allocation of all frequencies below 28 mc/s for the various countries. The list, which will be presented to the conference has been prepared by committee which has been sitting in Berne for a number of years. We should soon learn after the completion of the conference when our 21 mc band will become available.

Amateur societies will be represented and delegates from the RSGB and ARRL will be in attendance with their national delegations.

The annual session of the ARRL Board of Directors was held late in May. Most of the discussions centred around the organisation of the League itself. The more interesting decisions are as follows: A drive will be held during the next year to increase the full membership of the League by 10,000 (full membership is available to VE, W, and American territories amateurs). The feasibility of a teletype assignment between 7250-7300 kc/s is to be investigated.

Committees will consider and work on expansion of 160 metre facilities, urge voluntary use of 29.8-29.7 mc/s for extensive mobile operation, effect liaison with the Federal Public Housing Authority in connection with regulations governing antennas and masts in housing projects (regulations at present exclude erection of beams on such projects).

## PHONETICS

SOME time ago the WIA proposed to the IARU that a standard phonetic alphabet be adopted throughout the world. The matter was incorporated in an IARU calendar and all National Societies voted in favor of the idea.

The alphabet proposed and adopted was the inter-services one, used by the Allied Nations in the last war and is the one recommended by the PMG in their Handbook for the Operators of Amateur Wireless Stations.


Generally speaking, the use of fancy phonetics so prevalent a few years ago has fallen from favor, and most amateurs use similar phonetics to the following accepted list: A—Able, B—Baker, C—Charlie, D—Dog, E—Easy, F—Fox, G—George, H—How, I—Item, J—Jig, K—King, L—Love, M—Mike, N—Nan, O—Obot, P—Peter, Q—Queen, R—Roger, S—Sugar, T—Tare, U—Uncle, V—Victor, W—William, X—X-ray, Y—Yoke, Z—Zebra.




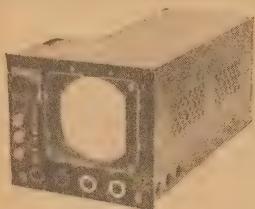
## RHEOSTATS

Bargains in Heavy Duty Rheostats.  
1RC 250 Ohm 25 Watt, wound on Mica  
and Porcelain insulated as illus-  
trated . . . . . 3/11  
100 Ohm Heavy Duty Rheostat, as used  
in English Aircraft . . . . . 2/3



## CATHODE RAY INDICATOR UNIT TYPE AI

This is an ideal unit to be converted to  
an oscilloscope or stripped for the  
excellent parts, valves, etc.  
Parts are, 1-5BP1 Valve complete  
with socket and metal shield.  
6-6AC7 (1852) Valves, 3-6H6 Valves  
12-Potentiometers  
10-Block Condensers.  
40-1 Watt 1RC Resistors.  
1-3-Position 2-Bank Switch,  
1-Toggle Switch.

All enclosed in neat metal case as  
illustrated. Easily worth £25.


Our Price . . . . . **£8/10/6**



## TELEPHONE

We have just obtained stocks of the  
Famous Don 5 Telephones, each phone  
equipped with new batteries, handset  
and buzzer, in good working order.  
Suitable for office, farm or factory.

A genuine bargain at **£2/15/-** ea.

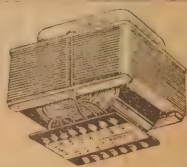


## TRANSFORMERS

Job lines of brand new transformers  
are available in the following types:—

60 m.a. Power Transformer.  
385 aside 6.3 & 5 Volt Filaments 18/6  
100 m.a. Power Transformer.  
385 aside 6.3 & 5 Volt Filaments 22/6  
125 m.a. Power Transformer.  
400 aside 6.3, 5 & 2.5 Volt Filaments  
37/6

Heavy Duty Output Transformer.  
6500 C.T. to 500 ohm line, approx. 30  
watts. 68/- reduced to 30/-  
Universal Output Transformer.  
500 ohms to 600 ohms, 12.2 ohms &  
2.3 ohms. Easily worth 19/6. Our  
price 7/6

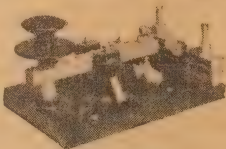Job line of Rola Isocore Transformers  
for 8", 10" or 12" Speakers in following  
sizes:—  
5000, 14,000 C.T., 10,000 C.T., and many  
others. Usual Price is 13/8.  
Our Price, 6/10 ea.



## MORSE KEY

Available in the following types.

**ADMIRALTY Type.**  
An extremely robust key mounted  
on bakelite base, all metal parts  
cadmium plated.

A lifetime job for the enthusiast or  
the amateur. Pre-war price of this  
key was 35/-.  
Our price 5/-.

**ARMY Type.**  
A lightweight key for portable equip-  
ment. Easily worth 25/-.  
Our price, 3/-.


**AIRCRAFT Type.**  
This key is flameproof and is standard  
equipment in most aircraft.  
Worth 37/6.  
Our price 7/6.



## CLOCKS
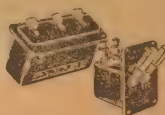
### CONTACTOR CLOCKS

Will run for 24 hours. Equipped with  
2 sets of contacts for switching Elec-  
trical Circuits. Ideally suitable for  
photography, etc. Luminous dial  
(Brand New and boxed). **25/-**



## SWITCHES

Aircraft Two-way Ignition  
Switches as illustrated. A very  
sturdy and reliable switch.

Price only . . . . . 2/-

Triple Toggle Switches, as illus-  
trated. Housed in solid bakelite  
case. Nickelplated toggles.

Price only . . . . . 2/0

Single Toggle Switches similar to  
above. Price . . . . . 1/6

Cuttler Hammer type Toggle  
Switches as used in aircraft  
bombing panels, available in  
SPST and SPDT. Price . . . . . 1/6

Cuttler Hammer type Double  
Pole Toggle Switches available in  
DPST and DPDT. Price only . 2/6

## MICRO SWITCHES

In perfect condition. Usual Price  
17/6. Our Price . . . . . 6/6



## A.T. 300 TRANSMITTERS

This radar Transmitter uses parts  
listed below and is available for strip-  
ping as well as use in its present form.  
Parts Include:—

2-AV11 Valves.  
2-Cyclatron Valves.  
2-4-pin Ceramic Sockets.  
1-24-Volt Motor.  
2-.01 5000-Volt Working Condenser.  
1-.02 10,000-Volt Working Condenser.  
1-.001 5000-Volt Working Mica Con-  
denser.  
3-Transformers (Heavy Duty).  
1-0-100 Volt AC Meter which is an  
0-1 ma movement with 1 ma Dry  
Metal Rectifier fitted.  
1-0-50 ma DC Meter.

and many other parts such as stand-  
off insulators, coils, etc., easily worth  
£20. Our price only . . **£4/19/6**

## PLEASE NOTE!

ALL PARCELS WILL BE SENT  
REGISTERED POST UNLESS OTHER-  
WISE STATED.

POSTAGE MUST BE INCLUDED  
WITH ORDER.



# MOTOR SPARES LTD.

547 ELIZABETH STREET, MELBOURNE.

## DX AND PERSONAL

(THE) NATION officials in the Middle East have been responsible for some interesting amateur activity.

ex-SM has used the following calls, JN, ZC6UNT, ZC6UNJ and is at present using SV5UN. Cards for any of the above calls can be directed to SV5UN, P.O. Box 100, Rhodes.

18AD Martinique cards in most cases be obtained by forwarding your name and a reply coupon to W4AZK, who controlling the distribution of the cards. Both W4AZK and W4AZN have done a fine job. The latter after hours' operating time, took a copy M8AD's log for a long period.

8GRC, operating portable from the pagos Is., worked 2118 stations during seven-day stay. QSL cards are always arriving in Australia. A DX man is experiencing a very time at the moment. Conditions worse than at any time since DX was a business.

Jack Pike, VK2JP, reports that VK1PG, Heard Island, an ex-VK2, sends wishes to the VK2 WIA crowd, and them to look out for him. He been worked at 0830 hours EAST frequency 14,360. Jack also mentions that ZM6AA has just come on in the Samoa on telephone 14,300 kcs. Aham Goodge, VR2BC, heard 26 VK's ZL's on 50 mc during last season, worked quite a number of them. Then on a number of occasions others have appeared, but were too late to be identified.

Mid-timer PK3LC reports that he is going strongly to reach his 7500 collection of prewar (he lost that during the Japanese invasion). It is over the 2000 mark already; he mentioned that the NIVIRA, the East Indies National Society, passed of existence this year. Founded in the PARI now takes its place. The old society was very active, and the commencement of the war ran down B/C station on normal B/C agencies.

Congratulations to Mae Robinson, HT, Alf Moye, VK2BW, and Brian Bell, who received certificates from Police Department for their very fine during the Wagga floods this year.

## W.I.A. NEWS

the recommendation of the Hunter Branch of the NSW Division of WIA led Dr. Adcock an honorary life-member. Members of the RAAT will number the Adcock D/F stations, the system of which was originated Dr. Adcock. Now a resident of Newcastle, the doctor has presented several res to the Hunter Branch.

A lecture at the July meeting of the NSW Division was presented by Mr. J. Stowe, Chief Electrical Engineer of the Sydney Water Board. His subject "Electronics in the Board." Equipment to be used for communication losses during the construction of the Warrumbungle Dam was on display, and was explained by Laurie Hughes, QP.

Mr. J. Stowe is a foundation member of the WIA in NSW, and is now an honorary life-member. He was the first A2W1, and his own call was K.

Several changes have taken place in the organisation of the NSW Division. The committee has been formed, its main function will be to assist members with technical advice. The members of the committee are Vaughan, VK2YV, chairman, Joe Reed, FR, and Dave Duff, VK2EO. Questions can be directed to the Box No. 1, GPO, Sydney.

Membership of the WIA throughout Australia is growing rapidly. A point of interest is a recent list issued by the WIA showing 14 new amateurs in NSW in a month nine of these had joined WIA.

## OUR OPPORTUNITY—

in the world-wide ranks of amateur enthusiasts! The Wireless Institute of Australia holds regular classes in Sydney, and Sydney and suburban enthusiasts obtain their Amateur Operator Certificates of Proficiency.

For particulars to the Class Manager, W.I.A., Box 1734, G.P.O., Sydney.

IO AND HOBBIES FOR SEPTEMBER, 1950

## NEW VALVES FOR OLD

(Continued from Page 43)

that they use the button base and eliminate wasteful internal leads. For this reason, they do show improved short-wave performance, even over the popular Australian-designed 2.0-volt series.

Here the story ends, however, because their electrode structures do not boast the close spacing and high gain figures necessary for extended V.H.F. performance. After all, they were designed primarily for portable use and close spacing, &c., would be a source of failure, particularly with a directly heated filament.

### BRITISH TYPES

Finally, readers may have wondered at the variety of unfamiliar British types which have been introduced in recent months. We refer not to miniatures, many of which do come from England, but to valves like the X61M, the KT61, the KT66 and a variety of other types intended for ac-dc operation.

The reason for their appearance locally is economic rather than technical. There are many types for which there is a moderate demand in Australia but not enough to justify local production, which must necessarily be on a mass-production basis. In the past, such valves were imported from America but dollar shortages and other considerations have switched the source of supply to the UK.

Fortunately, standardisation between England and America has proceeded to the point where many of the valves in question use the same base and even the same pin connections as more familiar types. The KT66, for example, can be regarded as a replacement for the 6L6 in most applications.

Once again, the home-builders need not worry too much about these types. The only thing strange about them is the type number and valve charts are available to tell as much of the story as one cannot remember.

## 1000 FREE BOOKS on DANCING



NOW you can test this wonderful course on dancing yourself—try this famous system in your own home, and if, after 30 days, you have not become an expert dancer, popular and sought-after, it costs YOU NOTHING—not one penny! But you must hurry; this offer may never be repeated. It places you under no obligation whatsoever, all you have to do is to post the coupon NOW!

### SIMPLE AS A.B.C.

IT does not matter if you have never danced a step in your life before—if you have been trying for years to dance. The famous BOLOT system, the system that has stood the test of 25 years, guarantees to make you an accomplished dancer in just 30 days—or IT COSTS YOU NOT ONE PENNY—it will teach you all the latest dances—Slow Foxtrot, Quick Step, Waltz, Tango, Rumba, Jitterbug, etc.—together with Modern Old-time. The Bolot System never fails—you have Professor Bolot's personal guarantee.

### BECOME POPULAR

MAGNETIC Personality—Popularity—confidence can be attained with Professor Bolot's wonderful course—you will find yourself sought after—admired by the opposite sex—invited out to all social functions—in short, you will become a "social lion." Dancing is the short cut to good times—non-dancers and bad dancers miss all the fun in life—now is the time to start. Take advantage of Professor Bolot's wonderful offer NOW, but hurry, this offer is limited.

"SURROUNDED BY PARTNERS"  
"I am writing to thank you for the dancing lessons, which I received safely. I cannot thank you enough, for I am coming on wonderfully with my dancing. The latest dance I went to I never missed one dance, and when the 'Medley' dance came I was in the centre of a

ring of men asking: 'Are you engaged for this?' 'Can I have this dance, please?' I did not know what to do, as I could not dance with the lot of them at once. I simply love dancing now, thanks to you. One man told me at the last dance that he could dance with me forever."—M.I. (Miss), Wyalong, N.S.W.

## SEND NO MONEY

PROFESSOR J. BOLOT, F.A.R.  
French Dancing Academy,  
Studio 54, Oxford St., Sydney.

Dear Sir—Please send me by return post your FREE Book, "DANCING AS FINE ART," (Enclose 2/6 in stamps.)

NAME .....

ADDRESS .....

..... SEPT., 1950/

### What this FREE BOOK is all about

- How to Learn at Home.
- How to Dance the Fox Trot.
- How to Dance all Dances.
- How to be Popular.
- How to Improve Conversation.
- How to be a Perfect Dancer.

Copies of this famous Book will be sent FREE. Send at once for your copy. Write to:

Prof. Bolot, Dept. 54,  
Oxford St., Sydney.



# OFF THE RECORD — NEWS & REVIEWS

The advent of the micro-groove records has thrown emphasis once again on the needle or stylus point. Over the years, records have been made with varying groove widths and shapes, each of which requires a different stylus shape and/or diameter for best results. Once again, the search is on for an all-purpose needle.

**A**S we have pointed out in previous articles, correct point fit has a marked effect not only on reproduction, but also on surface noise.

It seems generally agreed now that the best type of needle is one with a rounded tip, and of a diameter which allows the sides of the tip to rest in the groove near the bottom, but without actual contact with the bottom. In this position, the tip can follow the groove shape most efficiently, without getting jammed in the corners on the one hand, or skating about on the bottom of the groove on the other.

The earlier records were made

By JOHN MOYLE

with fairly wide grooves, which for this and other reasons seem to play best with a needle tip about 3.5 mils in diameter (1 mil equals one thousandth of an inch). Records of today, however—that is the 78 rpm types—do best with points between 2.5 and 3 mils. The RMA standard tip is given as 2.7 mils which, from our own experience checks in about right.

The micro-groove records, however, require a point of 1 mil diameter, or about one third of the 78

rpm standard. It is with the intention of discovering what happens when a point somewhere between these two dimensions is used that work is now being done.

The problem can be tackled using the smallest possible point—78 rpm and checking its results on micro-grooves, or using the largest permissible on micro-grooves and checking on the 78 records. In addition to experimenting with point diameter, further work has been carried out with tip shape, and varying the sharpness of the point—to put it more exactly, by varying the angle contained by the sides of the tip itself.

## COMPROMISES

From what I have been able to observe, none of the compromises so far suggested has shown promise of worthwhile results, even if one is prepared to lose a certain amount of the high frequencies in order to reduce the effects of distortion which follows a poor stylus fit.

A point diameter of 2 mils, for instance, isn't really bad for 78 rpm records. It sits in most cases very near to or on the bottom of the groove, and therefore produces a high scratch level. Its tendency to "skate" isn't hopelessly bad.

But used with micro-grooves, reports are correct, it's just too big. I'd be inclined to think its disadvantages here would rule it out. Inevitably, it would ride in contact with the upper edges of the record groove, and this is bad on almost every count.

Firstly, this type of needle point inevitably wears "shoulders" on the tip, as it tries very hard to grind itself into the shape of the too fine grooves. These shoulders mean the needle must be discarded early in its normally useful life, otherwise the irregular shape would play havoc with both types of records.

## RECORD WEAR

In this connection, the micro-grooves are likely to suffer to a greater extent than the 78 rpm. The material used is not remarkable for its hardwearing qualities, although the weight of the head is much less than the older type, it is concentrated on a much finer area. The actual pressure per square inch in other words, is probably much the same for less robust recording material.

Apart altogether from the matter of record wear, the distortion in the upper register brought about by the grossly large point and its inevitable



No work is more important than the care and training of War Orphans—helpless victims of war, the citizens of tomorrow. It is Legacy's chosen responsibility.

Legatees, all ex-servicemen, give their time and skill on a voluntary basis, as a tribute to the memory of fallen comrades.

To care for tens of thousands of Legacy wards needs more than time and effort—it requires ample finance. To provide it is an obligation all may share. To contribute is your privilege and Sydney Legacy War Orphans' Day your opportunity. Buy a badge—the best you can afford.

*Sydney Legacy thanks E.M.I. Sales & Service N.S.W. Pty. Ltd., 2 Parramatta Rd., Homebush, Sydney, for bringing this message to you.*

**THIS FRIDAY 8th SEPTEMBER.**

**Sydney**

**LEGACY WAR ORPHANS' DAY**

**Buy a Badge and Wear it With Pride**

ults is quite serious. The suggestion has been made that, given fairly severe top-cut in the amplifier, it can be largely removed. Though this may be partly true, although in a compromise design some fidelity may be sacrificed, it is only a back-door type of solution which has little appeal to me.

No, it seems as though a better approach must be thought out if the one pick-up is to be used for 78 and micro-grooves.

One of these is already exemplified in this country by the Goldring people, who have produced a new magnetic cartridge with interchangeable styli. The cartridge is of the saddle-armature type, and this, added to careful design, has resulted in a very good job. The frequency range is good with no undue peaks right up to 20 kc and at only a few narrow dips throughout the range is waveform distortion noticeable.

The necessity to change the stylus each time the change is made from 78 to 33 isn't much of a nuisance, particularly when we remember that we have had many years of changing needle points for every record.

## DIFFERENT HEADS

Other pickups are available with interchangeable heads, each fitted with a stylus of the required point diameter. Connoisseur, I believe, uses such a head, and the new Acos P20 uses the same idea.

In America, there are pickups available with two styli permanently fitted, one above and one below. A change from one to the other, the ad is simply turned through half revolution. There doesn't seem much wrong with this idea in principle, but, inasmuch as both styli form part of the armature, it might be difficult to avoid bringing its resonance low enough down the scale, because of the extra mass of the second stylus.

I think, therefore, that the micro-grooves will be best considered on their own as far as such requirements are concerned. Although I, for one, would not object to changing head or a stylus to accommodate them, I think the idea of a single stylus for each type represents too much of a compromise to be entertained, except where record wear and high quality are not important. Maybe they might have an application in juke boxes.

## AUTOMATIC STOPS

Another sidelight on the micro-groove records is their doubtful performance with the present day automatic stop mechanisms, to say nothing of record changers, although the latter, I hope, due for a well merited funeral.

A microgroove pickup, with about seven grams of weight applied, and, given, one mil point, isn't the best thing to use for pushing around an automatic stop, particularly when movement gets a bit heavy through wear, dust or sticky oil. Moreover, the compliance of such a pickup must be quite high, and the displacement of the stylus right at the end of the record where it is most undesirable,

can't be considered a good thing.

One need not entirely abandon automatic stops, however, if they are considered essential. I could suggest on the spur of the moment that a simple, mercury type switch could be perfectly satisfactory, as it requires very little push to tip it to one side and thus break the circuit made initially by the tiny mercury pool.

So far, I have heard very few claims on behalf of the microgrooves for extremely high fidelity. Their performance in this connection has, of course, been mentioned, but it doesn't seem to have been stressed as a major selling point. Perhaps this is because the long playing feature is considered to be the best plunger, or it may be that so far manufacturers haven't been satisfied altogether with their results in this respect.

I don't think it's fair for me to comment very much on this point, because, frankly, I don't think the records I have heard to date have been really good examples. My impression of them has been that they are inclined to be patchy, with some very poor examples mixed up with others which are mighty good.

I do feel pretty confident, however, that we need have no doubt about the eventual quality of micro-grooves. I believe, too, that we will soon get used to the fact that we must handle them more carefully in every way than the long suffering 78's. The day will come when we will wonder just how we put up with wearing a path through the carpet to change records nine or 10 times during a symphony!

## HOME RECORDING

The fun of making one's own recordings seems to be growing more and more in popularity, from what I can see, with a varying interest in the claims of discs, tapes, and wires.

At the moment, only the discs seem to be catered for to any extent for the average experimenter, although there are recorders using the other types with a more or less commercial appeal to them. A goodly cross section of more advanced readers have made attempts at home-manufacture of them all, and some appear to have obtained really good results.

In my view, the disc is hard to beat for general use, as much for its convenience as anything else. For more serious work, however, tape and wire have plenty in their favor, particularly when long playing is wanted.

We are continuing experiments from time to time with disc recordings. Only the other day, the BRS people sent me along one of their latest recorders and discs, and I intend to see what can be done to produce a design which can be built up.

Recent articles indicate the broad lines along which the result will emerge, although, at this stage, I can't say just when it will be forthcoming.

## The Australian

# SHORTWAVE HANDBOOK

Containing complete list of the world's short wave stations, Australian and New Zealand amateur call signs, international prefixes, etc. Also a host of constructional articles on short wave receivers and test equipment, aerials, amateur transmitters, etc.

NOW ON SALE

Price Two Shillings  
Obtainable at all Newsvendors



**GRAMOPHONE NEEDLES**

*For the Connoisseur*

Hard - chromium plated needles with green shanks. Radius of needle point guaranteed accurate to within the tolerance of .002"/.003". Each needle will play 20 sides, and up to 50 without damage to record.

**20 for 6/-**

Connoisseur Sapphire Needles .. 13/6 ea.

**J.H. MAGRATH & CO.**  
208 LT LONSDALE ST.  
MELBOURNE C.I. CENT. 3688.

**PHONOMOTORS**

Keen buying enables us to offer these high quality English motors at this rock bottom price.

Features are: Silent —high power— constant speed —self-lubricating bearings —plays 10" to 12" records.

**45/-**

Postage and Packing Extra.

**WILSON'S MUSIC STORE**  
HAY STREET, SYDNEY.  
Opp. Capitol Theatre. MA3208

**SONGSTER**  
REG.  
**PICK-UP & PHONO NEEDLES**



# DISPOSAL BARGAINS

## RADIO BENDIX MN.26.C COMPASS RECEIVERS

**Huge Purchase, 300 Brand New in Original Cases**  
**THE LAST OF THESE RECEIVERS THAT COST £286/-/-**

The saving in cost on this purchase passed on to YOU. This is the finest broadcast receiver ever offered. 12 valve. Operates from 24V. Converts easily to 240V-AC also 6V, 12V or 32V.

**COMPLETE WITH  
 12 VALVES  
 and  
 CONVERSION CIRCUIT**

**£15'17'6**

**LESS MOTORS £14/5/-  
 LESS VALVES £10/10/-**

Completely converted, including Speaker, Dial and Control Panel, fitted, tested and Dial calibrated ready for use.

6V. D.C. Operation .. £25/17/6  
 12V. D.C. Operation .. £25/17/6  
 24V. D.C. Operation .. £21/17/6  
 32V. D.C. Operation .. £22/17/6  
 110V. A.C. Operation £23/17/6  
 240V. A.C. Operation £23/17/6

**THE  
 CONVERTED  
 RECEIVER**


with 55 to 1 ratio  
 dial. 8" speaker in  
 bakelite cabinet.

★

Chassis fitted for  
 S/W Converter.

★

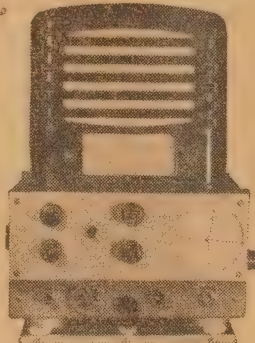**THE  
 MOST SENSITIVE  
 SET AVAILABLE  
 IRRESPECTIVE OF  
 PRICE.**



**CONTROLS:**

Volume,  
 Sensitivity B.F.O.  
 Tone & Tuning  
 Wave Change  
 Switch

★

**DIRECT  
 RECEPTION**

of Europe, USA,  
 and Asia on the  
 Broadcast Band.

**VALVES USED 2 6J5 2 6N7 1 6F6 1 6B8  
 1 6L7 5 6K7 IF FREQUENCY 112KC.**

Coverage 3 Band. 150KC to 1500KC. An outstanding receiver with a sensitivity of 1 microvolt. Ideal for home use, cars, boats, or communications and amateur use as Q 5er on 455 or 1600KC. A few sets less valves and motors. £7/15/-.

### **No. 101 TRANSCEIVERS**

Air Tested. Complete

**£10/10/0**

### **VIBRATOR POWER SUPPLIES**

All Air Tested. Complete

101 .. .. . £3/15/0  
 FS6 .. .. . £5/5/0  
 109 .. .. . £8/10/0

### **ALUMINIUM & DURAL TUBING**

9/16th" O.D. 10 Gauge

Lengths to 15 feet. Walls heavy  
 enough to thread and screw.

**1/- per foot**

Weight: 4oz per ft.

### **SCR. 522 TRANSCEIVERS**

17-VALVE. 100 to 156 Megs.  
 Ideal for Amateur 144 meg. Band or  
 for conversion to vehicle band.  
 PERFECT ORDER.  
 Complete with Valves **£22/10/0**

Low Impedance Headphones.  
 New, with Cord & Plug 10 6

Low Impedance Headphones.  
 Used. Tested .. .. . 7 6

Mark 3 Microphones.  
 New. With Cord & Plug .. 7 6

Gas Filled Vibrators.  
 Synchronous.  
 New, 6v. F.S.6 Type .. .. . 12 6

2-Gang F. & N. Tuning  
 Condensers.

NEW. Midget .0004. .... 5 9

E.F. 50 Valves. With Ceramic  
 Sockets.

NEW .. .. . 12 6

V.H.F. Transmitters, including  
 7193 Valve.

For 144 or 288 Meg. .... 12 6

### **A.S.V.R. RECEIVERS**

14-VALVE, 190 to 220 Meg. Ideal  
 for conversion to 144 or 288 meg.  
 Also a ready-made Television  
 Receiver. 30 meg. I.F.

**£8/10/0**

### **New Bendix T.A.12B Modulators**

Including 24v. Power Supply. 50 watts  
 output. B Class 807 P.P. Excellent  
 High-power P.A. System.

**INCLUDING CIRCUIT  
 DIAGRAM .. .. . £25/0/0**

### **GENEMOTORS NEW**

Input	Output	60 mA.	£ s d
24 Volt	250 Volt		
24 "	230 "	100 "	1 10 0
24 "	275 "	50 "	2 10 0
32 "	275 "	100 "	1 15 0
32 "	300 "	215 "	3 10 0
12 "	325 "	50 "	2 5 0
12 "	550 "	160 "	1 10 0
24 "	550 "	160 "	5 10 0
24 "	315 "	200 "	4 0 0
			3 0 0

Phone:  
 LA1604

# EXCELAIR RADIO

Phone:  
 LA1604

136 Victoria Road, Marrickville

**For the Benefit of Distant Patrons, Phone Attended Till Midnight.**

# FROM THE SERVICEMAN WHO TELLS

(Continued from Page 35)

with the possible arrival of vision. If things like that can be on a few hundred volts, what adjustments will be necessary for picture circuits which run at anywhere between 7 and 15 thousand

en the deflecting voltages can be quite high and enough to make me look twice at the insulation. It's nothing like being cheerful! back to servicing.

A little meter I wrote up a few graphs back nearly came to my aid this morning. It happened this way:—

## NT SET

A 4-valve mantel receiver came in for service. The owner explained it must be a valve because the set lit up and therefore the power was getting to the set. He seemed surprised when I explained everything could appear normal—all the valves be alright, and the set remain stonily silent. I thought how people automatically blame the valves for a failure.

The set was completely dead and I did not hear even a whisper of life from the speaker. A shorted tuning line, the usual explanation for complete failure, causes the rectifier to get pretty hot, but this one was relatively cool. What went on? The set was removed from the case, switched on with one hand and I reached for the meter with the other. Just then, I was called away and the set was switched off again.

Coming back five minutes later I had the general impression that the speaker field was probably open so, after switching on again I handed the prods over to "Ohms" and proceeded to take a reading. The pointer flew over with a click which could be heard all over the room. I had been trapped.

The field was indeed open and the brief period when the set had been switched on previously had been sufficient to charge the input condenser. Being a good one, it had retained its charge—a matter of nearly 400 volts.

When my poor unsuspecting meter was connected across the terminals of the open-circuited field coil, one side was virtually earthed through the B-plus circuit in the rest of the set, putting the whole of the voltage across the meter. The pointer was bent slightly but otherwise undamaged.

If you want to bend a meter pointer in this fashion, there is actually no need to run a drill into the speaker field. It is rather expensive, like the old Chinese method of roasting pork.

All you have to do is to switch the set on without the speaker and its field plug in. When switched off again, the input condenser will be nicely charged and the stage all set to give yourself a "belt" or ruin your pet ohmmeter.

## BOOK KEEPING

By way of conclusion, I made a few wisecracks some issues back about keeping books and making up tax returns. However, I can well imagine, in these complicated days, that such matters are a real problem to many servicemen. Not being a financial or bookkeeping wizard myself, I won't undertake to suggest ways and means.

However, I have a very good friend who knows all about columns and figures and I am trying to persuade him to invent a system for servicemen. Don't be surprised, then, if your serviceman article takes a very different form next month.

# THE 1950 PENTAGRID FOUR

(Continued from Page 59)

ture valves when plugging them into their sockets. Take it easy and gently slide them into place. Ideally, a dummy plug or a valve should be inserted into each socket during the socket-wiring process to avoid misalignment of the sleeve contacts.

Connect the speaker via its plug and socket at the rear of the chassis. The speaker should have the usual transformer mounted and suitable for a load impedance of around the 10,000 ohm mark. Switch the set on again, connect an aerial and turn up the volume. In most cases you will be able to tune-in a station even before the alignment procedure is commenced.

## DIAL ADJUSTMENT

However, before going any further, adjust the dial drum drive on the tuning gang so that there is equal overlap of the pointer at each end of the dial travel.

Now tune down toward the high frequency end of the dial and select a station. Adjust the aerial trimmer, that is, the one nearest the dial, for loudest volume from the station. Identify the station and, if it does not coincide with its marking on the dial glass, adjust the oscillator trimmer a little at a time until it does. Having done that, readjust the aerial trimmer for maximum volume. You may find it necessary to follow each adjustment of the oscillator trimmer with readjustment of the aerial trimmer to keep the station loud enough.

Now swing the tuning up toward the low frequency end of the dial, that is, toward the end where 2FC appears. Identify a station, note its position on the dial and adjust the slug protruding from the bottom of the oscillator coil until the station is tuned in at its correct position on the dial. While listening to this station adjust the slug protruding from the bottom of the aerial coil for maximum volume.

## FINAL CHECK

These adjustments may have altered slightly the situation down toward the other end of the dial so chase up the station which you had tuned in before and go through the adjustments of the oscillator and aerial trimmers as mentioned earlier. If the necessary readjustment was of some magnitude, recheck the setting of the slugs at the other end again. This will not usually be the case, however.

Now select any station on the dial, preferably a weak one, and adjust the slugs protruding from both the top and bottom of each I.F. transformer for maximum volume, starting with the No. 1 transformer. Go through this procedure twice to counteract any interaction between windings.

That's all there is to the alignment procedure. It isn't as complicated as it might sound and can occupy less time than it takes to

(Continued on Page 103)

# PUTTING YOUR CRO TO WORK

(Continued from Page 39.)

ep. The nature of the pattern indicates that the signal on the oscilloscope plates has twice the frequency of the horizontal deflection. In other words, the characteristic is an 8 shape, lying sideways, indicating a predominantly 100-cycle component, arising from the filter unit.

This would obviously be the case, since the instrument was connected directly across the first filter condenser.

By disconnecting the lead temporarily and substituting an input from an audio generator, we determined that the pattern height corresponded to a voltage of 10 RMS. In other words, there were 10 volts of hum across the condenser.

The set actually had two condensers in parallel in this position. By disconnecting one of them more than doubled the height of the trace

(figure 6). The effect of extra capacitance on the hum level could thus be observed very readily.

Measurement across the second filter condenser indicated a very small ripple voltage indeed. It was necessary to turn the amplitude control to maximum and even then only the faint suggestion of a figure 8 pattern could be detected (see figure 7). This was measured as being equivalent to .04 volt RMS. Related to 250 volts d-c, it represents a ripple percentage of .016.

Disconnecting the first filter condenser naturally dropped the HT voltage and increased the hum level to an objectionable percentage. The effect on the CRO screen is indicated in figure 8. The pattern is highly irregular in shape but the double loop characteristic is still apparent, indicating the predominance of the 100 cycle filter component.



# ANSWERS TO CORRESPONDENTS

R.N.N. (Ayr, Q.), sends a subscription for Radio and Hobbies, and a copy of the "Short Wave Handbook" when available. He also sends a problem for the "Answer Tom" section, gives some details of converting a No. 19 army set to a short wave set, and also asks about the availability of tropic proofing solutions.

A. Many thanks for your letter R.N.N. and the subscriptions have been forwarded to the appropriate department. Your contribution for "Tom's" page is also being handled and should appear in due course. Your conversion job makes interesting reading and as you say should give excellent results. The phone circuit has been used before R.N., or at least arrangements very similar, but if you worked it out yourself, all due credit to you. Glad you like "The Serviceman," who appreciates your remarks. Regarding tropic proofing. We suggest you contact some of the large manufacturers of paints and varnishes. These firms apparently did most of the research in this field during the war.

H.R.C. (Cobden, Vic), thanks us for information supplied through the Query Service which has enabled him to improve the characteristics of a bass boost circuit. A. Many thanks for your report and we are pleased to note that the amplifier is now performing in a better fashion. We are also pleased to note that you liked the top-cut filter which we agree is absolutely essential with the combination of present day gramophone records and high fidelity loud speakers. Most enthusiasts using similar equipments have had the same experience as you mention.

J.S.T. (Cooks Hill, Newcastle), forwards a couple of suggestions for our "Reader Built It" page, one being a circuit sent to him by an American experimenter.

(A.) Many thanks for your contributions J.S.T., and we have noted your circuit for future use. The crystal triode circuit is quite interesting, and appears to follow fairly standard practice in the use of these devices. It is not likely to be of a great deal of interest to Australian readers however, as unfortunately these units are not available in this country.

W.R.C. (Victoria): Advise of a change in amateur call sign, and requests that it be included in the "Call Sign Handbook."

(A.) Your notification arrived rather late. However your entry now appears as VK3ARC, as it should be.

L.H.C. (Nutgrove, Qld.), congratulates us on the high standard of the magazine and at the same time asks a number of queries.

Many thanks for your very kind remarks with regard to Radio and Hobbies. Your expression of interest is greatly appreciated. We would not advise connecting headphones in the circuit of a 115-G since the plate current is likely to be 6 mA. or greater which is more than most headphones are designed to carry. A better scheme would be to place a choke in the plate circuit to connect the phones between plate and ground. A coupling condenser of from 1 to 5 mfd. should be included, of course, to isolate the plate voltage from the phones. The choke could conveniently be the primary winding of a speaker transformer. The secondary winding could be left disconnected or a permanent speaker could be connected to it if desired. Both of your modulated circuits appear to be in order. The primary winding of a push-pull audio transformer could be used in place of the centre tapped choke specified. Some adjustment of the parallel condenser may be necessary in order to obtain a satisfactory audio note. As you suggest, shorting the audio output terminals should stop the modulation but if the effect is not complete it would be permissible to increase the value of the coupling condenser. The thickness of twelve copies of Radio and Hobbies varies from volume to volume and in following the binding instructions in the February, 1949, issue it is necessary to make allowances for this. Among the test

equipment we have already described are included several signal tracers and modulated oscillators but we have not yet described a valve tester due to the difficulty in obtaining the special components within the required quantity and quality.

C.W.W. (Lakes Entrance, Vic.), is operating a 6J7-G pre-amplifier under the usual resistance coupled audio amplifier conditions but with a supply voltage of 400. He wonders if he should use a dropping resistor.

(A.) No series dropping resistor is required to satisfy valve operating conditions but it may be desirable to employ a decoupling resistor of, say, 1 megohm and a by-pass condenser of 8 mfd. to prevent coupling through the power supply with resultant low frequency oscillation or motor-boating. Since the valve is operating at a low level the position on the operating curve is not critical.

E.M.McF. (Windorah, Q.), sends a circuit of a short wave converter which he is using in conjunction with the "Reader Built It" published in R. & H. for July, 1950, and suggest that it might also be suitable for publication in the "Reader Built It" section.

(A.) Many thanks for the circuit, which we have filed for possible future use. Strictly speaking this is not what is known as a converter, which term is usually reserved for those units which operate

## YOUR QUERY?

1. Queries will be answered in rotation through the columns of our magazine if not accompanied by a fee for a postal reply.
2. Queries, neatly and concisely set out, will be answered by mail as quickly as possible if accompanied by 1/- in postal notes or postage stamps. Endorse envelope "Query."
3. Back numbers are rarely available but reprints of most circuits, wiring diagrams, and parts lists will be supplied for 6d each, minimum charge 1/-. Thus a circuit, layout, and parts list will cost 1/6 in stamps or a postal note. Endorse envelope "Circuit."
4. Blueprints of exact size chassis layouts with all essential holes, and cut-outs will be supplied if available for 2/6. Endorse envelope "Blueprint."

Address your letters to the Technical Editor, "Radio & Hobbies," Box 2728C GPO, Sydney.

on the superhetrodyne principle. The unit you have described is generally referred to as an adaptor, and the idea was a very popular one in the days before the superhetrodyne was in common use. Being a regenerative short wave set it should be capable of very good results, always provided that it is correctly handled.

(Randwick, NSW) says he is very keen on the "Simplified Superhet" in the August issue. He suggests that we should describe a short-wave unit for it, also a record-player attachment.

A.—Many thanks for your encouraging remarks and we trust that you will be well over your sickness by this. We have covered the record-player angle but are not so sure about the short-wave "unit." We are trying to keep the "Kit" series to essentially simple projects and the idea of a short-wave or dual-wave version may not fit into this plan. We prefer to reserve judgment on that for the time being. In the meantime, the Australian Short-wave Handbook contains details of a simple short-wave con-

verter which could be used ahead of this set.

E.E.D. (Sydney, NSW) says he likes circuit of the simple superhet in Australian Short-wave Handbook. However, he has had difficulty in obtaining the necessary 2.0 Mc. I.F. transformer.

A.—Actually the term 2.0 Mc. is rather broad one and it would be possible to use transformers resonating at where near this frequency. The A.Mfg. Co. produces 1900 Kc. (1.9 Mc.) transformers as a standard line, while there have been quite a few 1600 transformers around the shops, taken from disposals equipment. Either could be used without alteration to circuit or coil data. We would advise you to use 455 Kc. transform however, as the inductance response would be adversely affected.

A.C.D. (Northcote, Vic.) wants additional information on loudspeaker baffling methods.

A.—Sorry but we cannot give you information over and above that which has already been published in previous issues. We rather feel that you have sent this from your reference to speakers.

ports." However, just to repeat, the cabinet of a vented enclosure it should have an internal volume of about cubic feet for an ordinary light 12 in. speaker and up to eight cubic feet for the larger, heavier type with a cycle cone resonance. The cabinet need to be built from heavy timber, preferably inch thick and lined with some soft absorbent material. The vent should approximate 0.8 times the area of the opening but it can be located in any position which happens to suit the appearance of the cabinet. Your use of the tapestry covering for speaker hole is quite a good one, particularly as it is of such open weave.

H.I. (Kalgoorlie, WA) sends in the circuit of a DC mains operated double push-pull amplifier for possible use in the Reader Built It page.

A.—Many thanks for the circuit, which will be filed for consideration as you request. We agree that the method of controlling the volume offers serious problems in this type of amplifier. So form of ganged potentiometer would probably be the only really satisfactory solution.

A.T. (Beecroft, NSW) sends in a circuit for comment. It appears to be an attempt to combine, in a small set, diode detector and a triode amplifier.

A.—Apart from the desirability otherwise of such a combination, circuit contains several fundamental errors. The filaments of both the detector and amplifier sections are operated from the same supply without provision for rendering them independent with regard to audio currents.

The grid and filament of the output valve are directly connected together by virtue of this circuit, which means that would not amplify or even pass a signal. If a single valve operating a leaky grid detector is used, there is point in having a separate diode. We would suggest, therefore, that you use a standard one-valve circuit. Such circuit is available through the query service and we would be pleased to forward a copy to you on request.

F.H.M. (South Brisbane, Qld.) writes to ask about a large dual-wave rectifier he has constructed by combining a number of Radio and Hobbies circuits.

A.—Many thanks for your letter and we are very glad to note that you have found so much of interest in our magazine over such a long period of time. The set certainly sounds a big job, might be possible to cure the instability you mention (probably motor-boating) by operating one or more of the voltage amplifier stages directly from the filament of the rectifier rather than from the normal high tension supply. A separate decoupling resistor and condenser would be necessary, of course.



## ANSWERS TO CORRESPONDENTS

(Footscray, Vic.) wishes to know how the circuit of a one-valve receiver on file.

Yes. We have details of at least one one-valve receiver in our files and should be pleased to forward any of them to you on receipt of the 1/- query fee. One circuit uses a 30 valve, while another is a 1.4-volt type 1Q5-GT. The third uses the 2-volt 1K5-G and may be of special interest to you since the is available at an especially reduced price.

(Dubbo) sends a subscription and makes some encouraging remarks about R. and H. He also says that we test some of the records on the market at the present and comment on their performance. Your subscription has been forwarded to the appropriate department, and many thanks for your kind words. We are glad you like the "Off Record" feature. We have not had opportunity to give the various record-changers a thorough trial, but we may be able to publish something on the subject in the near future.

(Chatswood, NSW) has a commercial communications receiver which can tune the broadcast band. He says it is possible to make a converter to feed in at 1700 kc/s, the lowest frequency to which the set tunes. The circuit of such a converter would present any problems and could be along the same lines as the S.W. set described in the January, 1948. Use a standard broadcast band coil. The output coil can also be a broadcast aerial coil which, with the variable condenser shown on the circuit, can be tuned with the set at approx. 1700 kc/s. The oscillator, however, is a non-standard item. The coils for use with a 1000 kc/s. aerial have been manufactured by two companies, but it may be better to try a number of radio houses before you can locate one. The decrease in the value of the capacitance may be necessary to good tracking.

(St. Brisbane, Qld.) tells us he built the Jeep circuit, published in October, 1942, issue of R. and H. Although very pleased with the results, he would like to know if we have circuit diagrams of a set which is built along the lines of this set but employing an audio driver stage and an output. He makes mention of valve types which he has on hand, and of power transformer and of a speaker that he wants to use a particular speaker. We had to know that the "Jeep" provided service, W.H.N. With regard to requirements of a larger set, we suggest the 1946 Standard (B/C), which was described in the May, 1946, issue of R. and H. This set employs valve types down to the push-pull 6-G's in the output stage. Furthermore, there is provision for using up to standard type having reasonable output. Incidentally, the pick-up should be shunted with a resistor of about 0.05 megohm to 0.1 megohm when using a magnetic type. The 385 volt per side power transformer shown in the circuit diagram is replaced by the 285 volt per side type which we have on hand. The 1000 ohm electrodynamic speaker field coil in the filter network should be replaced and the electrolytic filter capacitor increased to 16 mfd. If filter is still apparent, it may be necessary to add another filter choke and electrolytic capacitor to the filter, although this should be avoided if possible, as the output voltage from the first choke will be down to between 125 and 250 volts as it is. An extra choke will drop this figure to about 90 volts, depending upon its d.c. resistance and the actual HT drain when used to a signal. However, the main reason for this lower voltage will be the audio output but the push-pull should be able to provide you with much more than you can actually use for general home listening. The 80 ohm resistor has the same electrical characteristics as the 5Y3-GT and hence can be used without any circuit change.

## Keep Your Queries to the Point!

ONCE again I must ask our readers to assist in making the query service efficient and helpful. Unfortunately for us, most people these days prefer to pay their 1/- for a postal reply rather than wait perhaps weeks for an answer in the Correspondents' Columns. I can't blame them for this, of course, but at present we have such a flood of shilling queries that I just don't know what to do about it.

At the moment, it is taking a great part of three men's time every day to find out the answers to your questions. This cuts into the normal work so much that I am doubtful whether it can go on. Particularly as the 1/- charge does not nearly cover the cost of time and office handling for such letters, many of which are really too wide in their coverage for us to handle quickly.

In the early days, I did not visualise the 1/- service as anything else than a quick way for a reader to get out of trouble experienced in building one of our sets. It was not meant to become a discussion centre for almost everything

in radio, and from what I can see from the questions we are asked, that just about sums it up at the present time.

Now if we are to continue the service as at present, we must either be able to handle your queries more quickly, or charge more for the service, or cut it out altogether. The last I don't want to do, the second I'd rather not do, and the first we must do.

From now on, will you please make your questions short and to the point, numbering them if you like, which will help you to sort out your ideas before you write them down. Do not ask questions about general radio matters—that is why people write textbooks! Remember, our main object is to help you get your R & H receiver working, and from now on we may have to commence returning your money if the letter strays beyond the scope of the service.

I do hope you will help in this matter. It may be a compliment to us to deluge us with so much confidence and question. But spare a thought for my perspiring staff who must bear the weight, and please don't make it heavier than they can stand!

—THE EDITOR.

to the power supply wiring. The B/C version of the 1946 Standard did not incorporate a tone control, although, of course, negative feedback was used. The D/W version of this set as described in the June, 1946, issue of R. and H., included a tone control, the particulars of which are as follows: Between the plate of the "top" 6V6-G and the centre-tap of the output transformer connect a 0.1 megohm and a 0.02 megohm resistor in series with the 0.02 megohm on the transformer centre-tap side. Again between

these two points connect in series a 0.002 mfd. capacitor, the outside ends of a 0.25 megohm potentiometer and a 0.01 mfd. capacitor, the 0.01 mfd. being on the transformer centre-tap side of this series network. Join the moving arm of the 0.25 megohm potentiometer to the junction of the 0.1 megohm and the 0.02 megohm resistors and from this point take a 0.25 megohm plate load resistor to the plate of the 6J7-G audio driver valve. This tone control arrangement is not new but it is quite effective.

## AIRCRAFT Dashboard CLOCKS

(U.S. & U.K. Air Forces)

These clocks are suitable for HOME, CAR, MOTOR BIKE, BOAT, AIRCRAFT, PIGEON RACING, and IDEAL for DARK-ROOM precision timing or any place where a reliable timepiece is required. All clocks listed have jewel lever movement.



AMERICAN

(Brand New as Illustrated above.)

BULOVA, 8-day, luminous dial with sweep centre, second-hand. £5/7/6

BRAND NEW £5/7/6

ELGIN, 8-day, luminous dial, with sweep centre, second-hand. £5/5/-

BRAND NEW



1-day, luminous dial with sweep centre second-hand and dummy time of flight hands.

BRAND NEW £2/17/6

## AMERICAN ELGIN WATCHES



These WORLD FAMOUS POCKET (ex-Army) WATCHES (as illustrated), with all luminous dials, jewelled movements with second hand, are worth £8/10/0. Reconditioned as new. A necessity to the man on the land or in the tropics. 65/-

SCREW FRONT AND BACK



SMITH'S, 8-day non-luminous dial with dummy time of flight hands.

BRAND NEW £4/12/-

All orders promptly attended to. Please send Cheque, Money Order, or Postal Notes. SORRY, No C.O.D.

**M. GOODMAN**

422 PITT STREET, SYDNEY, N.S.W.



## Readers say:

### SHIELDED WIRE

I have been interested in recently published remarks on the effects of shielded wire in amplifier circuits. I have always had a sneaking suspicion of shielding, particularly long leads running from volume controls, &c.

On reading the aforementioned remarks I decided on an impulse to do away completely with all shielded wire in the audio section of my receiver by way of experiment.

Rather a drastic step to take, I might say, and one which I thought would most likely be a complete failure because of the instability and hum pickup. But I set to work and when I had finished I had plastic-covered wire running all over the place, draped across everything by the shortest possible route.

Well, I switched on and let her rip. It appeared to be better but most likely it was only my imagination, because at the maximum of 5 kc/s even, the capacity

actual sound output versus frequency would look like, so I bundled all my junk into the old bus and buzzed off into the Radio School at MTC where I attend. I set up my enclosure in a sound-proof room with BFO feeding into the pickup terminals and a standard microphone set up at the same height as the speaker and about eight feet directly in front of same, the output feeding into a sound level meter.

I fiddled with the BFO while listening to the output and was pleasantly surprised to hear the output well sustained to below 30 c/s and above 13 k/s. I thought this was pretty good so I set to work with a friend and eventually completed a set of tabulations which in turn resulted in the curve enclosed. I showed the result to one of the instructors and he seemed to think it was not too bad but I pointed out the rapid falling off in the response above 7 kc.

Although the speaker response is supposed to fail here I did not expect to see it give up the fight so quickly, taking into consideration the apparent loudness as I listened to it. But I was surprised to learn that the db meter also fell off rather rapidly after 7 kc, so I thought things may not be as bad as they appeared.


Personally, I don't think it is so bad considering it is only a simple 2-valve amplifier with a high-mu triode for 1st amplifier.

### OUR COMMENT

By way of comment, it would be impracticable to remove the shielding from most amplifiers, for the reasons you mention. The proper course is to arrange the layout so that long shielded runs are not necessary.

The setting of the volume control during the tests is not indicated but, as we pointed out, it can have a vital bearing on top response, particularly when feeding into a high-mu triode.

The curve of the treble response is inconclusive in detail, because of the db. meter limitations, but its general shape is more or less as we would expect it to be. Inexpensive speakers will reproduce 13 kc. without a doubt but at many db. below the output at middle frequencies. Your curve corresponds closely with a typical speaker curve published on page 41 of the January, 1950, issue and this rather proves the point.

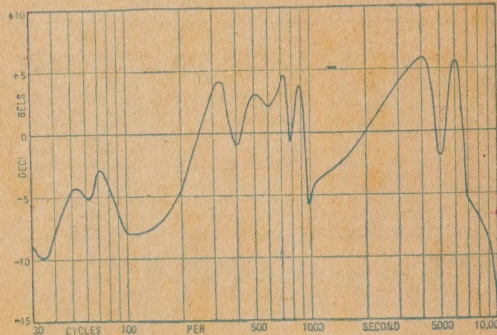

would not become very troublesome. By suitable adjustment of the I.F. channel, &c., I managed to obtain a very pleasing effect with cymbals and things beginning to faintly resemble their true sounds.

On recordings the amplifier seemed as though it had a rising treble characteristic because the high notes were scintillating, that is when you could separate them from needle scratch. This latter condition had me quite peeved for a while because I thought that the thing was all treble and no bass until I played a disc with plenty of cellos and bass drums, &c.

I suppose it wouldn't be a bad idea to mention here the method of speaker loading. It is mounted in a vented enclosure, and is a Rola 8K, which is supposed to have a response from 80 c/s-6.5kc. The enclosure is made to dimensions (roughly) suggested in an article which I think appeared in June or July of 1947. It has a cubic capacity of 3.3 feet and is lined with an old blanket.

I thought it would be interesting to see just what a curve of

## CALLING ALL RECORDISTS!

The SOUND RECORDING INSTITUTE OF AUSTRALIA

announce their

## RECORDING CONTEST FOR 1950

To be held in the Radio Theatre Melbourne Technical School, Friday, November 3rd, 1950, 8 p.m.

Entries for this Contest are invited from all Amateur or Professional Recordists, whether Members the Institute or not, and may be made on Disc, Tape, Wire or Film.

Generous Prizes are offered for the best entries, including COMPLETE PORTABLE DISC RECORDING AND PLAYBACK MACHINE.

Full details and entry forms available from the Institute 4 Parliament Place, Melbourne C.2., where entries should be lodged by Friday, October 13, 1950.

Peter Inglis (Publicity Officer)

## COLLINS RADIO

409 Lonsdale Street, Melbourne

Have the following positions available.

1. Wanted, a young enthusiastic man with a knowledge of radio and amplifier circuits and parts.  
Duties:—  
To sell radio parts over the counter.  
To advise customers on technical problems.  
To prepare parts for dispatch to order customers.  
To answer some mail technical enquiries.  
Applicant must be keen and take a keen interest in and be obliging to customers.  
GOOD PAY AND INCENTIVES to man.
2. Wanted, a junior student of Radio-Physics, to assist in shop and Mail-orders. GOOD PAY and a chance to start in early in a lucrative profession with a great future.  
APPLY by letter in first post stating qualifications, to:—  
R. J. COLLINS.



Special Line of Blanks:—

6" . . . 1/9 8" . . .  
7" . . . 2/6 10" . . .

Write for Price List of Recording Accessories

MANUFACTURED BY "PLAYBACK"


BOX 5041Y, G.P.O., MELB., VIC.



# Tape it Easy
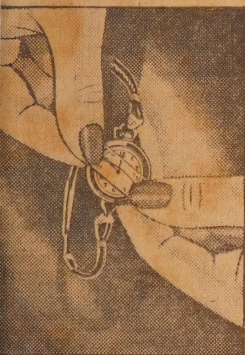
## with DUREX' TAPE

Cracked your watch glass?  
Protect the face temporarily  
with strong, clear  
"DUREX" Tape.



Handy Plaid Dispenser with  
300 ins. 3-in. TAPE. 2/6  
150 ins. 3-in. TAPE. 1/3  
Also a Heavy-Duty Dispenser  
at 15/- plus tax, and a refillable  
plastic Hand Dispenser at 3/-.  
Tape extra.

SEALS WITHOUT MOISTENING

# DUREX

BRAND

## Cellulose TAPE

TRANSPARENT AS GLASS  
AVAILABLE EVERYWHERE

Made in Australia by  
AUSTRALIAN DUREX PRODUCTS  
PTY. LTD., Lidcombe, N.S.W.

07/110

**MODELS:** Technical Engineering Supplies. Diesel, Oil, Steam. Send for latest 2/- catalogue. O. B. Bolton, Room 1, King St., Sydney.

## THE 1950 PENTAGRID FOUR

(Continued from Page 99)

read about it. The important point, however, is that the dial glass must match the type of tuning gang, otherwise the stations will not align up correctly.

You should find that the set will perform remarkably well for the number of valves and the power output should be quite sufficient for general home use. If you encounter slight instability when the volume control is turned up, particularly on a weak station toward the low frequency end of the dial, it could be due to a number of things, notably lengthy speaker leads or the speaker leads running close to the aerial lead.

The point is to keep the speaker leads down to the minimum length necessary for the cabinet installation and away from the aerial lead. Other measures include running a third wire to the speaker earthing the speaker frame and one side of the voice coil to the set.

A more elaborate course involves placing a resistor of about 0.05 megohms between the grid of the 3V4 and the junction of the 0.005 mfd coupling capacitor and the 3 megohm grid resistor. Install a 100 pF. capacitor from the grid of the valve to chassis.

The choice of cabinet is left to the individual. We actually had in mind a table-model size, with the set taking up one half of the cabinet and the speaker and batteries taking up the other half. Incidentally, don't expect the set to do a good job if fed into a small-size speaker. The eight-inch is a good all-round size.

## MODEL PLANE CONTROL

(Continued from Page 86)

same shaft and so arranging the dead spots so that they do not occur at the same place or time.

The unit on the right is the English "Cossor" spring-driven escapement, with the clock-type spring housed in the circular cover at the side, and the magnet system underneath. Two control arms connected one to the elevator and the other to the rudder provide in sequence, up, down, left and right, with a neutral position between each. A pair of switch contacts "made" after each revolution of the main wheel can be used for engine ignition control if required.

## Electronic Torch

**H**OT enough to cut holes in fire-brick or to melt tungsten, a new torch utilizes the action of 1000-mc. radio waves on gases.

An antenna made of two short cylinders, one within the other, leads from the 1000-mc generator. A high-frequency arc can be formed on the end of the antenna.

When certain gases, among them nitrogen and carbon dioxide, are fed past the arc, a flame about 9in long is produced. The arc breaks up molecules of gas atoms. These atoms joining together again on any surface placed in the flame give off heat.

## JABEL PRODUCTS

*are quality products*



insulated Spring Terminals in 6 colours.



Standard trimming and padding condensers. Polystyrene base.



Junior trimmer condenser, Polystyrene base.



Polystyrene Egg Insulator.

## STOCKISTS EVERYWHERE

Factory Distributor:  
Watkin Wynne, North Sydney.

## INSTRUMENT CASES

We specialise in All Classes of Covered Cabinets—Instrument, Portable and Mantel Radio Cabinets in either Leather or Leatherette.

## GIBBONS & DENHAM

122 DARLING St., BALMAIN  
Phone: WB2772, Sydney  
For trade only

## EASY MONEY FOR YOU

Make £6 a week at home in your spare time. Send stamp to-day for details of Special Postal Courses in:—

POTTERY  
MILLINERY  
PLASTICS  
FLOWERS  
SLIPPERS  
GLOVES  
HANDBAGS

CONFECTIONERY  
TOYS & DOLLS  
LINGERIE  
EVENING BAGS  
MOULDING ARTS  
PHOTO COLOURING  
BEADCRAFT

and other Modern Money-Crafts.  
Dept. B, Le Bon College (regd.),  
Box 279, Haymarket P.O., Sydney.

## RADIO DESPATCH SERVICE September Special

These lines are Now Available.

Universal Sewing Machine Motors  
Collaro A.C. 500 Record Changers.  
Hotpoint Radio Receivers, Philips  
and Radiotron Valves, complete range.

All other Radio and Electrical Accessories stocked. Trade supplied.

Phone: MA1876 or call

Wembley House, 841 George St.,  
Railway Square, Sydney.

Printed and published by Associated Newspapers Ltd., at the registered office of the Company, 60-70 Elizabeth Street, Sydney, NSW.



## Electronic Self-loading Camera

THE application of electronics opens new fields in the development of high-speed photography. The increasing use of the Cathode Ray Oscillograph in present day scientific, industrial and atomic research, calls for the recording of traces resulting from transient phenomena occurring in millionths of a second. To record these traces by normal photographic technique would require a film speed unattainable by mechanical means.

The problem has been solved after years of patient research by a British electrically controlled, self-loading camera.

Basically the camera unit consists of a 16in diameter drum, housing two spools with a total capacity of 100ft (30.48m) of 35 mm film, together with an automatic reloading mechanism. A 4.5in (139.7 mm) f/1.9 anastigmatic lens is fitted and the camera controls are centralised on an electronic control unit which is self-contained.

Operation of the camera is exceedingly simple. A motor is started; the drum slowly revolves. Electronic control is brought automatically into operation; speed increases; a rate of 3600 rpm is achieved. A triggering mechanism releases the cathode ray tube beam and an exposure is made (each exposure involves one complete revolution of the drum). The cathode beam is deflected, the drum reloaded. The camera is set for the next recording.

World's best stories,  
novellettes in **6D**  
Pocket Book Storyteller

YOUR AMPLIFIER, RADIO, TESTING EQUIPMENT OR  
LABORATORY INSTRUMENTS NEED THE ULTIMATE IN



## TRANSFORMERS

"NOVA" can help you in the minimum time, or cost, with any type of transformer to your own or our design, to suit your requirements.

Williamson & "Parry" Cathamp. output transformers to the designers' specifications.

Variable Transformers, up to 4 K.V.A.

Current Transformers for testing equipment or switch-board type made to order in any range.

Contact Your Dealer or

**NOVA ELECTRICAL & ENG. CO.,**

311 SUSSEX STREET, SYDNEY

MA 1756



## COYNES ELECTRONICS

A practical Instruction Manual for Home Study and Job Use for men in Radio and Electricity covering: OPERATION—INSTALLATION—MAINTENANCE TESTING—TROUBLE SHOOTING. Price, 38/6.

Exclusive Representatives:

**ASSOCIATED TRADE JOURNALS COMPANY**

FRAZER HOUSE, 42 BRIDGE STREET, SYDNEY, N.S.W.



## Wanted to Buy, Sell or Exchange

**EXCHANGE:** Complete Radio Eng. Course, 44 Copies R & H Valves, including (1D8GT, new), 6v. Trans. and sundries, for small receiver, S. Ireland, 90 Asquith St., Auburn, N.S.W.

**EXCH.:** Valves EBF35, EK32, 6SN7GT, (2) 6X5GT, 6SJ7GT, (2) P30 Trans. (2) 7" Speakers and require XG1M, 6SK7GT, 6SQ7GT, 5Y3GT, 7" speaker (Trans. 240v. Prim., 290v. sec., 60mA), pair IF Trans. Ring LU1386 and I will call.

**FOR SALE:** Thornton Pickard 1 p camera, F8 lens, 3 double P. holder. Working order. £20 or offer. B. Champion, Nowra, N.S.W.

**FOR SALE:** Two 12-volt 500-watt generators. Good condition, but have no further use for them. Offer. Loveday, Elmhurst, Q.

**FOR SALE:** Movie Projectors (silent, 35mm, £17. 16mm, £45. No. 5403, Sun Advertising.

**FOR SALE:** R. & H. Feb. '47 to May '50. Incl. S.W. Handbook, minus March '47 and Jan. '48. Price £2/10/-, 141 Carlingford Rd., Epping, N.S.W.

**SALE:** 5-valve A.C. Stromberg Carlson Aust. wide B/c receiver—£10. 2-valve battery set with speaker, £74. L. Davies, Southport School, Southport.

**SALE:** ARB Receiver A. Cook, 490 Kooyong Rd., Caulfield, Vic. XM2724.

**SALE:** Lexington m/c Pick-up, transformer, laboratory equaliser, 8 saphires, £20 or offer. A. Joachim, 17 Huntingfield Road, Brighton, XB3349.

**SALE:** Radio College Ham Operators' (AOCOP) Course, PMG Key, Morse Oscillator and phones, £5. D. Adams, 81 Beaumont St., Hamilton, N.S.W.

**SELL:** New 12w. amp. G12 SPKR, £17. New 5v. A.C./B.C. Mantel Chassis, £13. G12 SPKRS £4; each. A. W. Fuss, 49 Balmaln Rd., Leichhardt, N.S.W.

**SELL:** Radio and Television Course, and set three volumes Radio and Television, all new. Cost £23, take £10. Sell separately. Davies, Bronte Pk., Tas.

**SELL:** R. & H. most copies since 1941. Single copies or as a whole. Stamped addressed envelope for reply. W. MacGillcuddy, 23 Bangs St., Prahran, Melbourne.

**SELL:** Rola 5" spkr., 1500 field, 45 m. at 10/- ea.; 2 "H" 2-gang cond. DA5 glass, at 7/6; Tasma baby 3v. chassis with R.F. less cabinet and series, £5/10/-, or offer. Details call T. A. Walker, Dulacca, W. Line, Q.

**SELL:** Phillips Push-Button Tuner, complete with instructions, £4/10/-, Aerial Coil Kit (special) new to 200m in 3 bands, (3 stage), £9/10/-, Reed, 10 Edgar St., Brighton, Vic.

Readers wishing to buy, sell or exchange goods are invited to insert an advertisement on this page. The cost is 1/6 per line; approximately 5 words to a line. Advertisements for the next issue must reach our office by NOON WEDNESDAY, September 12, 1950. Details Advertisements not accepted.

**SELL:** 807 Triode Amplifier with control stage, "Axiom Twin Twin Speaker, Decca FFRB PU, imaginary brand new. HMV rim-driven gramophone motor. "Rola" 12" speaker with OP25 10,000 ohm 2 PP Transformer. "Vox Minor" 41-watt Amplifier, complete with Xtal PU and Ampion 12" Speaker. Best offers, Sunday or Tuesday only. Vivian, 37 Kensington Rd., Summer h.

**SELL:** Two good Type 3 Mk. II Transceivers, with modulators and Power Packs. AR7 with ANL, EF50 PU. Supply, coil cabinet. Will sell separately. What offers? L. M. Bills, Gawler, S.A.

**SELL:** Transceivers, 2-FS6 cond. New, Aerial, Wavemeter, £35 Lb. West, 2 Queen's Rd., S.C.2., Melb.

**SELL:** Brand New Collaro Electric turntable and Crystal Pick-up 67/10. Davies, 83 Fourth Ave., St. Peters, S.

**AERIALS ELIMINATED**

The CAPTAIN AERIAL UNIT gives a 50% high aerial, even tone, volume, sensitivity, more stations, freedom from lightning, static, fits inside your set. Do away with poles and wires, Broadcast or short-wave reception. Install in a minute—nothing to get out of order. **PRICE ONLY 6/9.** Registered Post Free. No C.O.D. Money Refunded if Not Satisfied.

**REG COOKE,**  
P.O. Box 9 (H), Gerringong, N.S.W.



**CAMERA  
COVER OF  
WORLD EVENTS**

**PIX**  
EVERY **6D**  
MONDAY